

Course Outline





- Semiconductor Industry and Technology Overview
- IC Design Flows
- **Timing in Digital Systems**
- Front-end Design Flow
- Back-end Design Flow
- Interconnection and Signal Integrity
- Low-Power Design
- Design-for-Testability (DFT)
- Based on “Introduction to VLSI Design” slides by Professor Yusuf Leblebici of the Microelectronic Systems Laboratory (LSM) and others.

Synchronous vs. Asynchronous Systems


- **Synchronous Systems**
 - All memory elements are simultaneously updated using a global clock signal
 - Functionality is ensured by strict constraints on the clock generation and distribution
- **Asynchronous Systems**
 - Self-timed systems with no global clock but have asynchronous circuit overhead (e.g., handshaking logic)
- **GALS**
 - Hybrid systems that are global asynchronous with no common clock between blocks, while each block is locally synchronous.

Synchronous Digital Logic

 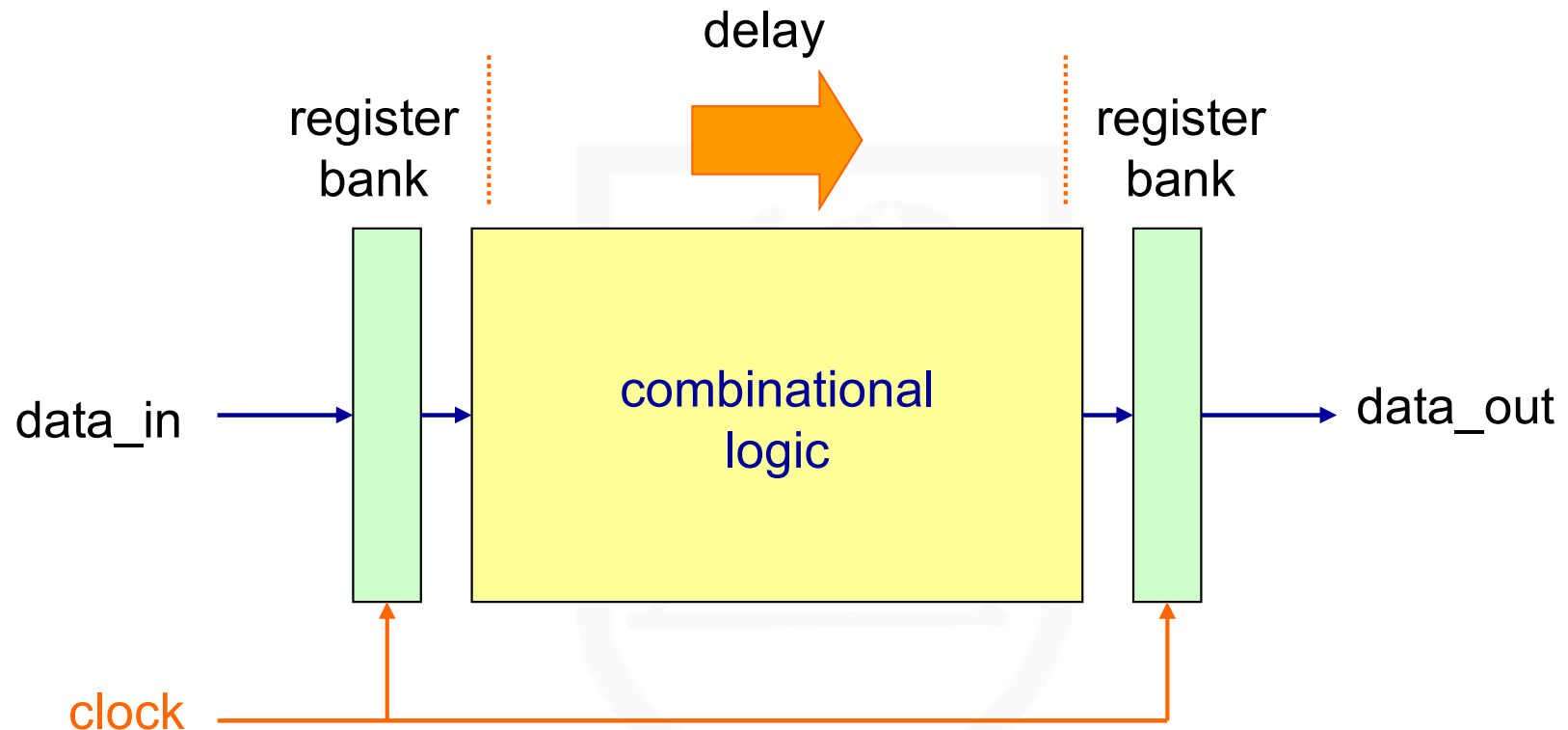

The clock period cannot be shorter than the delay of the combinational block !


Pipelined Digital Logic

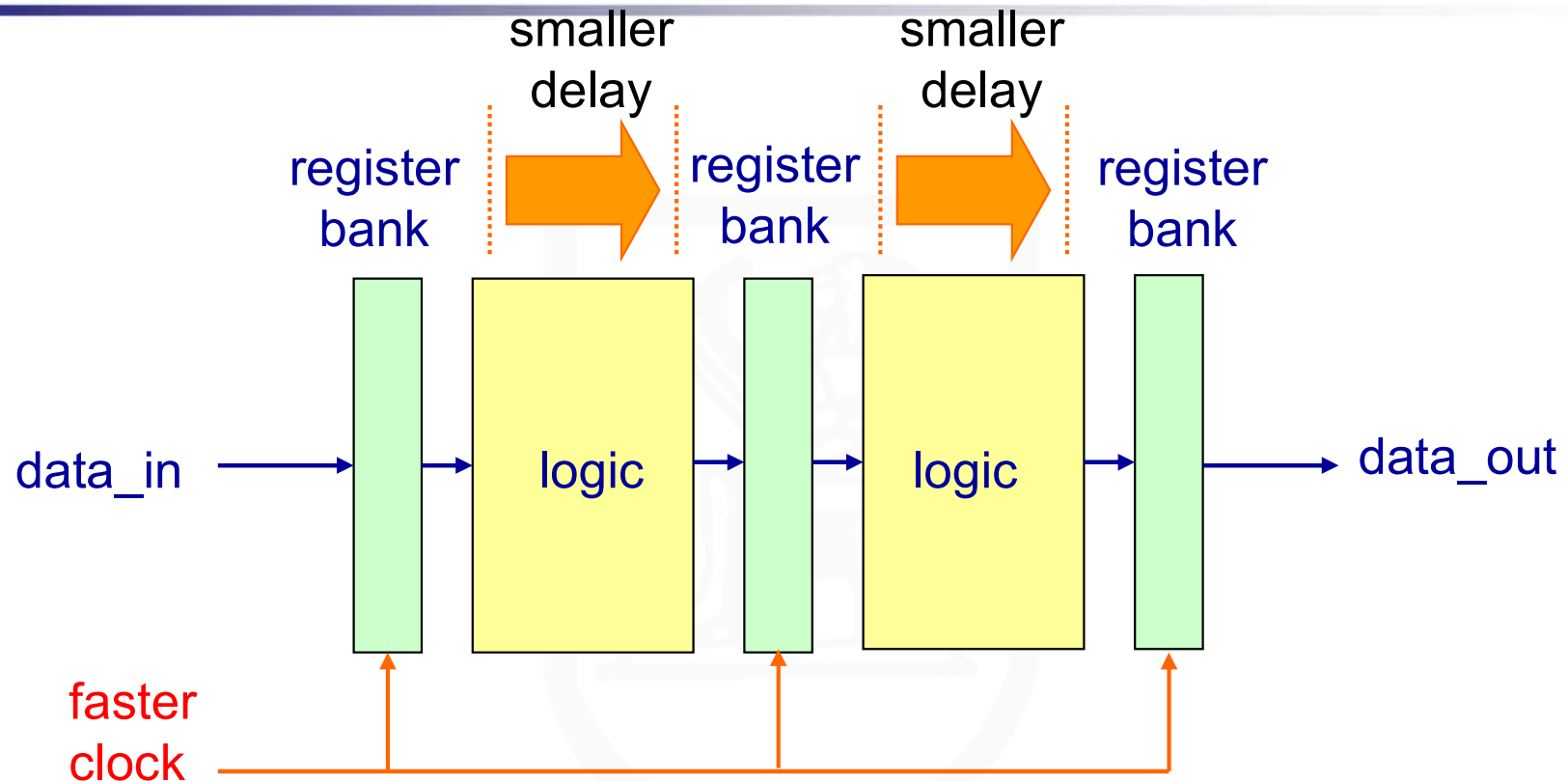

Pipelining results in smaller stage delays between register banks, and consequently, faster clock frequencies → System **throughput** increases !

However, **latency** also increases slightly and hardware overhead grows as a result of additional registers and clock distribution network.

Clocked Logic Example

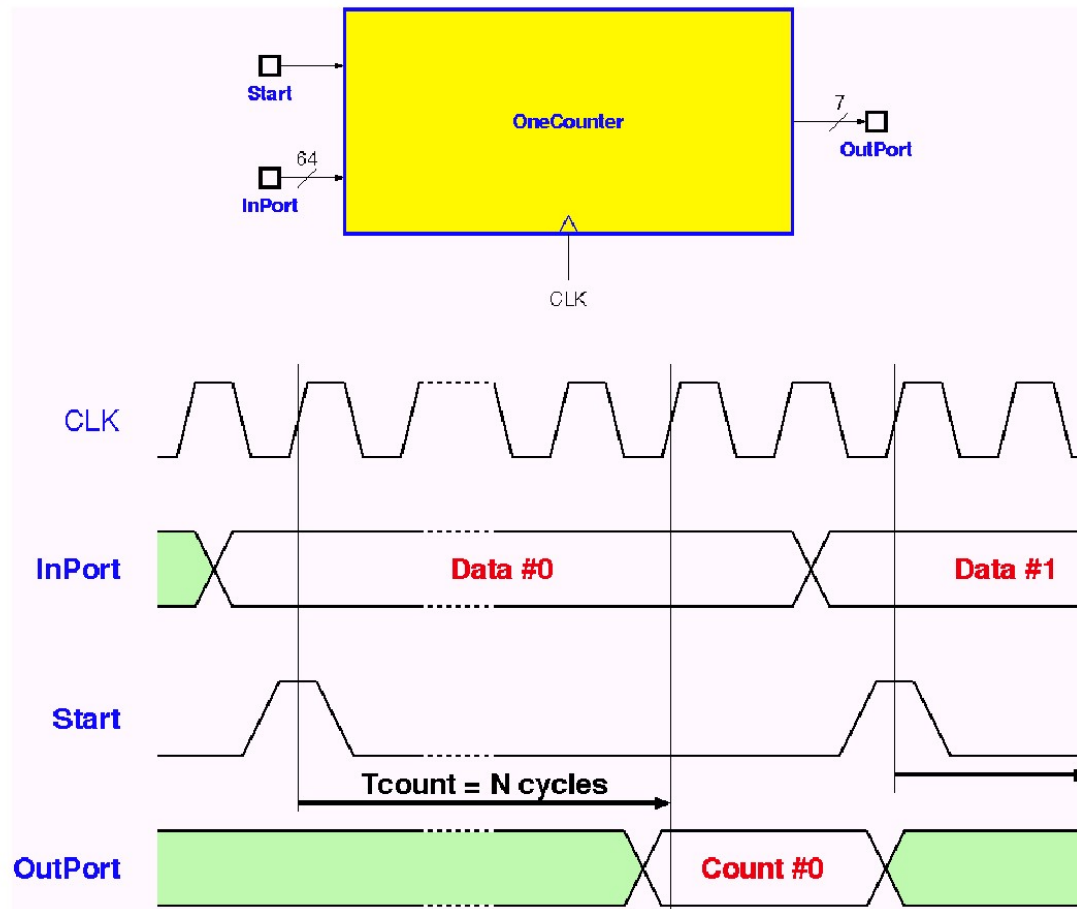

Parallel Counter


Example:

if **InPort** is
 $1248c6391248c639_{16}$
then **OutPort** must be
 $0011000_2 = 24$

Number of cycles
(N) is unspecified

There is always more than one way of solving a problem !



Clocked Logic Example

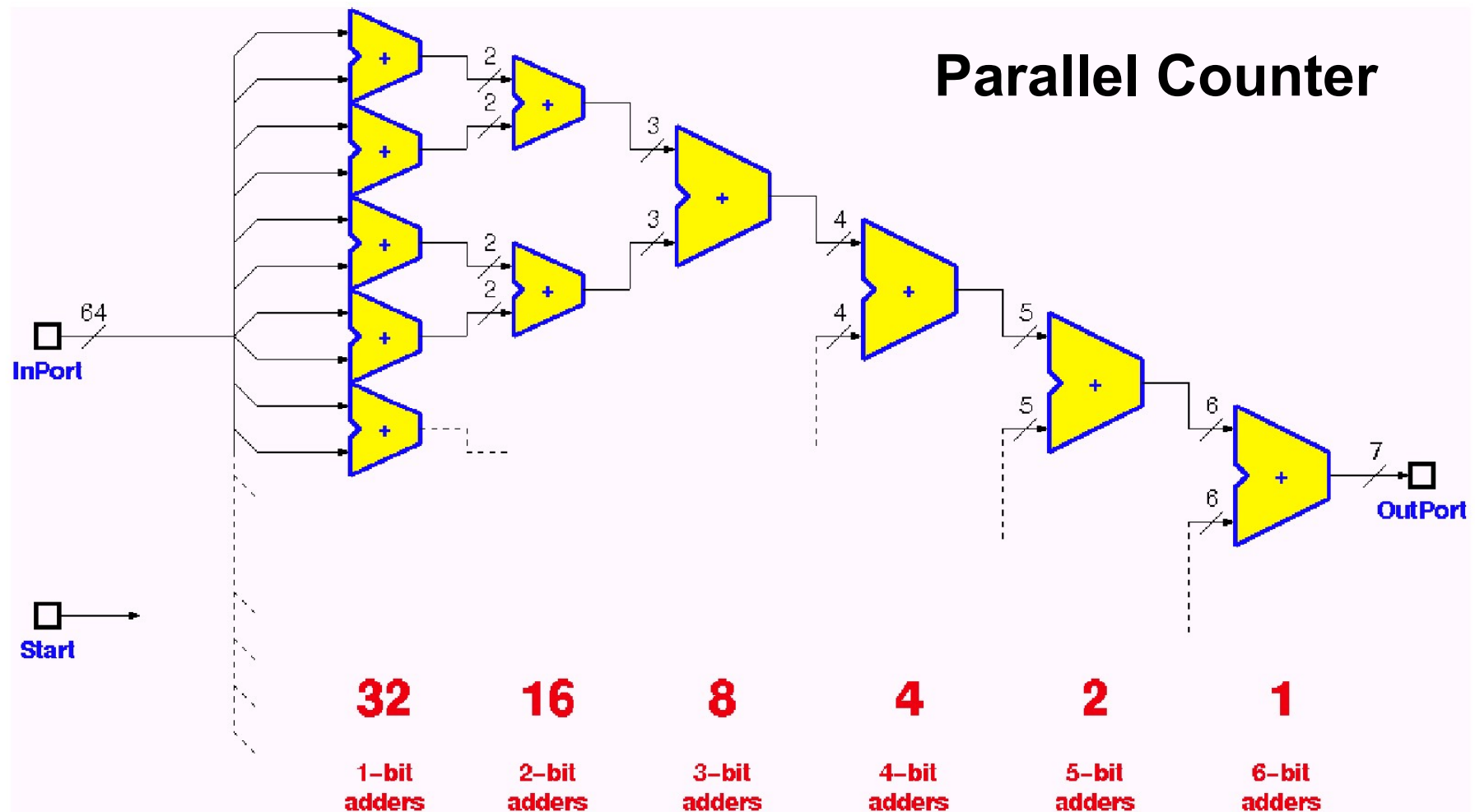


Much faster but also complicated hardware !

Latch versus Register

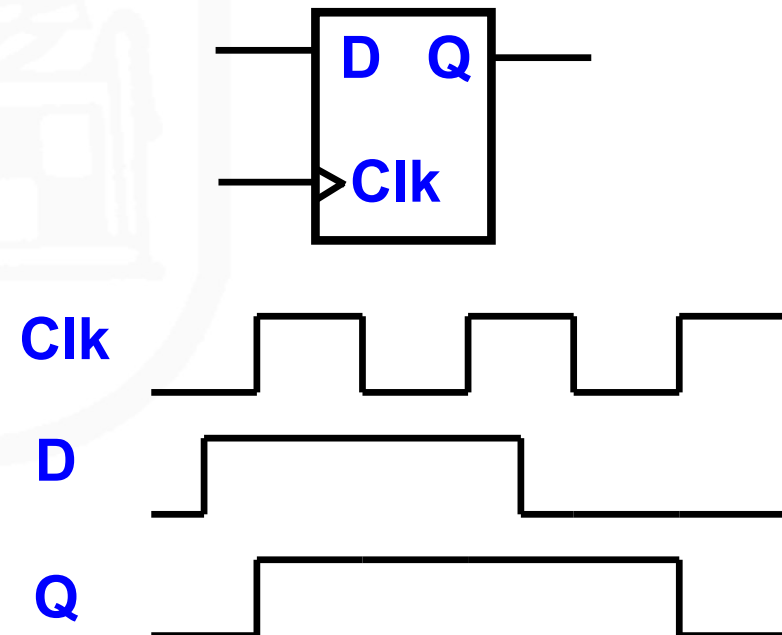 
- **Latch**
stores data when clock is low
- **Register**
stores data when clock rises



Characterizing Timing

 


Latch

 


Register

Latch Parameters

 


Delays can be different for rising and falling data transitions

Register Parameters

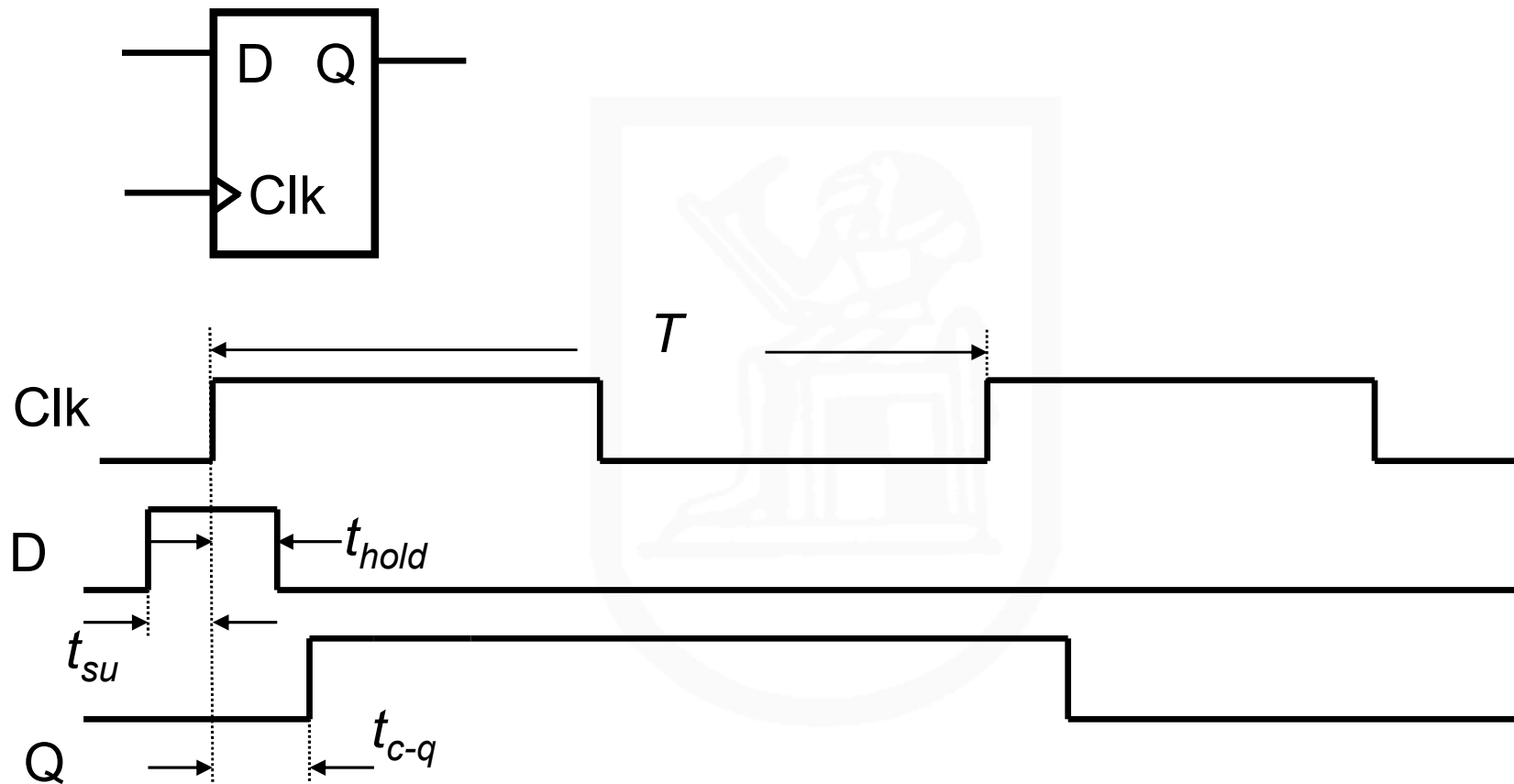


Delays can be different for rising and falling data transitions

Positive Feedback: Bi-Stability

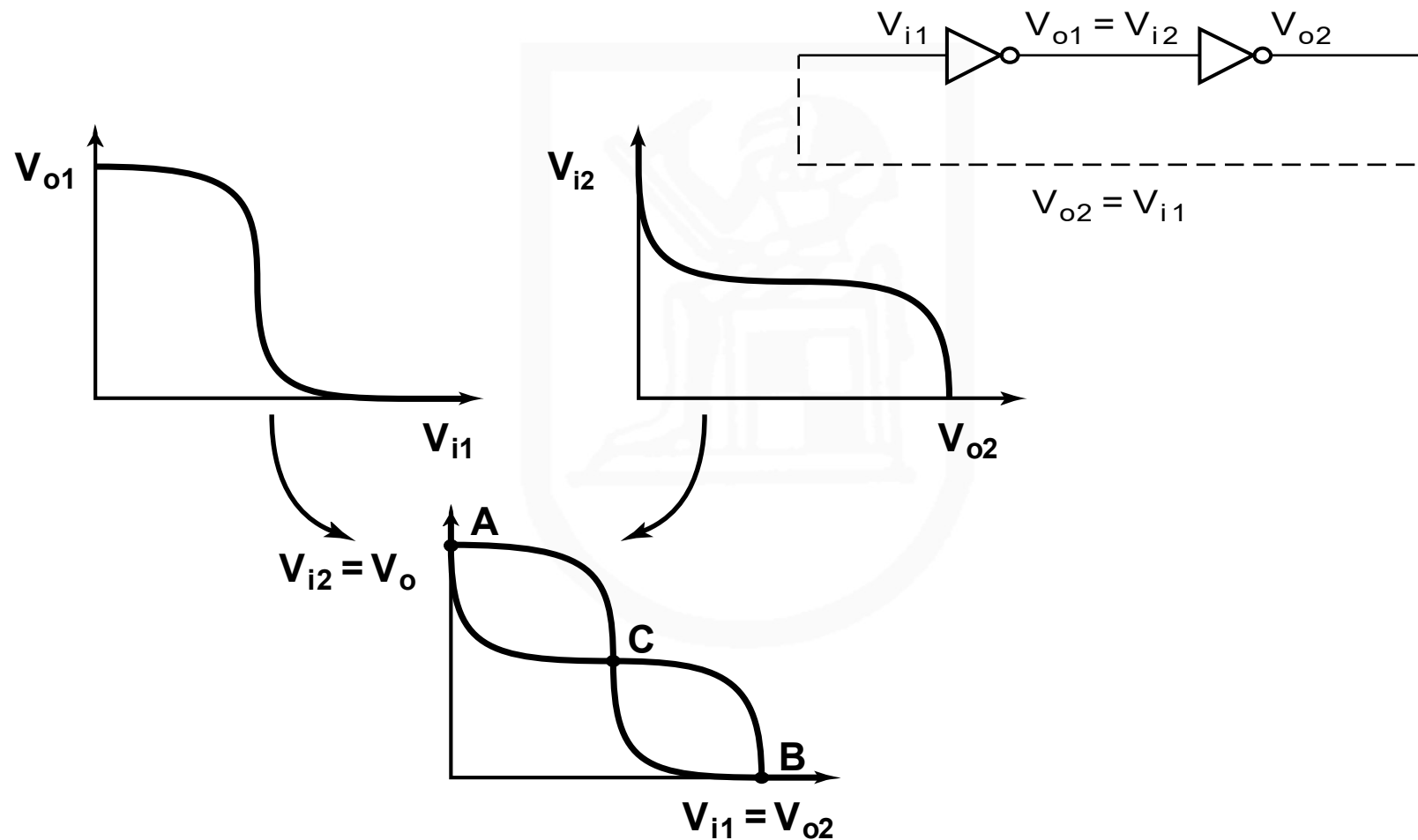


Meta-Stability

 

Gain should be larger than 1 in the transition region

Writing into a Static Latch

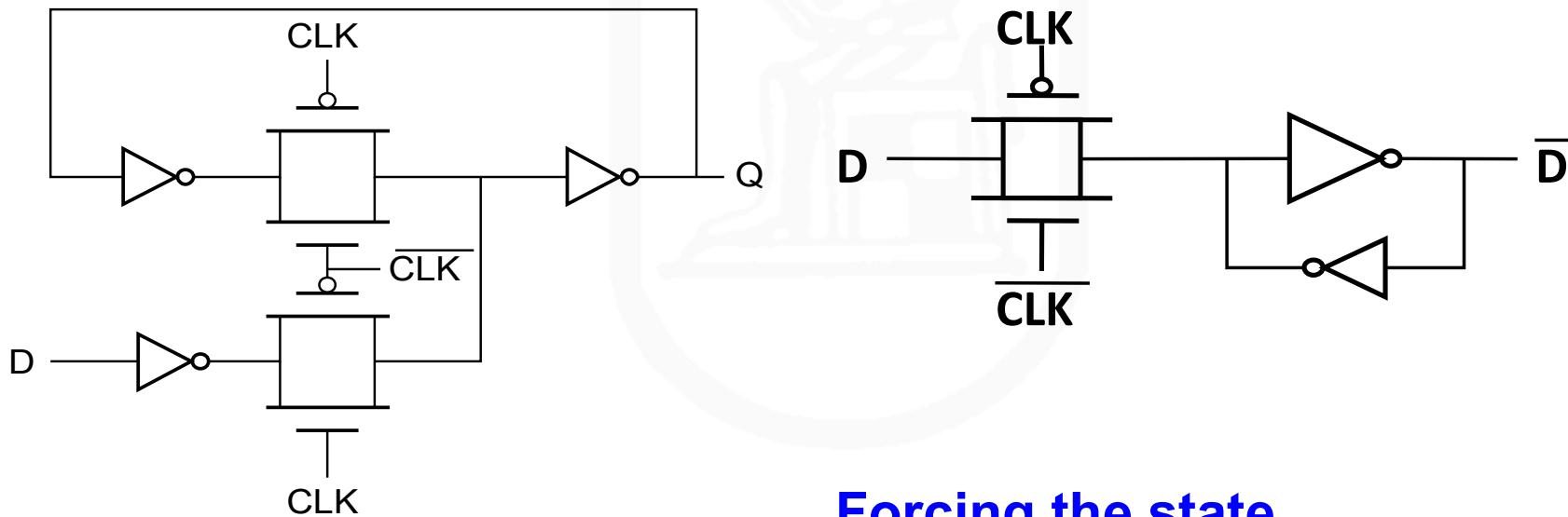Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Converting into a MUX

Forcing the state
(can implement as NMOS-only)


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$

Mux-Based Latch

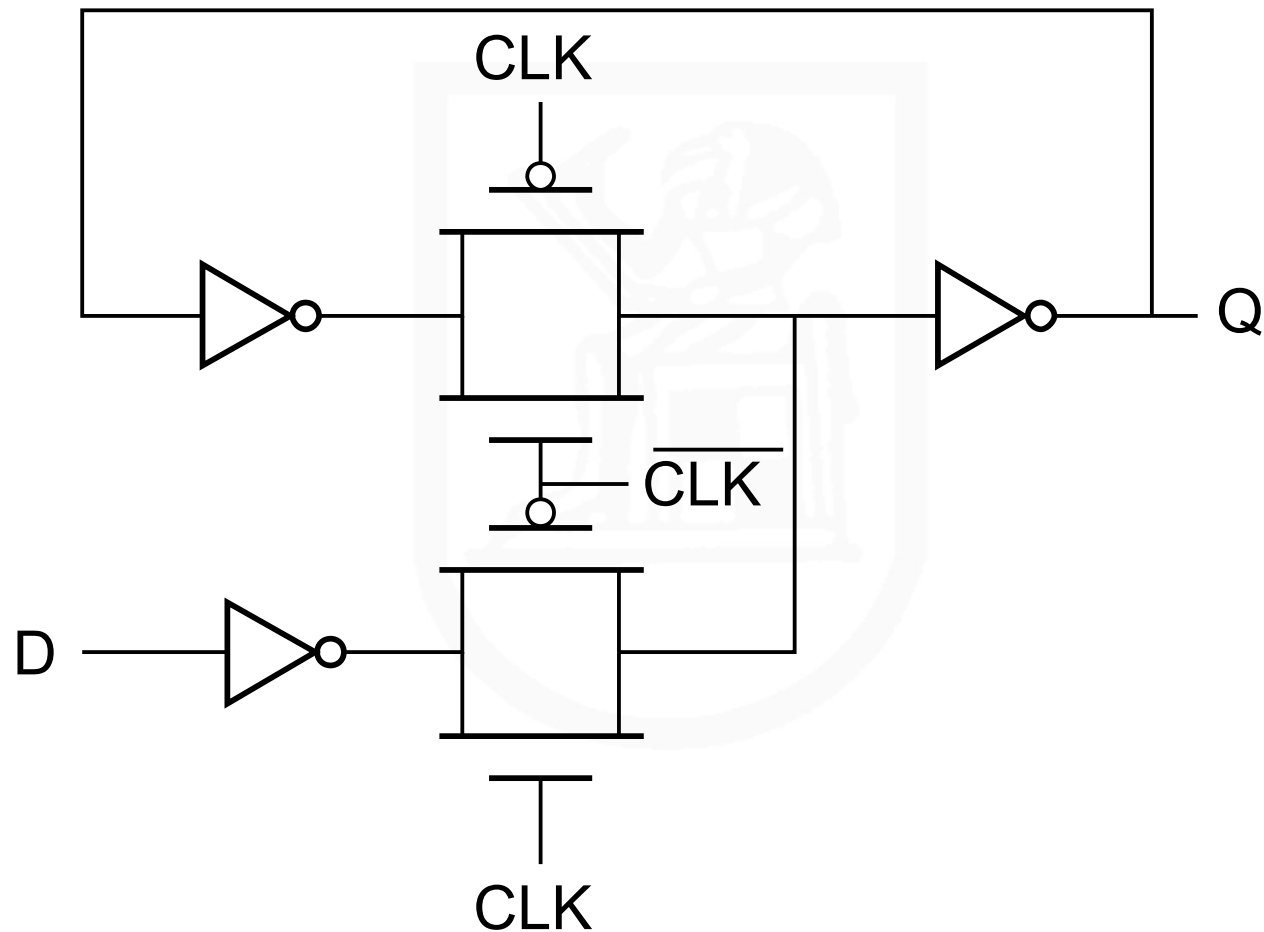


Mux-Based Latch

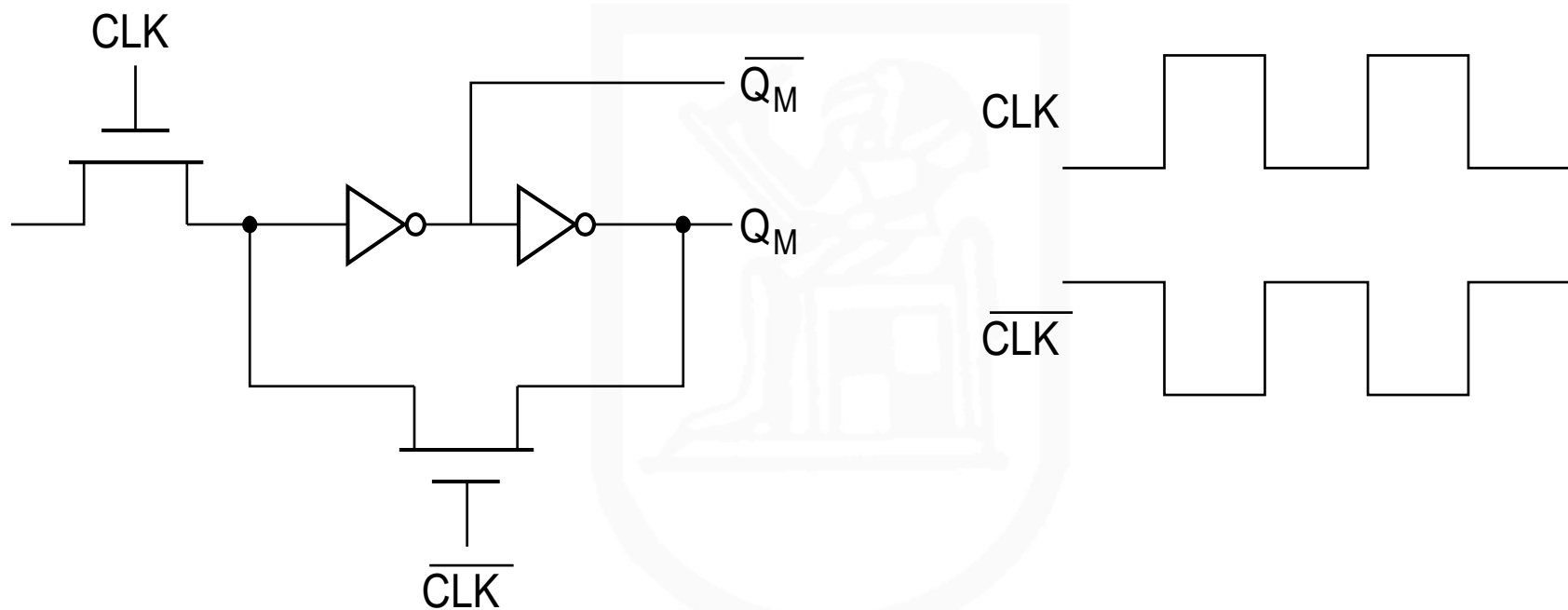

NMOS only


Non-overlapping clocks

Master-Slave (Edge-Triggered) Register

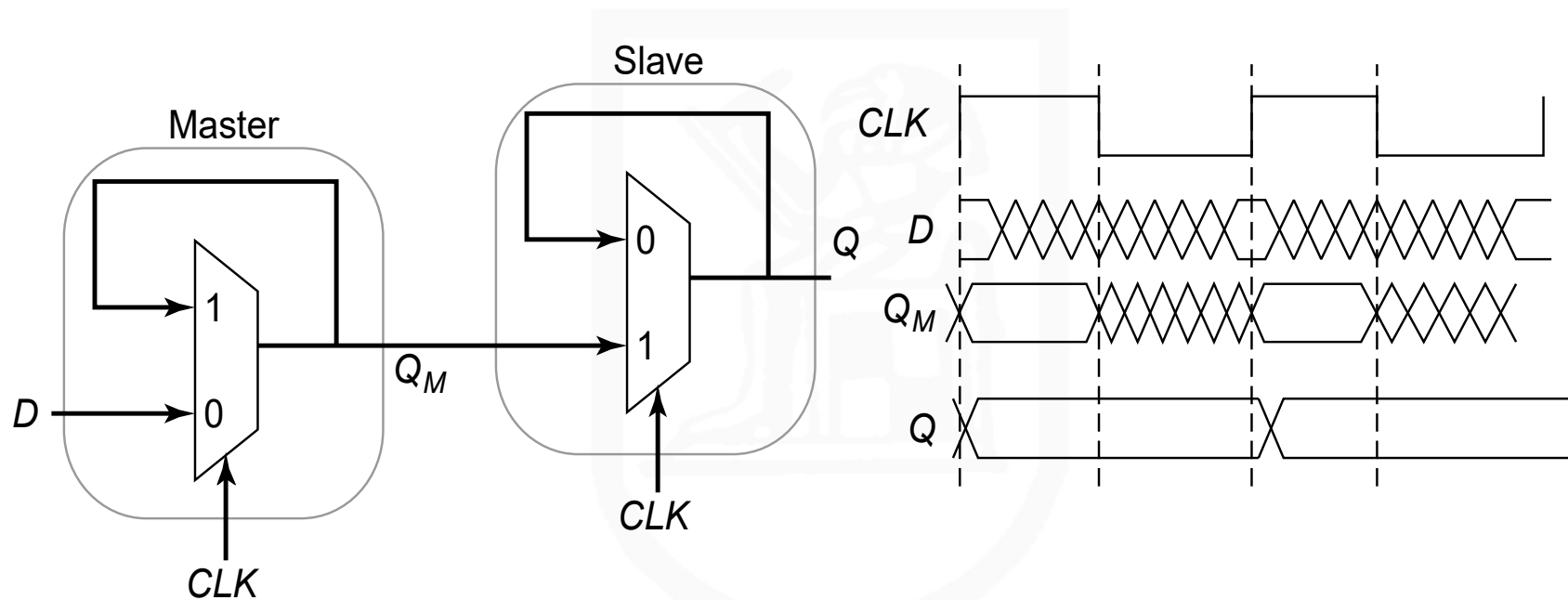

Two opposite latches trigger on edge also called as master-slave latch pair


Master-Slave Register

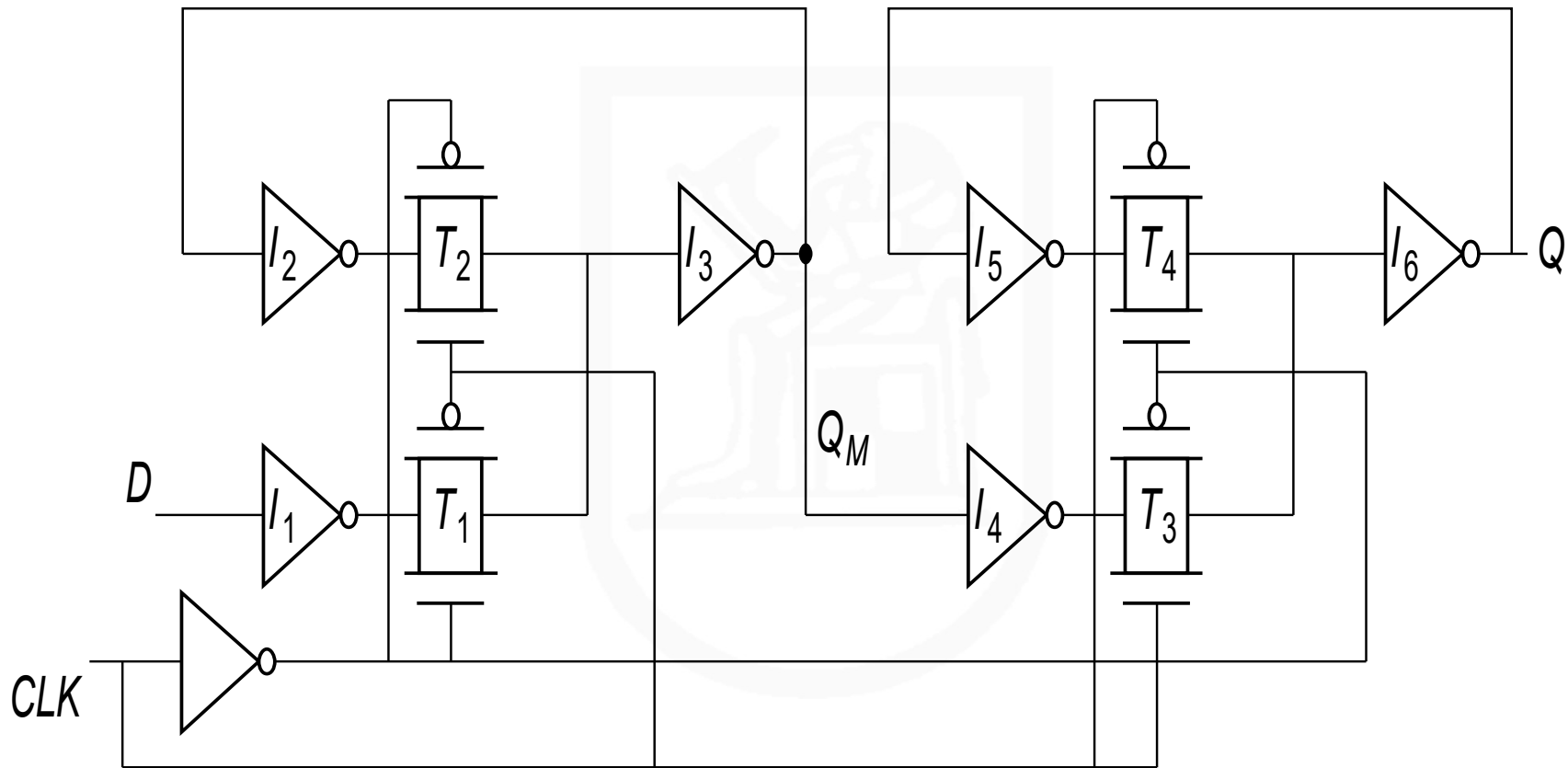


Multiplexer-based latch pair

Storage Mechanisms

Static

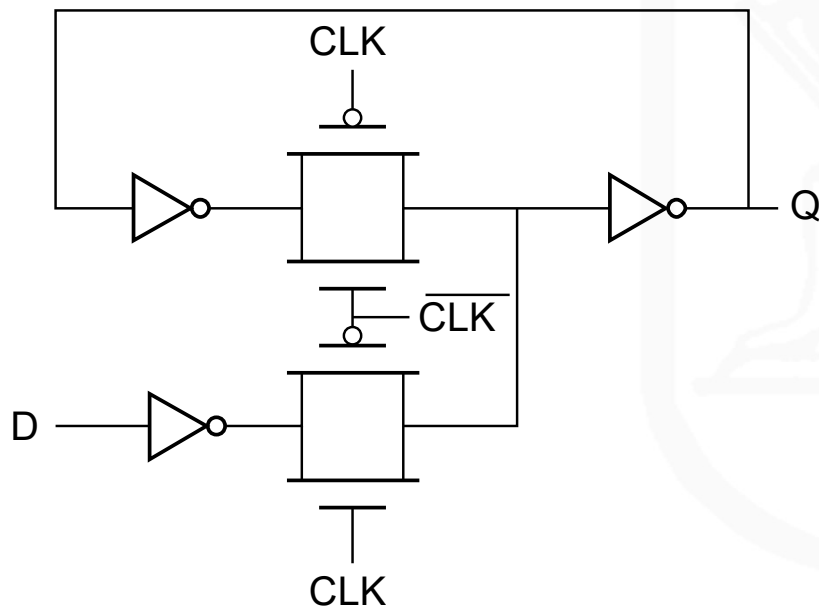


Dynamic (charge-based)

 


Critical Path

 The clock speed is determined by the slowest feasible path between registers in the design, often referred to as *the critical path*.




Critical path is longer with increased *logic depth* (# gates in series)

Pipelining

 


Reference

 

Pipelined

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Clock Uncertainties

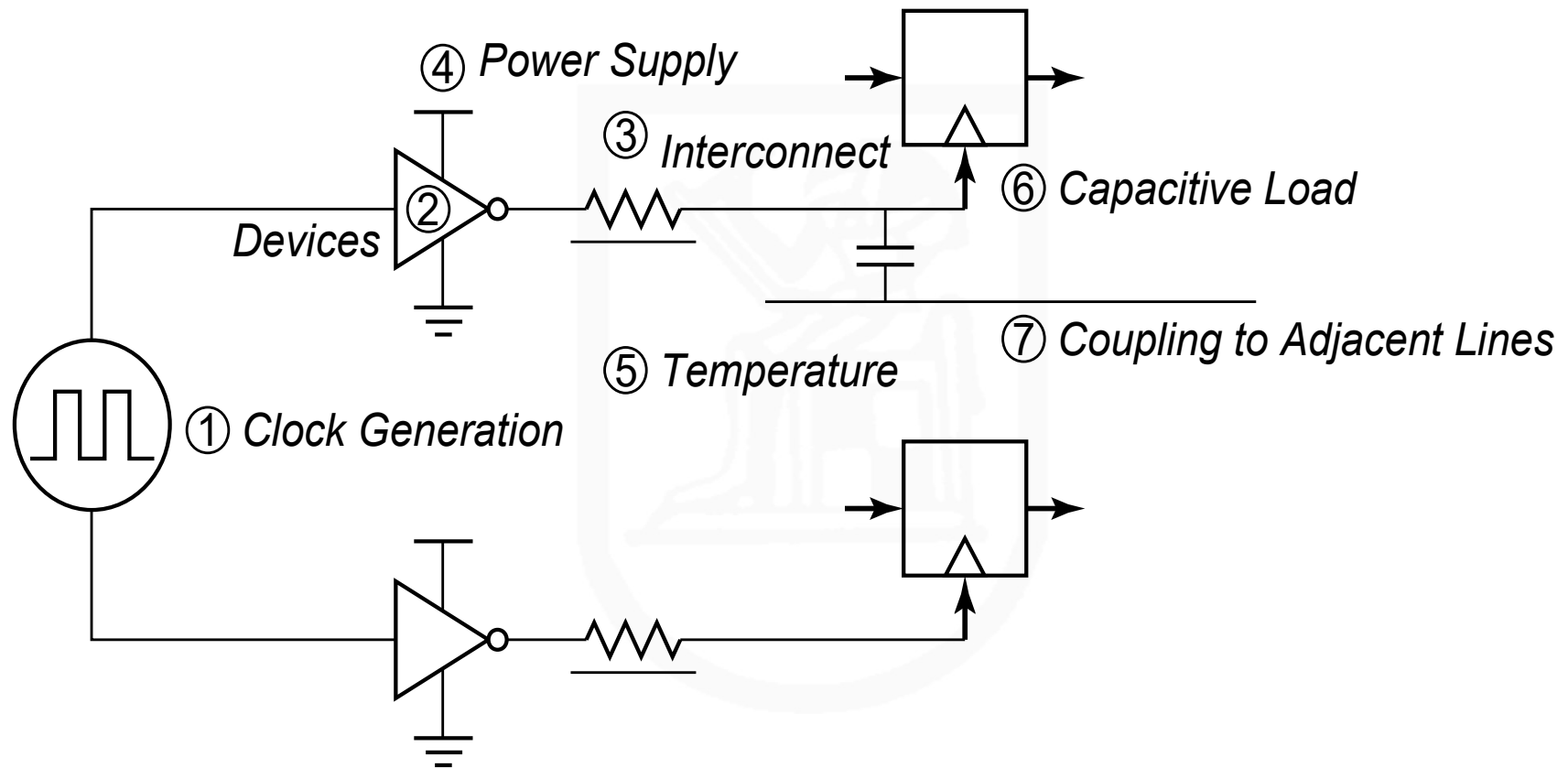

Sources of clock uncertainty

Clock Nonidealities

- **Clock skew**

- Spatial variation in temporally equivalent clock edges; deterministic + random, t_{SK}
- Skew is constant from cycle to cycle by definition.

- **Clock jitter**


- Temporal variations in consecutive edges of the clock signal; modulation + random noise
- Cycle-to-cycle (short-term) t_{JS}
- Long term t_{JL}

- **Variation of the pulse width**


- Important for level sensitive and mixed-edge clocking

Clock Skew and Jitter

 
- Both skew and jitter affect the effective cycle time
- Only skew affects the race margin




Clock Skew

 

Positive and Negative Skew

 


(a) Positive skew

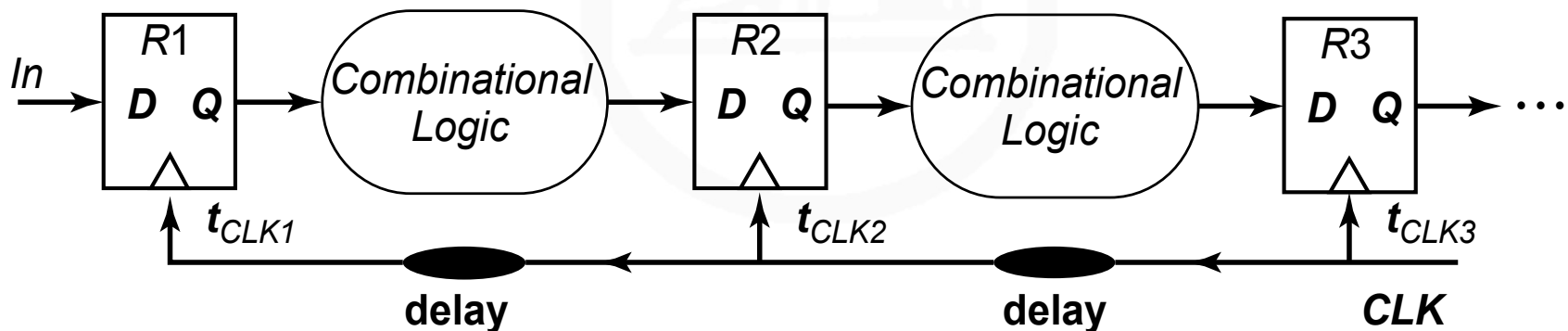


(b) Negative skew

Positive Skew

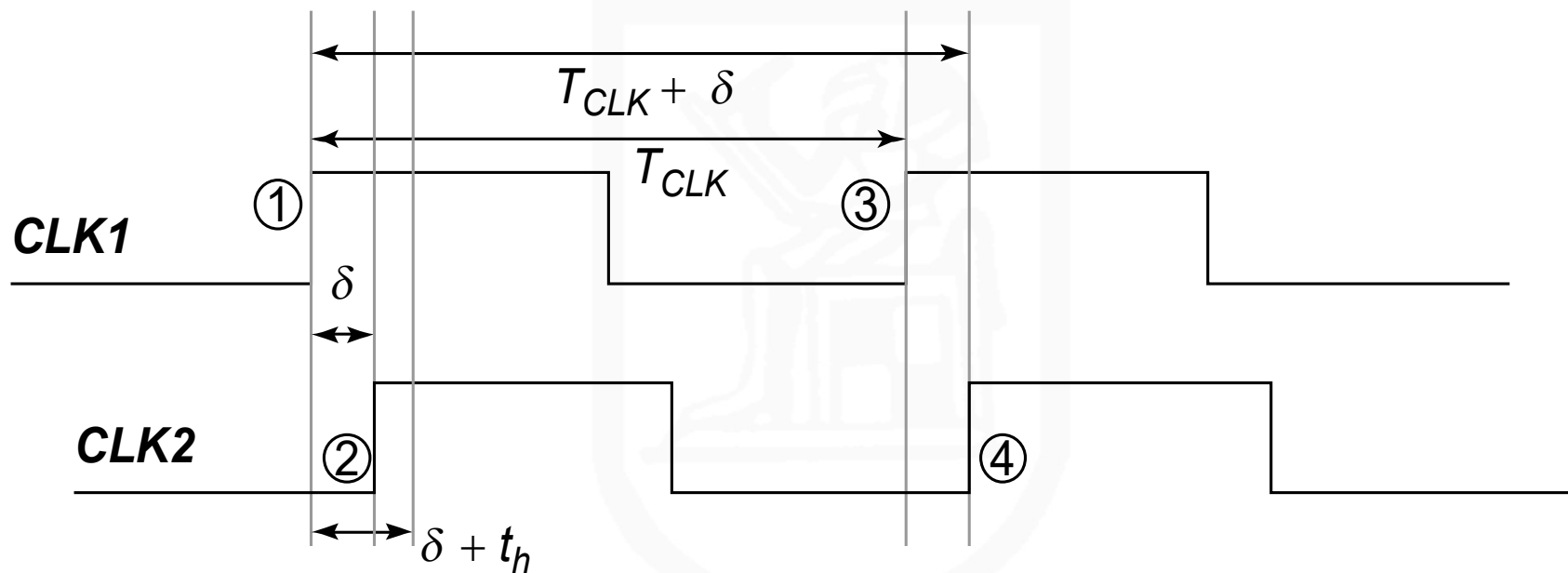


Launching edge arrives before the receiving edge

Negative Skew

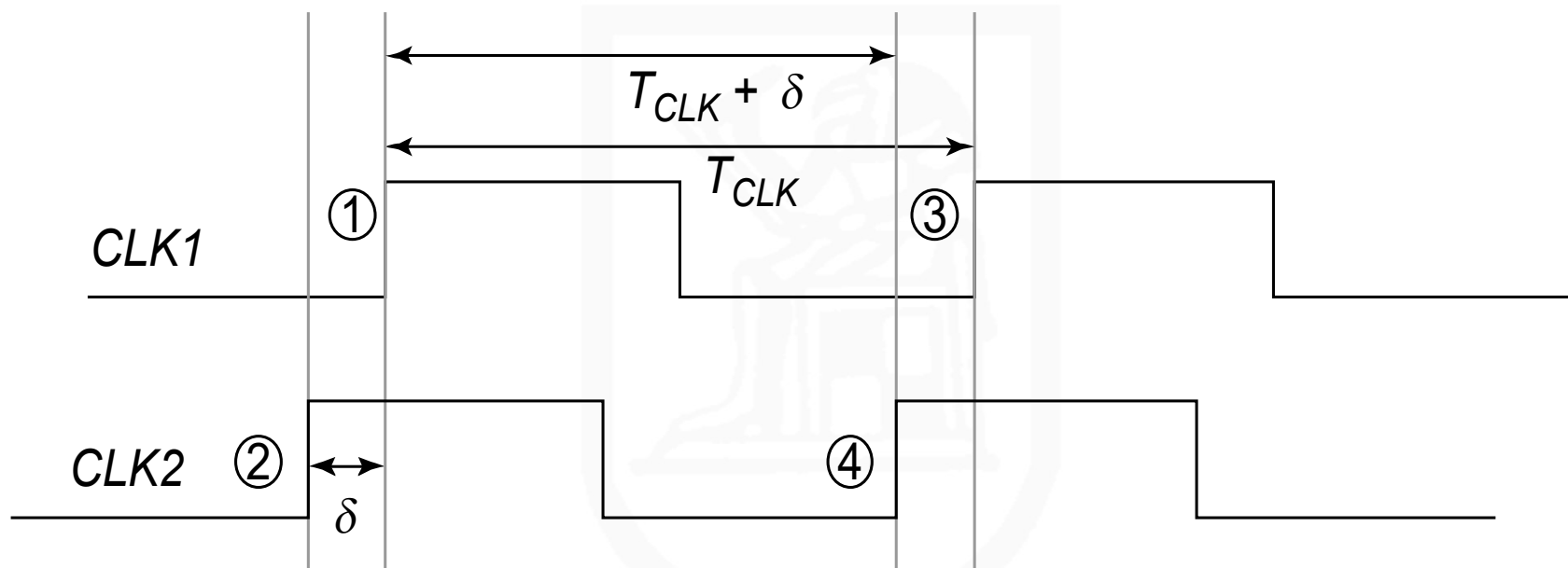

Receiving edge arrives before the launching edge

Timing Constraints

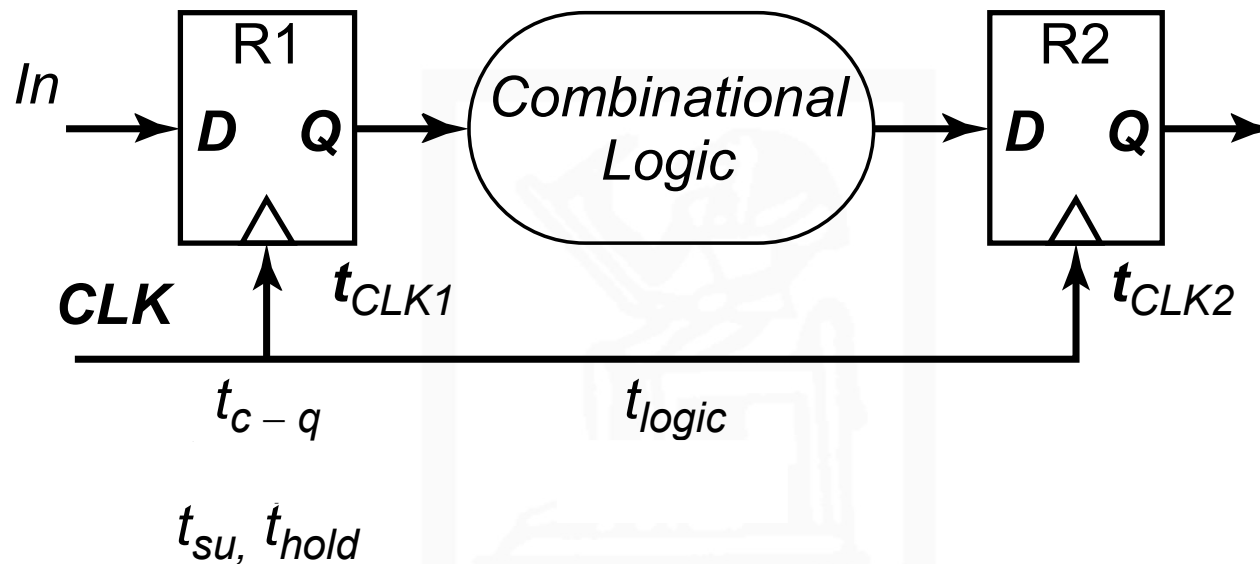

Minimum cycle time:

$$T_{CLK} + \delta > t_{c-q-max} + t_{logic-max} + t_{su}$$

Worst case is when receiving edge arrives early (negative δ)


Preventing Set-Up Violations

- **Set-up violation:**

Logic is too slow for the correct logic value to arrive at the inputs to the register on the right before one set-up time before the clock edge

- **Constraint to prevent this:**

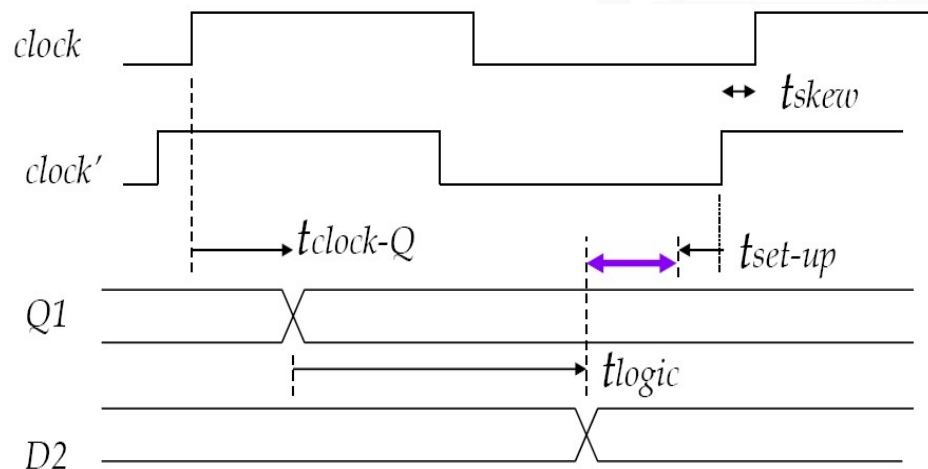
$$t_{clock} \geq t_{clock-Q-max} + t_{logic-max} + t_{set-up} - t_{skew}$$



The amount of time required to turn '>' into '=' is referred to as **timing slack**



Timing Constraints

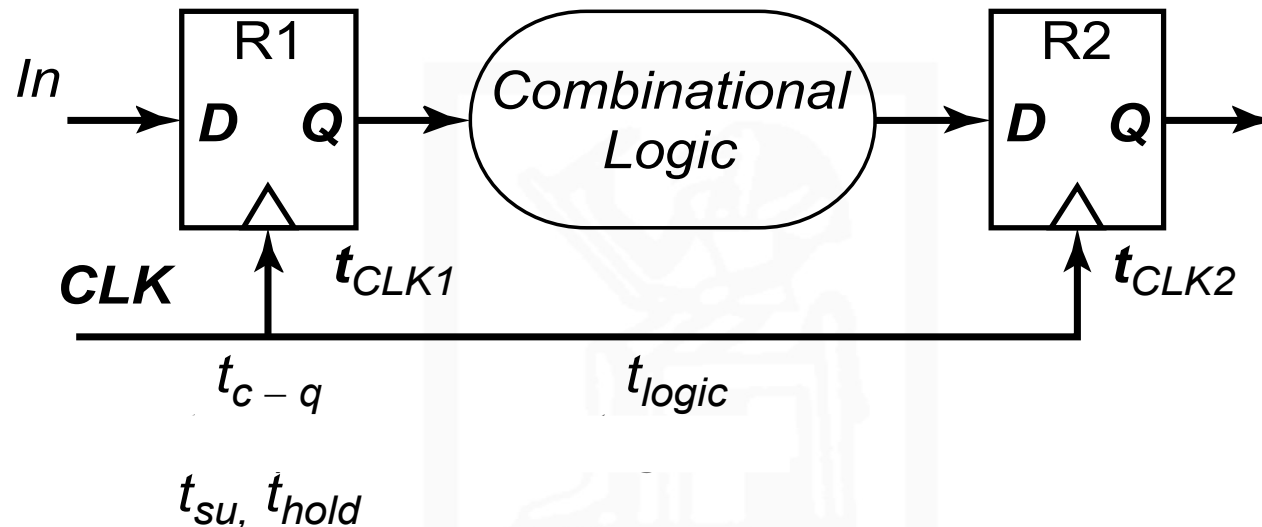


Hold time constraint:


$$t_{c-q-min} + t_{logic-min} > t_{hold} + \delta$$

Worst case is when receiving edge arrives late
Race between data and clock

Impact of Jitter

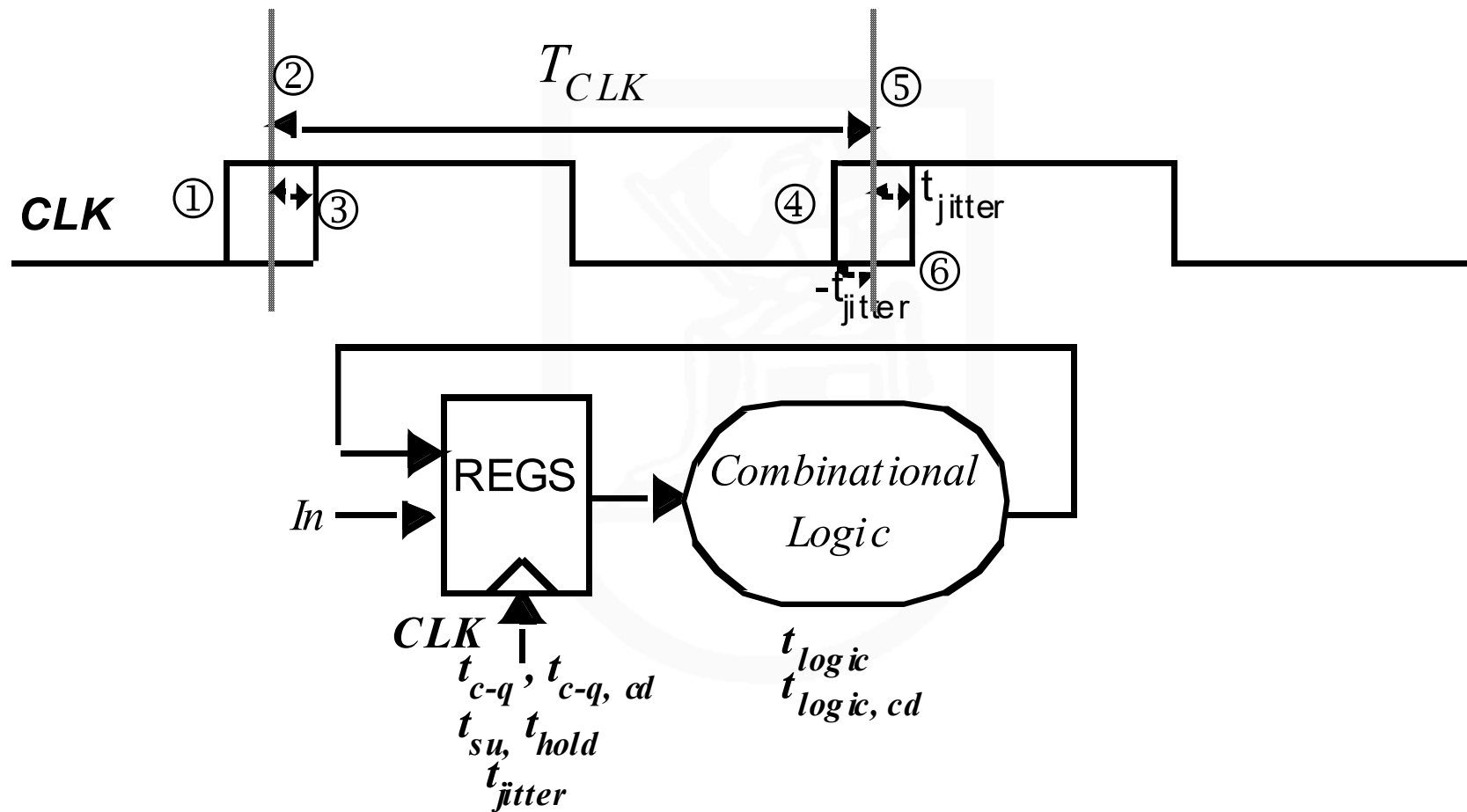

Impact of Jitter: Longest Logic Path

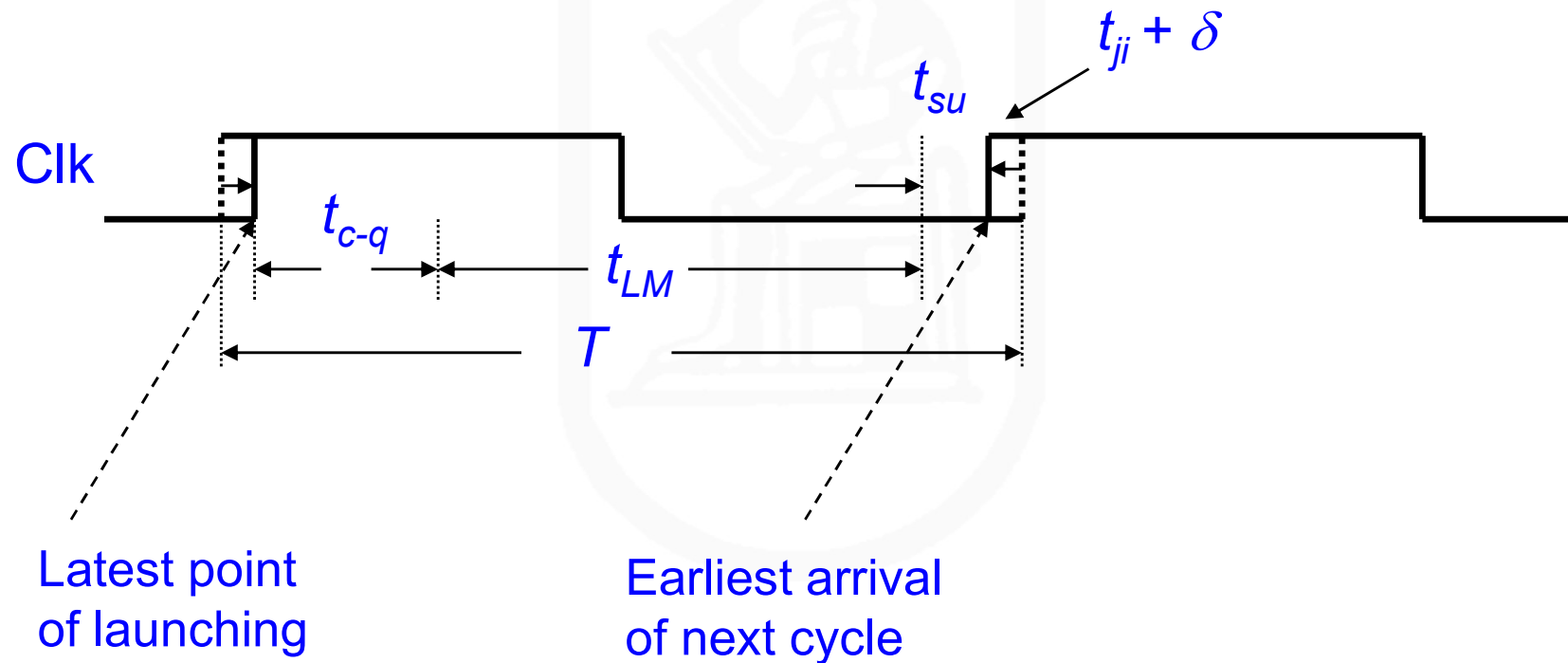

Clock Constraints in Edge-Triggered Systems

If launching edge is late and receiving edge is early, the data will not be too late if:


$$T_{\text{CLK}} + \delta > t_{\text{c-q}} + t_{\text{LM}} + t_{\text{su}} + t_{\text{ji},1} + t_{\text{ji},2}$$

Minimum cycle time is determined by the maximum delays through the logic

$$T_{\text{CLK}} > t_{\text{c-q}} + t_{\text{LM}} + t_{\text{su}} - \delta + 2 t_{\text{ji}}$$

Skew can be either positive or negative

Shortest Path

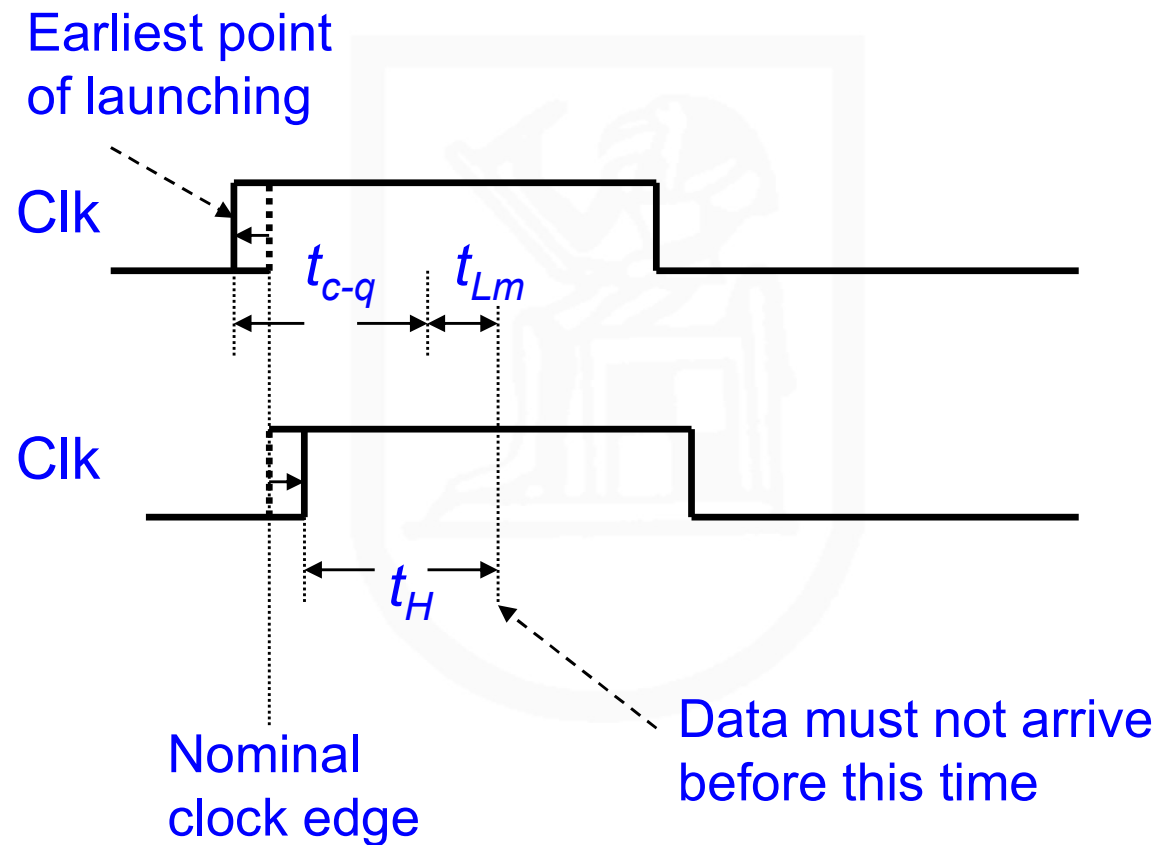


Clock Constraints in Edge-Triggered Systems

Minimum logic delay


$$t_{c-q} + t_{Lm} > t_{hold} + \delta$$

How to counter Clock Skew?

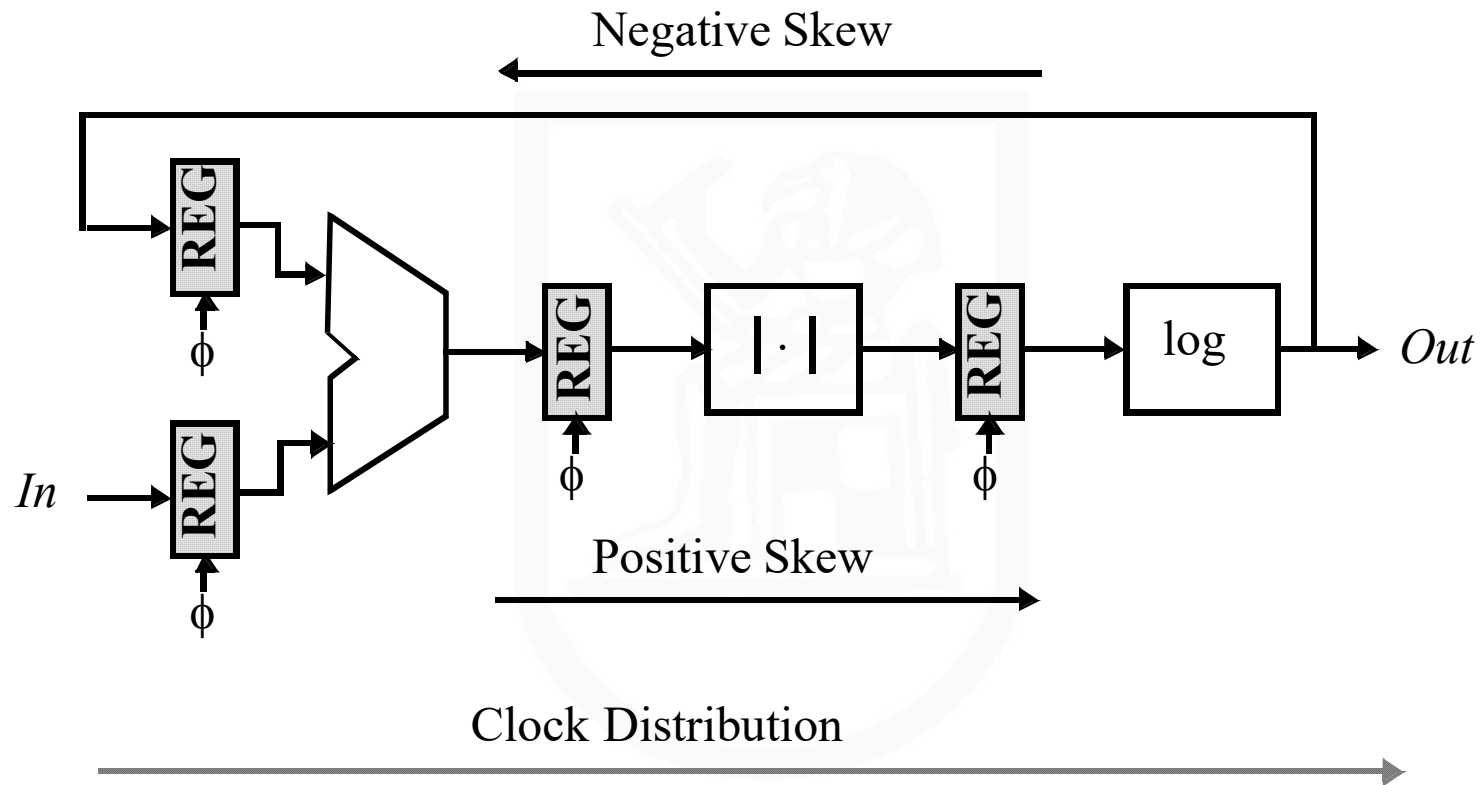


Data and Clock Routing

Flip-Flop – Based Timing

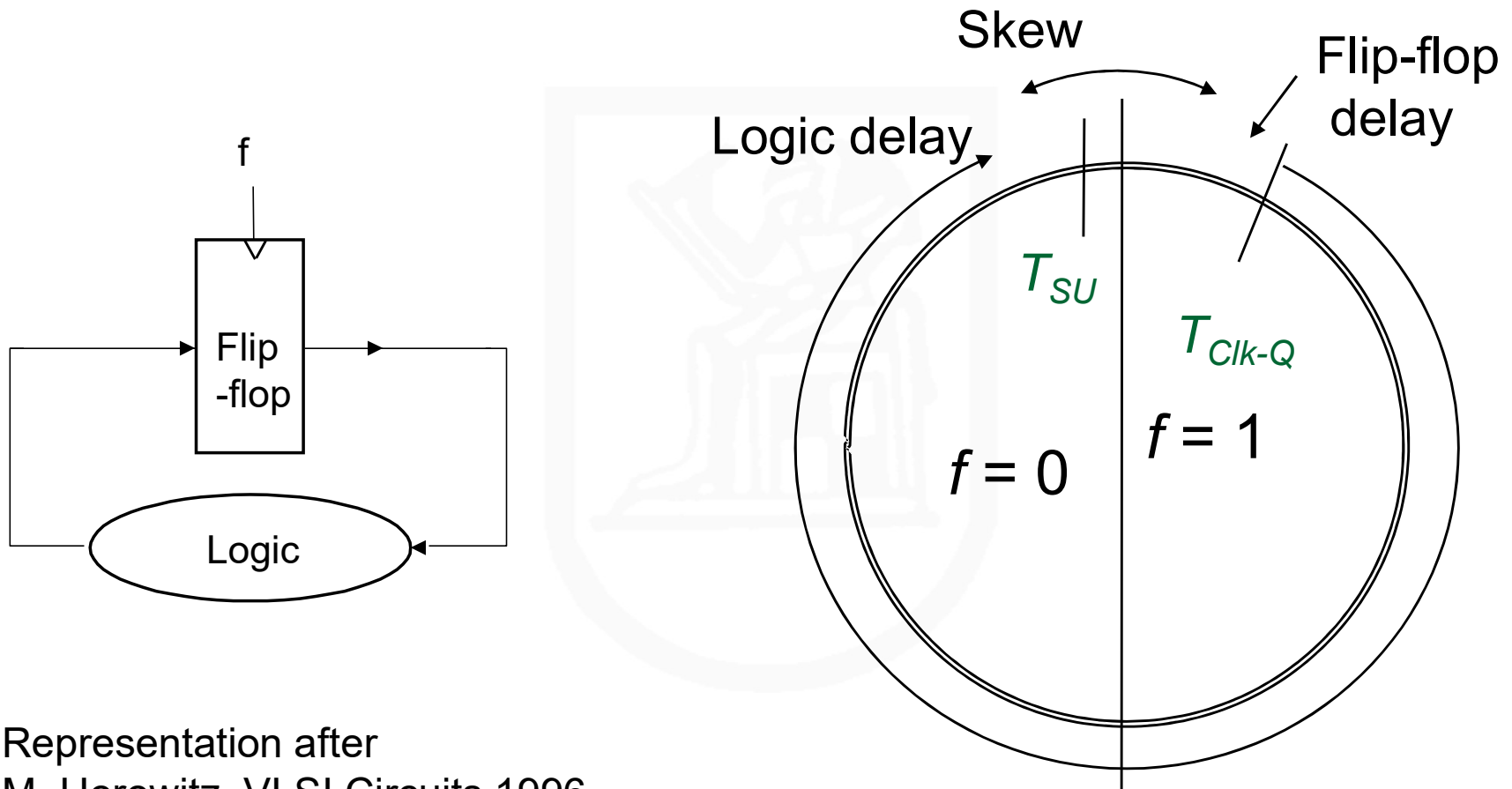

Representation after
M. Horowitz, VLSI Circuits 1996.

Latch Parameters

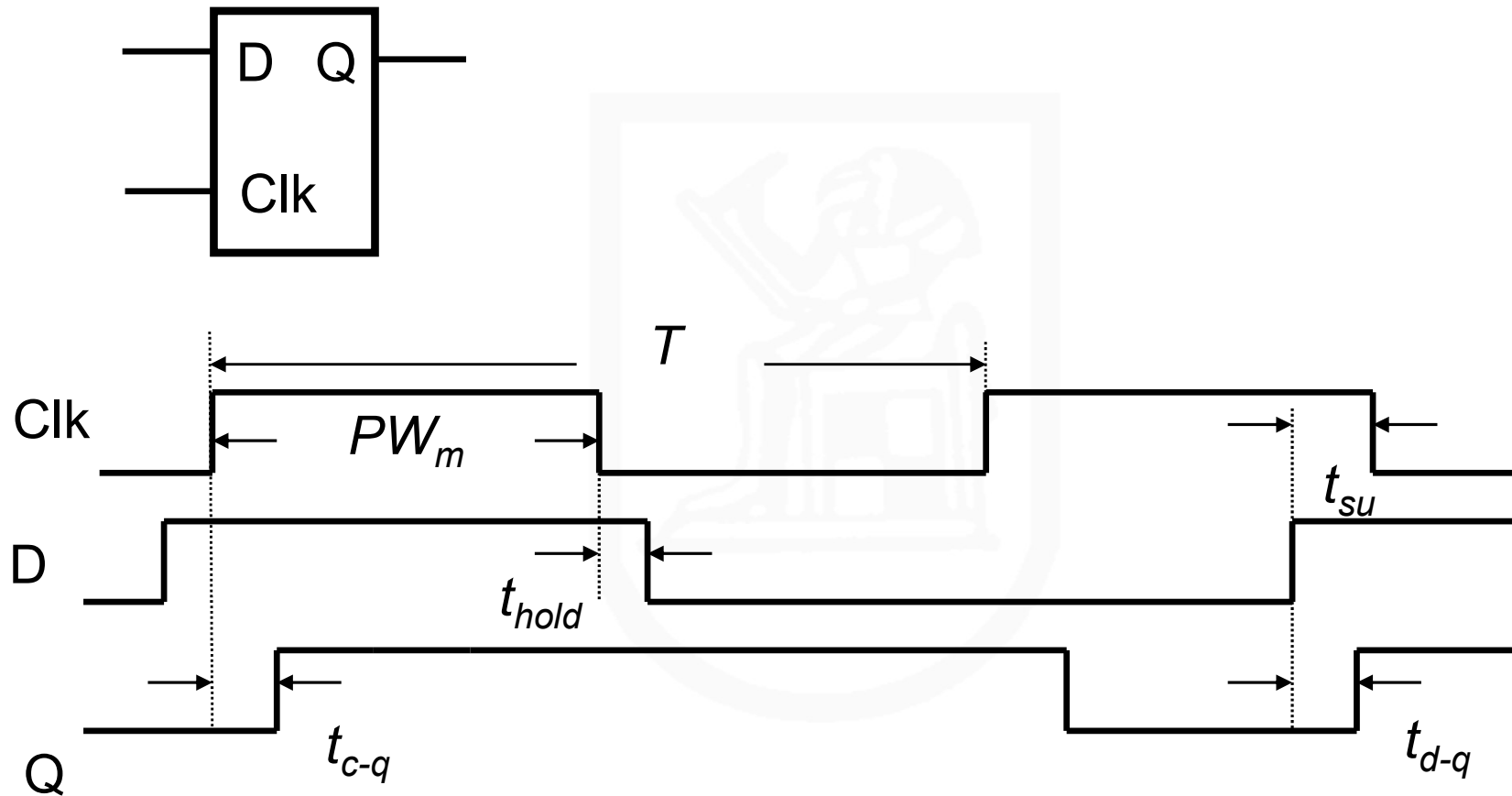


Delays can be different for rising and falling data transitions

Latch-Based Design


L1 latch is transparent
when $f = 0$

L2 latch is transparent
when $f = 1$

 


Clock Distribution

H-tree

 

Clock is distributed in a tree-like fashion

H-Tree

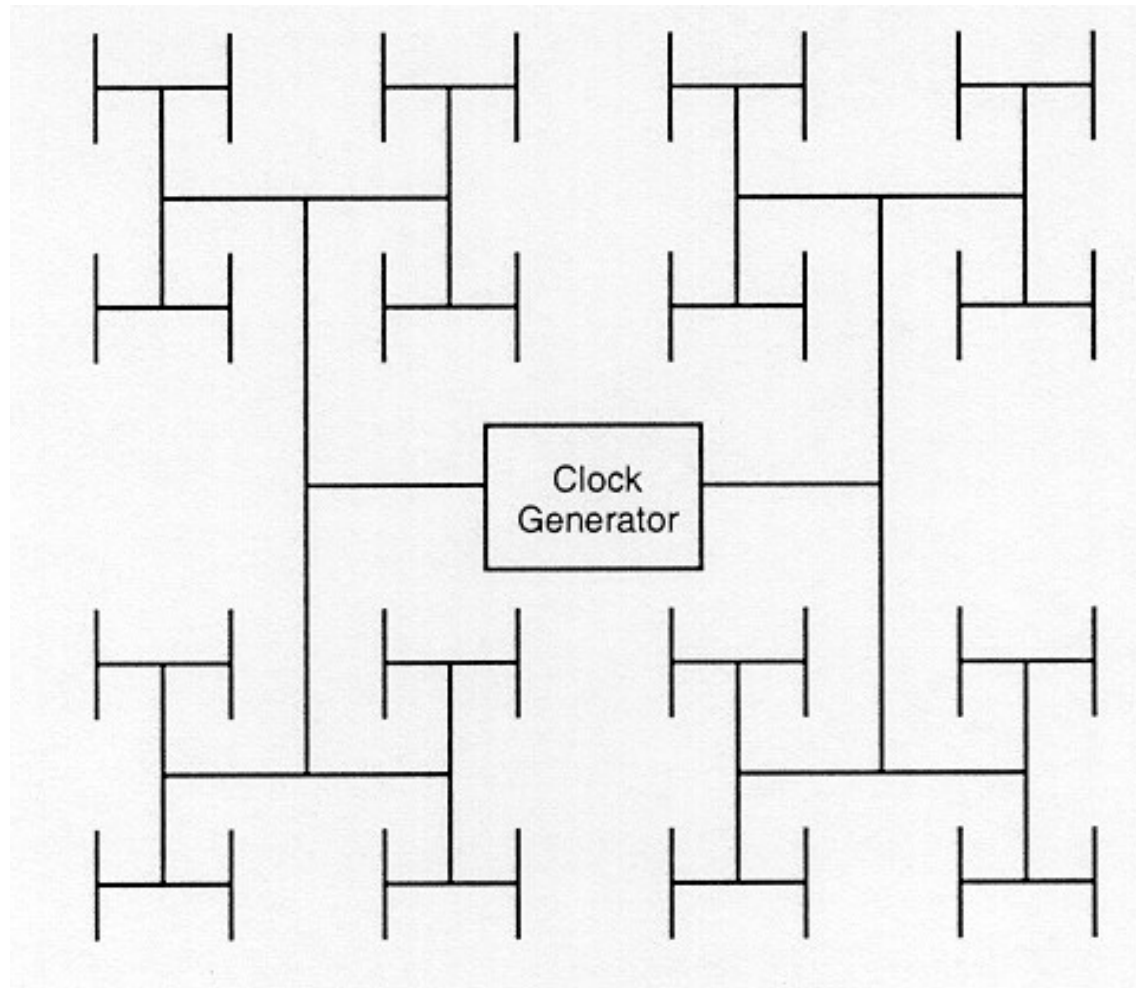


Goal:

Try to equalize clock distribution path lengths to minimize the skew !

H-tree clock distribution network


H-Tree

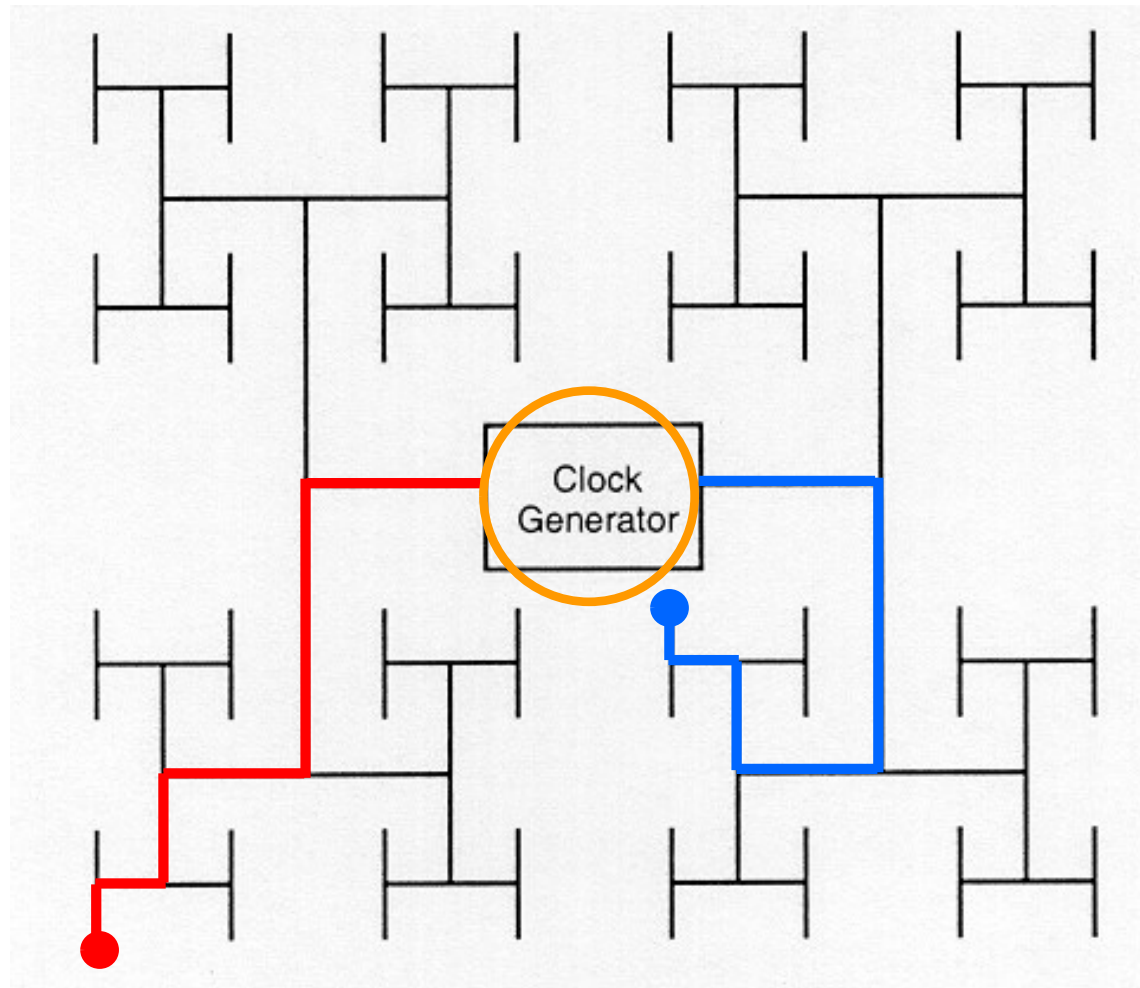

Goal:
Try to equalize
clock distribution
path lengths to
minimize the
skew !


H-tree clock distribution network

H-Tree

 


Typical clock distribution network of a real chip

Clock Driver Network

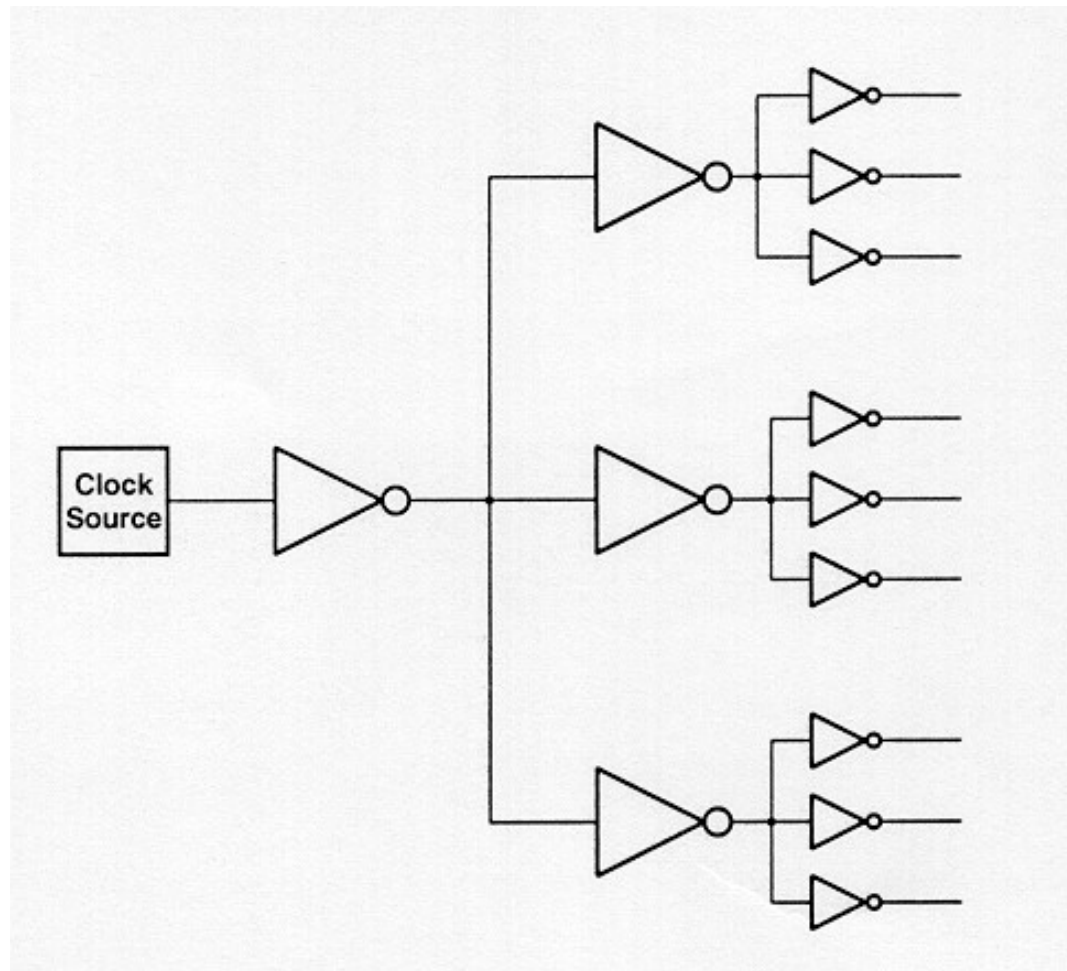


Balanced clock driver network

The Grid System

 

- *No RC-matching*
- *Large power*
- *Mostly in FPGAs*

Balanced Grid

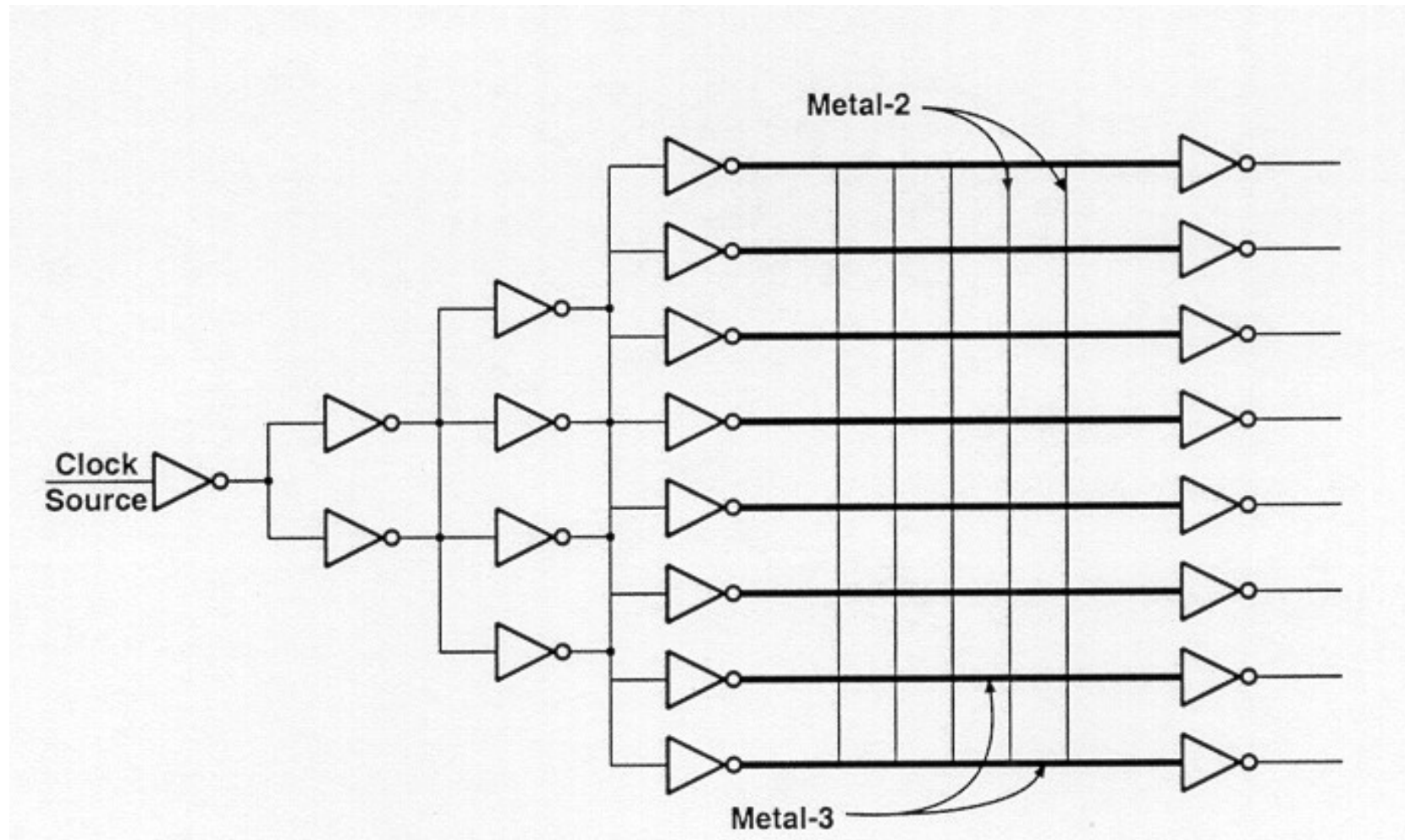


Balanced clock grid (Alpha processor)


Example: DEC Alpha 21164

- Clock Frequency: 300 MHz - 9.3 Million Transistors
 - Total Clock Load: 3.75 nF
- Power in Clock Distribution network : 20W out of 50
- Uses Two Level Clock Distribution:
 - Single 6-stage driver at center of chip
 - Secondary buffers drive left and right side
 - Clock grid in Metal3 and Metal4

21164 Clocking

 


Clock waveform

 


Location of clock driver on die

- **2 phase single wire clock, distributed globally**
- **2 distributed driver channels**
 - Reduced RC delay/skew
 - Improved thermal distribution
 - 3.75nF clock load
- **Local inverters for latching**
- **Conditional clocks in caches to reduce power**
- **More complex race checking**
- **Device variation**

21164 Clocking

 


Clock Skew in Alpha Processor

 


EV6 (Alpha 21264)

Clocking 600 MHz – 0.35um CMOS

 


Global clock waveform

 


- **2 Phase, with multiple conditional buffered clocks**
 - 2.8 nF clock load
 - 40 cm final driver width
- Local clocks can be gated “off” to save power
- Reduced load/skew
- Reduced thermal issues
- Multiple clocks complicate race checking


21264 Clocking

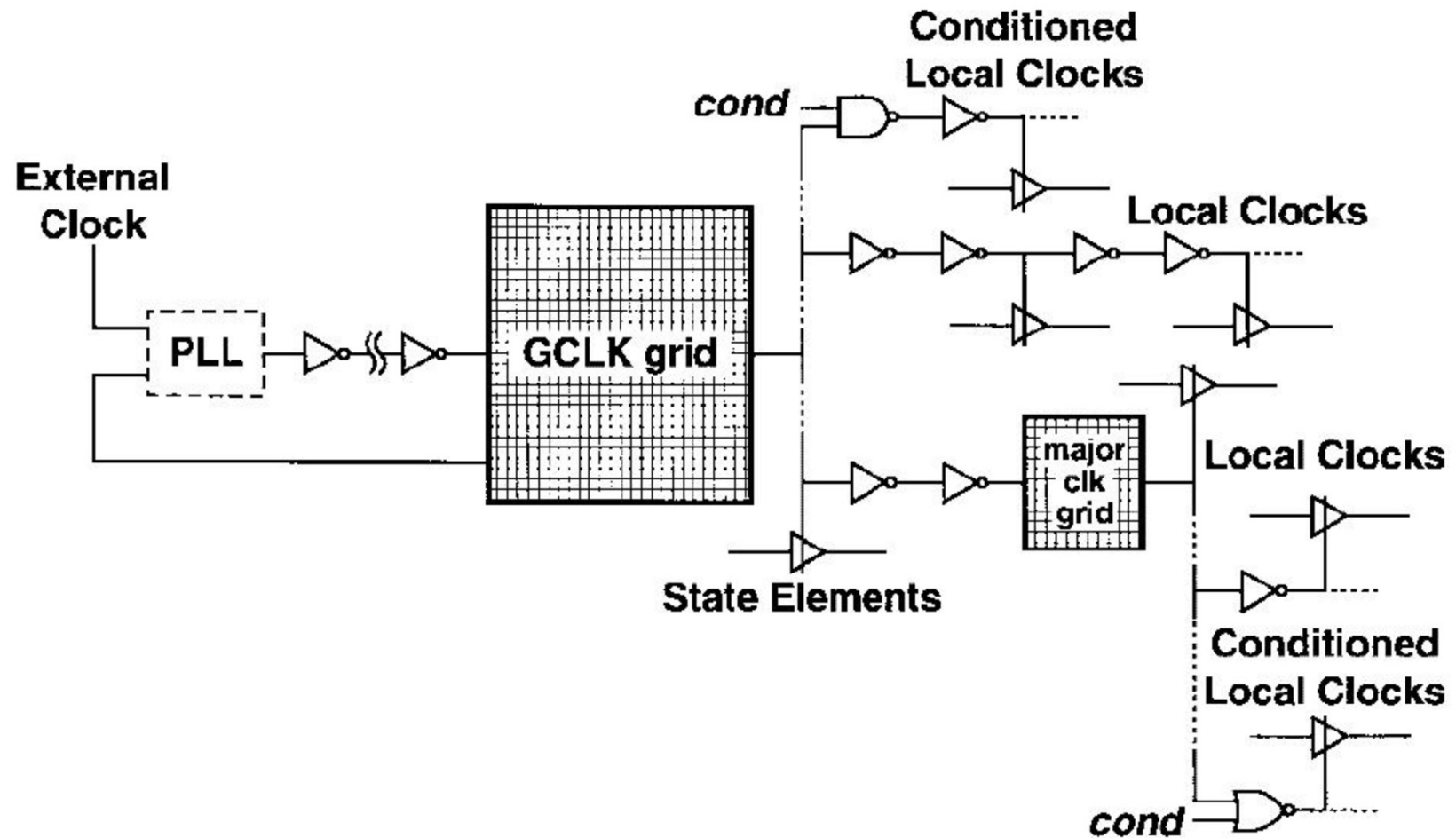

EV6 Clock Results

 


GCLK Skew
(at Vdd/2 Crossings)

 

GCLK Rise Times
(20% to 80% Extrapolated to 0% to 100%)

EV7 Clock Hierarchy

 Active Skew Management and Multiple Clock Domains



- + Widely dispersed drivers
- + DLLs compensate static and low-frequency variation
- + Divides design and verification effort
- DLL design and verification is added work
- + Tailored clocks


Cell Library Example

AμE Advanced Microelectronics
A Division of ITD

ms080cmosxCells
CMOSX 0.8 Micron
Standard Cell Library

D flip-flop

DFF

 

Logic Equation:
 $Q = [D \& CP[rise]] | (Q' \& \neg CP[rise])$
 $QBAR = \neg Q$

Size in microns (W x H):
63.4 x 45.0

Pin Capacitance (fF)

pin	best	typical	worst
CP	14.7	21.6	30.9
D	14.4	15.5	18.4
Q	5.01	10.6	11.7
QBAR	11.4	12.7	22.3

Truth Table

CP	Q	QBAR
01	1	0
10	0	1

Delay Information

Path	Timing	best, 5.5V, -55°C, load 0.25pF to 0.584ns, tFO.68ns			typical, 5V, 25°C, load 0.25pF to 1.15ns, tFO.68ns			worst, 4.5V, 125°C, load 0.25pF to 2.76ns, tFO.27ns		
		0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load
cp->qbar	01->10	PD			PD			PD		
		8.249	0.313	0.647	0.553	0.579	1.14	1.52	1.74	2.61
cp->q	01->01	PD			PD			PD		
		0.0997	0.256	0.881	0.144	0.354	1.29	0.281	0.668	2.32
cp->qbar	01->01	PD			PD			PD		
		0.211	0.256	0.545	0.459	0.624	1.25	1.24	1.74	3.34
cp->q	01->10	PD			PD			PD		
		0.0874	0.228	0.847	0.148	0.377	1.89	0.155	1.32	4.85
cp->qbar	01->10	PD			PD			PD		
		0.222	0.251	0.440	0.506	0.633	1.03	1.44	1.72	2.80
cp->q	01->10	PD			PD			PD		
		0.0659	0.154	0.565	0.140	0.407	1.26	0.364	0.900	3.24
cp->q	01->10	PD			PD			PD		
		0.209	0.316	0.797	0.429	0.631	1.37	1.16	1.54	2.91
cp->q	01->10	PD			PD			PD		
		0.107	0.310	1.39	0.210	0.537	1.92	0.441	1.06	3.55

Special Timing Information


	best, 5.5V, -55°C	typical, 5V, 25°C	worst, 4.5V, 125°C
Setup time on D	0.3	0.6	1.4
Hold time on D	0.1	0.05	0.01
Minimum pulse width low on CP	0.2	0.3	0.9
Minimum pulse width high on CP	0.08	0.2	0.6
Minimum period on CP	0.4	0.8	2.2
Maximum fall time on CP	4	35	2.8e+02

AμE Advanced Microelectronics
A Division of ITD

ms080cmosxCells
CMOSX 0.8 Micron
Standard Cell Library

2 Input NOR 1x drive

NOR2

 

Size in microns (W x H):
12.2 x 45.0


Pin Capacitance (fF)

pin	best	typical	worst
A0	15.5	24.2	37.1
A1	15.9	23.3	34.6
Y	5.54	10.1	15.6

Logic Equation:
 $Y = \neg(A0 | A1)$

Truth Table

A0	A1	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


Delay Information


Path	Timing	best, 5.5V, -55°C, load 0.25pF to 0.584ns, tFO.68ns			typical, 5V, 25°C, load 0.25pF to 1.15ns, tFO.68ns			worst, 4.5V, 125°C, load 0.25pF to 2.76ns, tFO.27ns		
		0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load
a1->y	01->01	PD			PD			PD		
		0.108	0.281	0.827	0.273	0.629	1.84	0.549	1.68	5.07
a1->y	01->10	PD			PD			PD		
		0.0757	0.243	0.81	0.108	0.221	0.81	0.313	0.527	0.81
a0->y	01->01	PD			PD			PD		
		0.108	0.281	0.827	0.273	0.629	1.84	0.549	1.68	5.07
a0->y	01->10	PD			PD			PD		
		0.0757	0.243	0.81	0.108	0.221	0.81	0.313	0.527	0.81
a0->y	01->10	PD			PD			PD		
		0.0757	0.243	0.81	0.108	0.221	0.81	0.313	0.527	0.81

C_{load} on Flip-Flop

 - C_{load} = output capacitance of flip-flop + input capacitance of NOR gate



Pin Capacitance (fF)			
pin	best	typical	worst
CP	14.7	21.6	30.9
D	10.4	13.5	18.4
Q	5.04	10.6	11.7
QBAR	11.4	12.7	22.3

 

Pin Capacitance (fF)			
pin	best	typical	worst
A0	16.5	24.2	37.1
A1	15.9	23.3	34.6
Y	5.54	10.1	13.6

Timing Tables


- Predict delay
 - Note delay different for rising and falling edges

Delay Information

Path	Timing		best, 5.5V, -55C, load:0.35pF tr:0.584ns, tf:0.638ns			typical, 5V, 25C, load:0.35pF tr:1.15ns, tf:1.12ns			worst, 4.5V, 125C, load:0.35pF tr:2.78ns, tf:2.27ns		
			0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load	0.25 * load	1 * load	4 * load
cp->qbar	01->10	PD	0.249	0.315	0.647	0.553	0.679	1.18	1.52	1.76	2.61
			0.213 + 0.308 * CL			0.517 + 0.478 * CL			1.46 + 0.831 * CL		
		TR	0.0697	0.206	0.811	0.144	0.354	1.29	0.281	0.668	2.32
cp->q	01->01	PD	0.211	0.266	0.545	0.459	0.624	1.25	1.24	1.70	3.34
			0.180 + 0.258 * CL			0.416 + 0.609 * CL			1.12 + 1.59 * CL		
		TR	0.0874	0.229	0.847	0.198	0.517	1.89	0.456	1.33	4.86
cp->qbar	01->01	PD	0.222	0.258	0.440	0.506	0.613	1.03	1.44	1.72	2.80
			0.202 + 0.169 * CL			0.475 + 0.403 * CL			1.35 + 1.03 * CL		
		TR	0.0669	0.154	0.565	0.140	0.347	1.26	0.364	0.901	3.24
cp->q	01->10	PD	0.209	0.316	0.797	0.429	0.631	1.37	1.16	1.59	2.91
			0.162 + 0.451 * CL			0.378 + 0.714 * CL			1.09 + 1.32 * CL		
		TR	0.107	0.310	1.19	0.210	0.537	1.92	0.441	1.06	3.55

Data Sheet Example

 - Using timing approximations in the datasheet, what is the maximum clock frequency for this circuit (ignore wire load, Tskew)?



Tclock-Q:

cp->q	01->01	PD	1.24	1.70	3.34
		TR	1.12 + 1.59 * CL		
			0.456	1.33	4.86
cp->q	01->10	PD	1.16	1.59	2.91
		TR	1.09 + 1.32 * CL		
			0.441	1.06	3.55

CL:

Pin Capacitance (fF)

pin	best	typical	worst
A0	16.5	24.2	37.1
A1	15.9	23.3	34.6
Y	5.54	10.1	13.6

DFF

Pin Capacitance (fF)

pin	best	typical	worst
CP	14.7	21.6	30.9
D	10.4	13.5	18.4
Q	5.04	10.6	11.7
QBAR	11.4	12.7	22.3

Q -> A0:

$$C_{L_max} = 0.0371 + 0.0117 \text{ pF} = 0.0488 \text{ pF}$$

$$T_{cp-Q_max} = \max(1.12 + 1.59 * CL, 1.09 + 1.32 * CL)$$

$$= \max(1.12 + 1.59 * 0.0488, 1.09 + 1.32 * 0.0488)$$

$$= \max(1.2, 1.15) = 1.2 \text{ ns}$$

Q->A1:

$$T_{cp-Q_max} = 1.2 \text{ ns}$$

Data Sheet Example

*T*logic:

C:				worst, 4.5V, 125C, load:0.35pF tr:2.78ns, tf:2.27ns		
a1->y	10->01	PD	0	0.25 * load	1 * load	4 * load
			1	0.749	1.68	5.07
		TR	0	0.503 + 3.27 * CL		
a1->y	01->10	PD	0	1.15	2.91	10.3
			1	0.502	1.25	3.40
		TR	0	0.420 + 2.17 * CL		
a0->y	10->01	PD	0	0.920	1.87	5.61
			1	0.636	1.50	4.85
		TR	0	0.371 + 3.21 * CL		
a0->y	01->10	PD	0	1.10	2.84	10.3
			1	0.609	1.31	3.43
		TR	0	0.505 + 2.12 * CL		
		TR	0	1.05	1.97	5.68

CL:

Pin Capacitance (fF) NOR2

pin	best	typical	worst
A0	16.5	24.2	37.1
A1	15.9	23.3	34.6
Y	5.54	10.1	13.6

DFF

Pin Capacitance (fF)

pin	best	typical	worst
CP	14.7	21.6	30.9
D	10.4	13.5	18.4
Q	5.04	10.6	11.7
QBAR	11.4	12.7	22.3

NOR2

$$CL = 0.0136 + 0.0184 = 0.032 \text{ pF}$$

$$\text{From A0 : } T_{\text{logic}} = \max (0.503 + 3.27 \cdot 0.032, 0.420 + 2.17 \cdot 0.032) \\ = 0.61 \text{ ns}$$


$$\text{From A1 : } T_{\text{logic}} = \max (0.505 + 2.12 \cdot 0.032, 0.371 + 3.21 \cdot 0.032) \\ = 0.57 \text{ ns}$$

Data Sheet Example

T_{su}

Special Timing Information

	best, 5.5V, -55C	typical, 5V, 25C	worst, 4.5V, 125C
Setup-time on D	0.3	0.6	1.4
Hold-time on D	0.1	0.05	0.01
Minimum-pulse-width-low on CP	0.2	0.3	0.9
Minimum-pulse-width-high on CP	0.08	0.2	0.6
Minimum-period on CP	0.4	0.8	2.2
Maximum-fall-time on CP	4	39	3.8e+02



$$\begin{aligned}T_{\text{clock}} &> T_{\text{cp-Q_max}} + T_{\text{logic_max}} + T_{\text{su_max}} \\&= 1.2 + 0.61 + 1.4 \\&= 3.21 \text{ ns}\end{aligned}$$

$$F_{\text{clock}} < 311 \text{ MHz}$$


Delay Metric

- **Usual Metric for delay:**
 - Delay of an inverter with a fan-out of 4: FO4
- **Estimating FO4:**
 - Typical $\sim 360 \times L_{\text{eff}}$ (ps)
 - Worst Case $\sim 600 \times L_{\text{eff}}$ (ps)
 - L_{eff} = Effective gate length in $\mu\text{m} \sim 0.7 \times L_{\text{drawn}}$
 - E.g., in a $0.18\mu\text{m}$ process, $L_{\text{eff}} = 0.126\mu\text{m}$ and $\text{FO4} \leq 75\text{ps}$
- **Examples:**

Inverter	= FO4	2-input NAND gate	= 2·FO4
1-bit adder	= 10·FO4	2-input Multiplexer	= 4·FO4
Flip-flop $t_{\text{c-q}}$	= 4·FO4	Flip-flop t_{su} & t_{h}	= 2·FO4
Clock skew	= 4·FO4	Clock jitter	= 2·FO4

Examples of Improving Timing Performance

 
- **Example 1 : Benefits of Pipelining and Parallelism**
- **Example:**



**If $t_{\text{comparator}} = 20 \cdot F_{O4}$, what is the clock period?
(Use values on previous page)**

Pipelining

- Replace with:

 


$$\begin{aligned} T_{cp} &= t_{ck-Q} + t_{logic} + t_{su} + t_{skew} + t_{jitter} \\ &= 4 + 20 + 2 + 4 + 2 = 32 \text{ FO4} \end{aligned}$$

- What is the delay improvement?
- What is the drawback?

Logic Level Parallelism

- Replace with:

 


- **Clock Period = $52 \cdot \text{FO-4}$**
- **No increase in area**

Retiming

- Impact of critical paths can often be reduced by retiming or rebalancing a design.


- Example:**

- Before:**

 

$$T_{cp} = 4 + 20 + 5 + 2 + 4 + 2 = 37 \text{ FO4}$$

- After:**

 

$$T_{cp} = 4 + 20 + 2 + 4 + 2 = 32 \text{ FO4}$$

Note: Clock level logic sequence has been changed

Timing Mantra

- One clock, one edge; Flip-flops only
 - For your design (at least for each module), use one clock source and only one edge of that clock.
- Only use edge-triggered flip-flops; why?
- Moving data between different clock domains requires careful timing design and synthesis “scripting”.
- If you need multiple clocks in your design:
 - Make them related by a powers of 2, e.g., 50, 100 and 200 MHz
 - Consider one clock per module
 - Consider **resynchronizing** using flip-flops between clock domains

Caveat

- Tools and designers are getting better at using latches and multi-phase clocks. However, this requires experience to get correct.