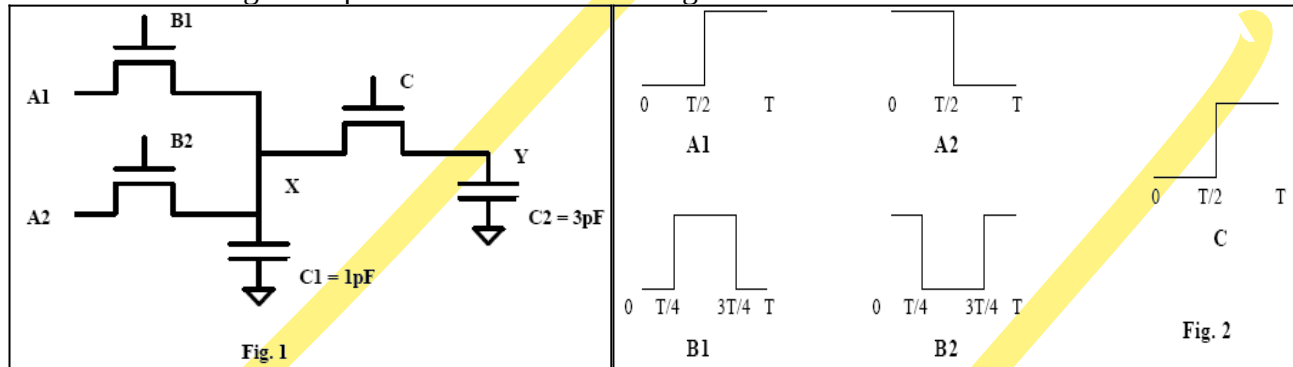




Problem #1



Consider the circuit of Fig. 1. The signal waveforms of each signal within one period are shown in Fig. 2. You may assume that these signals are repeated with a frequency of 1 MHz (or $T = 1\mu s$). Using the following device parameters: $V_T = 0.5 V$, $\gamma = 0$, $R_{on} = 10 K\Omega$, $R_{off} = \infty$.

- Draw the waveform of the signals on the nodes X and Y over one period T, assuming that all input signals are switching between 0 and 2.0 V. You may ignore the parasitic capacitance of the transistors.
- What is the logical expression of the circuit in fig. 1?



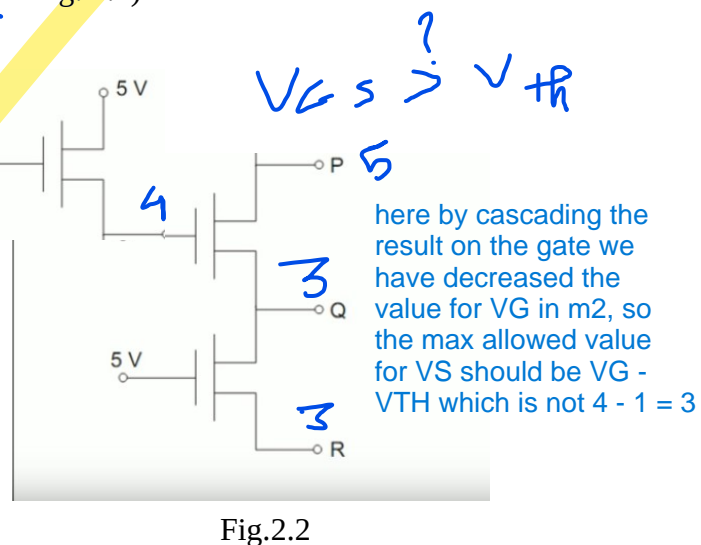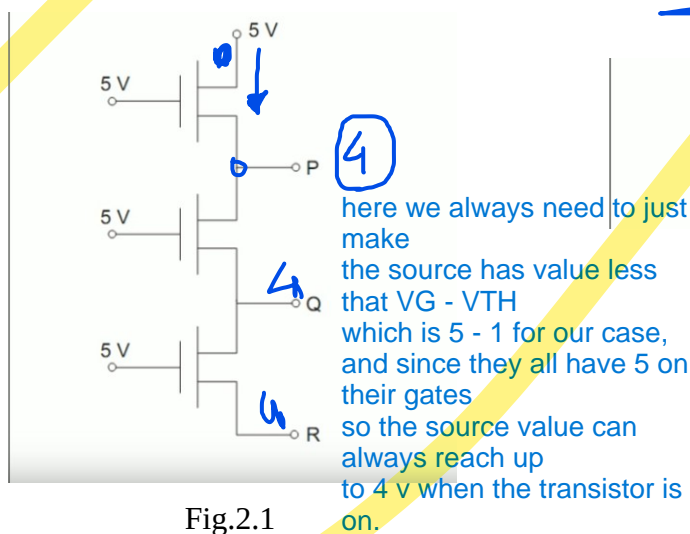Problem #2

For the given figures: Find the voltage at points P, Q, R if the threshold voltage = 1V (assume that we already took the body effect into account) (assume $P=5V$ in fig. 2.2)



this happens because we need to satisfy this equation $V_{GS} \geq V_{TH}$
so the maximum allowable value for v_s is all values that should be less than $V_G - V_{TH} > V_S$.

Problem #3

Implement the function $S = ABC + !A!B!C + !A!BC + !AB!C$ using pass logic

