



Cairo University

CAIRO UNIVERSITY

Cairo University
Faculty of Engineering
Computer Engineering Department

VLSI Sheet 2


Sandra Wahid

Problem 1:

- $Z = (AB+BC) \cdot D$
- First step get Z'
- $Z' = (AB+BC)' + D'$
- $Z' = (AB)'(BC)' + D'$
- $Z' = (A' + B')(B' + C') + D'$
- Here how many transistors: **each input 1 transistor** then all ***2** since we have both N and P networks.
- $\rightarrow 5*2=10$ transistors
- Can further optimize:
- $Z' = A'B' + A'C' + B'B' + B'C' + D'$
- $Z' = A'B' + A'C' + B' + B'C' + D'$
- $Z' = B'(A' + 1 + C') + A'C' + D'$
- $Z' = B' + A'C' + D'$
- $\rightarrow 4*2=8$ transistors
- Assume input and inverted input as given (e.g.: A and A' are both given)


Draw Transistors and Get Euler path (if any)

$$Z' = B' + A'C' + D'$$

 


- An uninterrupted diffusion strip is possible only if there exists an Euler path in the logic graph
 - Euler path: a path through all nodes in the graph such that each edge is visited once and only once.
- For a single poly strip for every input signal, the Euler paths in the PUN and PDN must be **consistent** (the same)


Euler Path Graphs

 

Arcs are transistors
Nodes are vertices

 


N-graph

 


P-graph

D'A'C'B' in N but in P no


Euler Path Graphs

 

Arcs are transistors
Nodes are vertices

 

N-graph

 

P-graph

Common Euler path D'B'C'A' in
N and also in P

Layout Drawing Steps

- 1-Insert the substrate (mostly P or N)
- 2-Insert the well
 - of P-MOS: N-well if substrate is P
 - of N-MOS: P-well if substrate is N
- 3-Insert diffusions (N+ or P+)
 - P diffusion is wider than N diffusion to compensate the lower speed of holes than electrons.
- 4-Insert VDD, GND and Output
- 5-Insert the poly's (in same order as in Euler's path)
- 6-Use metal to connect the sources and drains of the gates.
 - Add appropriate contacts
 - Easiest method is to follow the order in Euler path while connecting

Metal

Polysilicon


P-substrate

N-well


P+

N+

Contact or Via

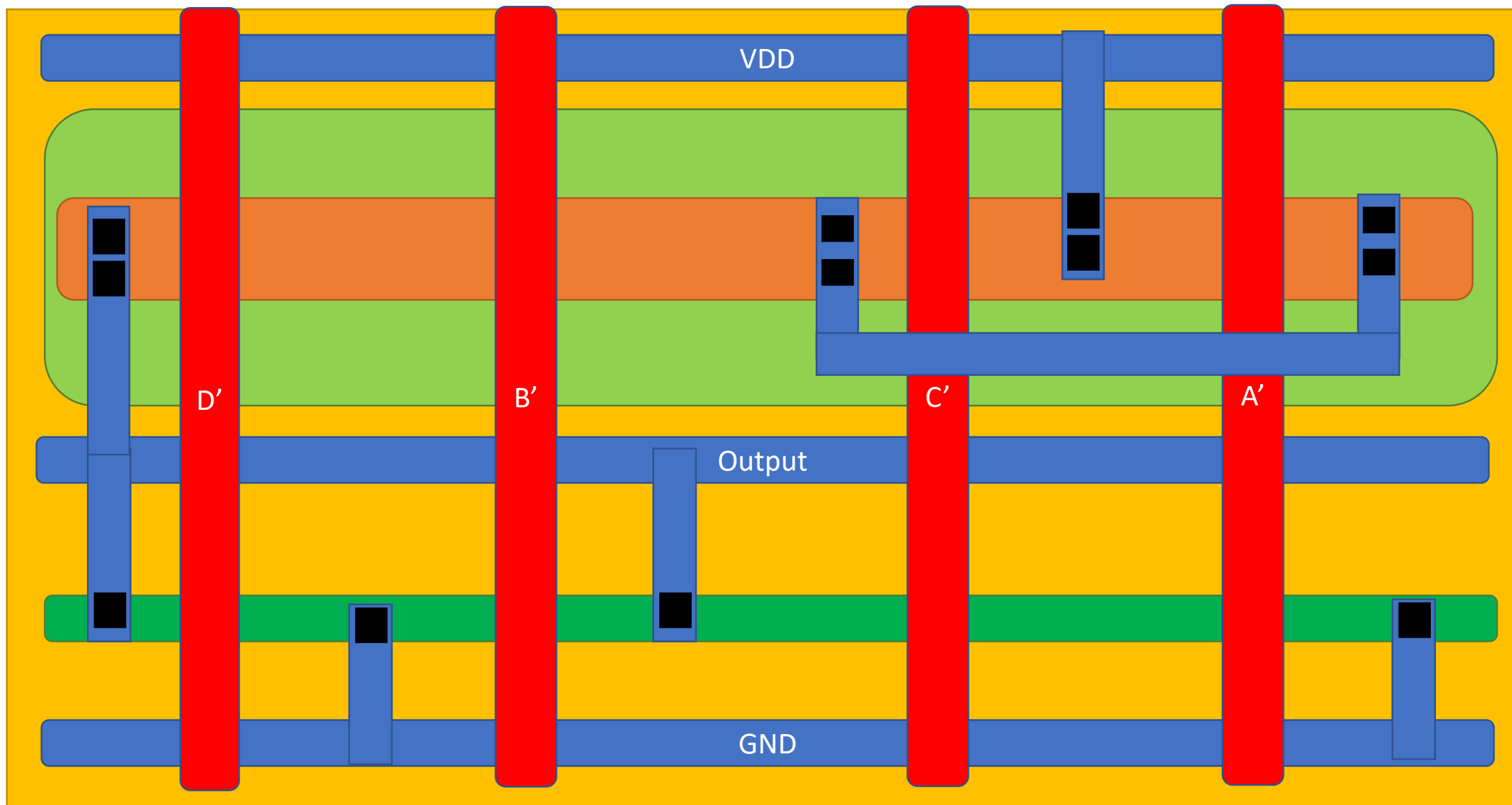

Get Euler path

 

What if the euler path in the pull-up is not similar to euler in the pull down ?

D'A'C'B' in N but in P no

Solution: follow euler path in the pull-down and cut the diffusion in pull-up

Metal

Polysilicon


P-substrate

N-well



P+

N+



Contact or Via

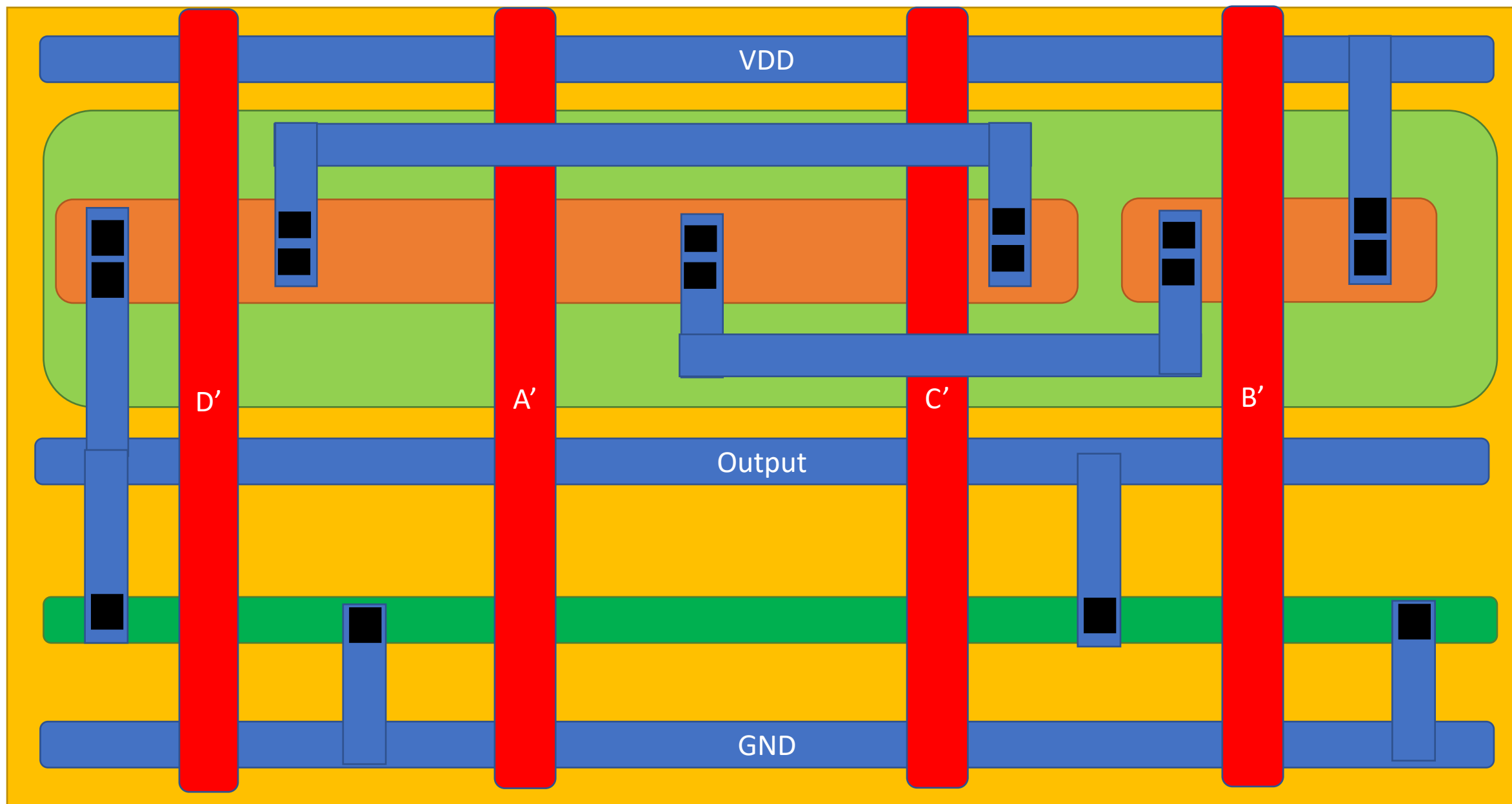

Problem 2:

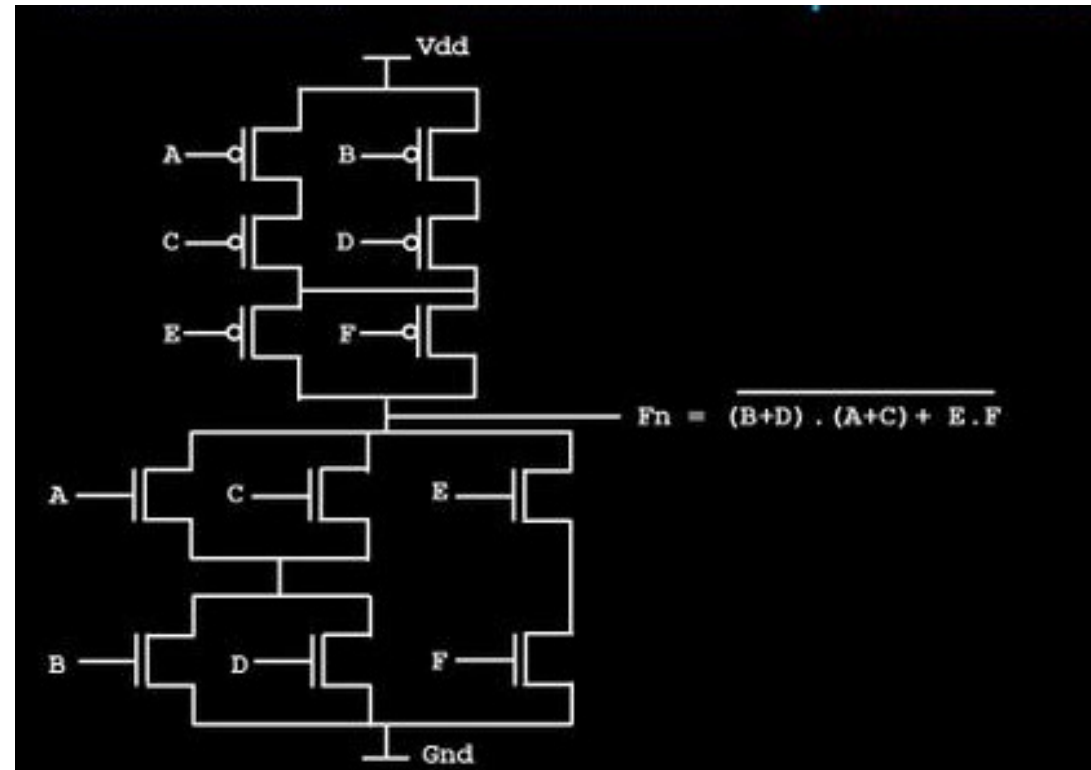 

Problem 3:

  

$$F = \overline{(A + B)(C + D)}$$



THANK YOU