 



Solution 3: Transmission Gates (TGs)

- Most widely used solution




- Full swing *bidirectional* switch controlled by the gate signal C , $A = B$ if $C = 1$**


TG Multiplexer

 

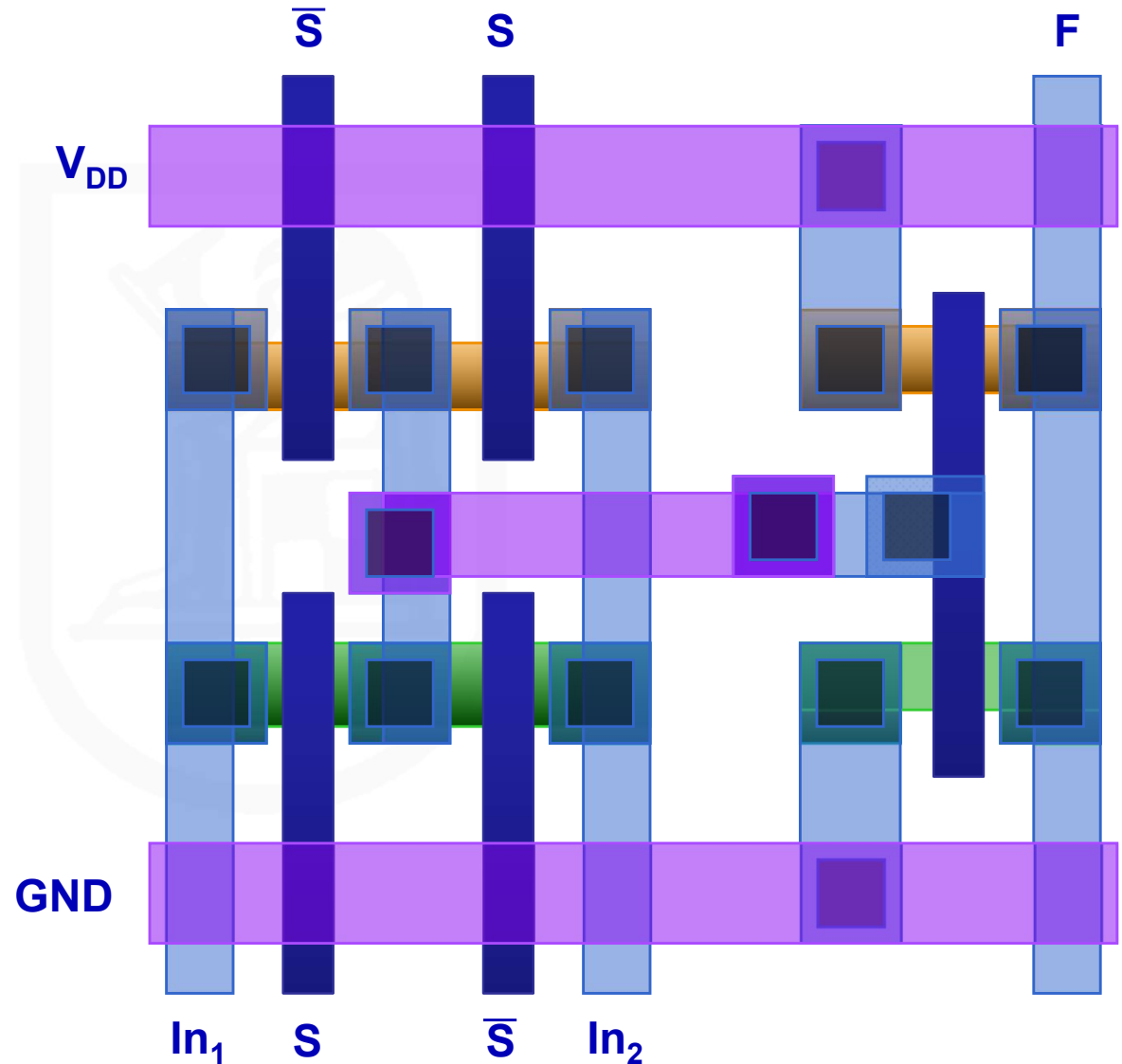
$$F = \overline{(In_1 \bullet S + In_2 \bullet \overline{S})}$$



Transmission Gate XOR

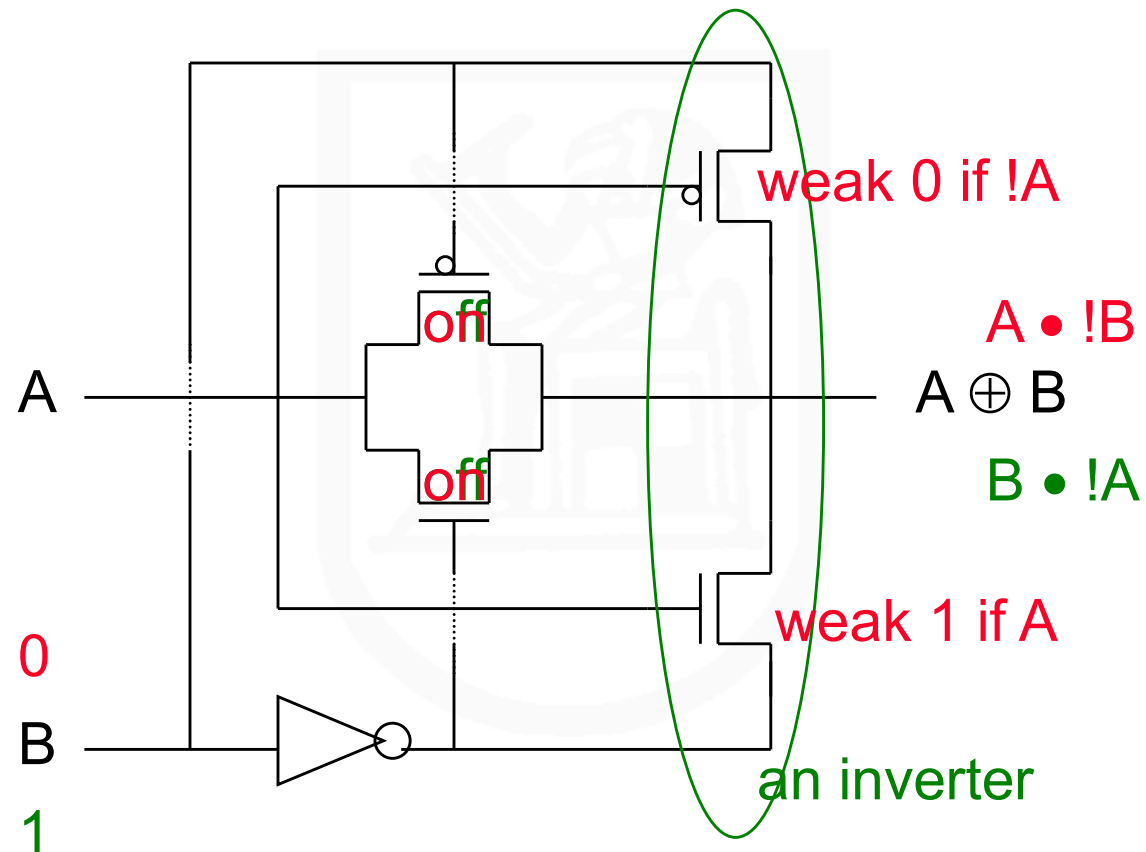


TG Full Adder

 

Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors


Dynamic Gate

 

Two phase operation

Precharge ($Clk = 0$)

Evaluate ($Clk = 1$)

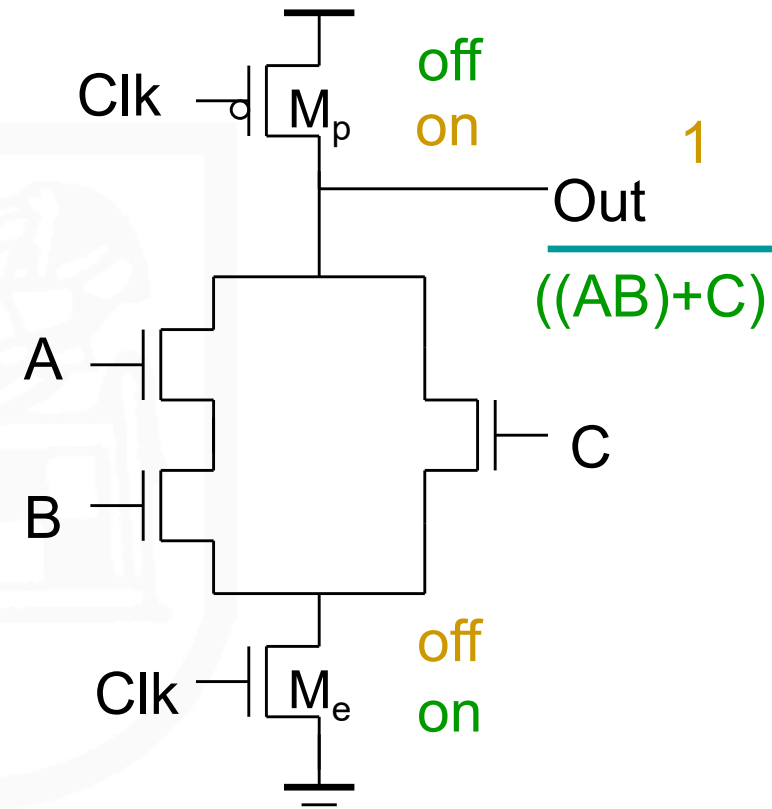

Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L


Properties of Dynamic Gates

- **Logic function is implemented by the PDN only**
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- **Full swing outputs ($V_{OL} = \text{GND}$ and $V_{OH} = V_{DD}$)**
- **Non-ratioed - sizing of the devices does not affect the logic levels**
- **Faster switching speeds**
 - reduced load capacitance due to **lower input** capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L

Properties of Dynamic Gates


- **Overall power dissipation usually higher than static CMOS**
 - no static current path ever exists between V_{DD} and GND (including P_{sc})
 - no glitching
 - higher transition probabilities
 - extra load on Clk
- **PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}**
 - low noise margin (NM_L)
- **Needs a precharge/evaluate clock**

 Issues in Dynamic Design 1: Charge Leakage



Dominant component is subthreshold current


Solution to Charge Leakage

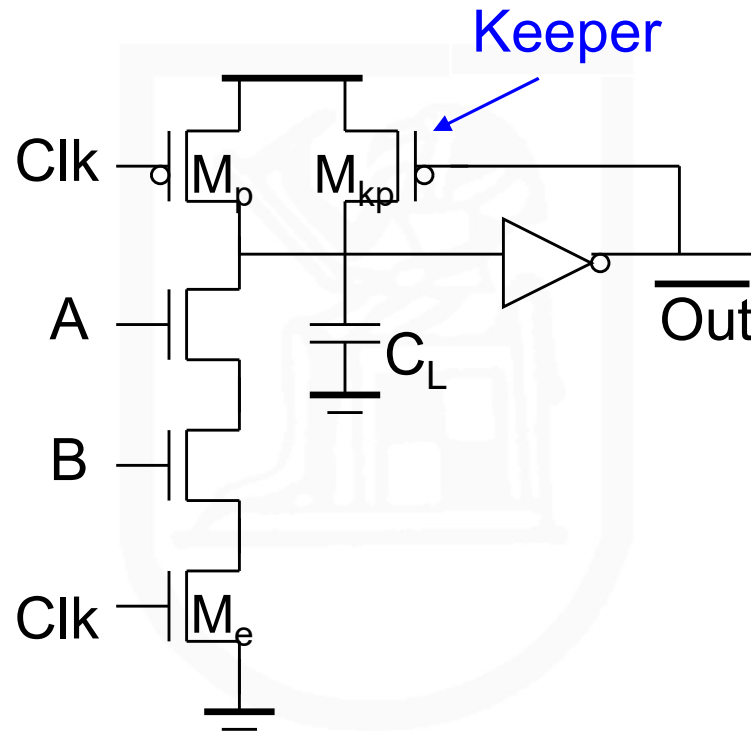

Same approach as level restorer for pass-transistor logic


Issues in Dynamic Design 2:

Charge Sharing

 


Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness

Charge Sharing Example

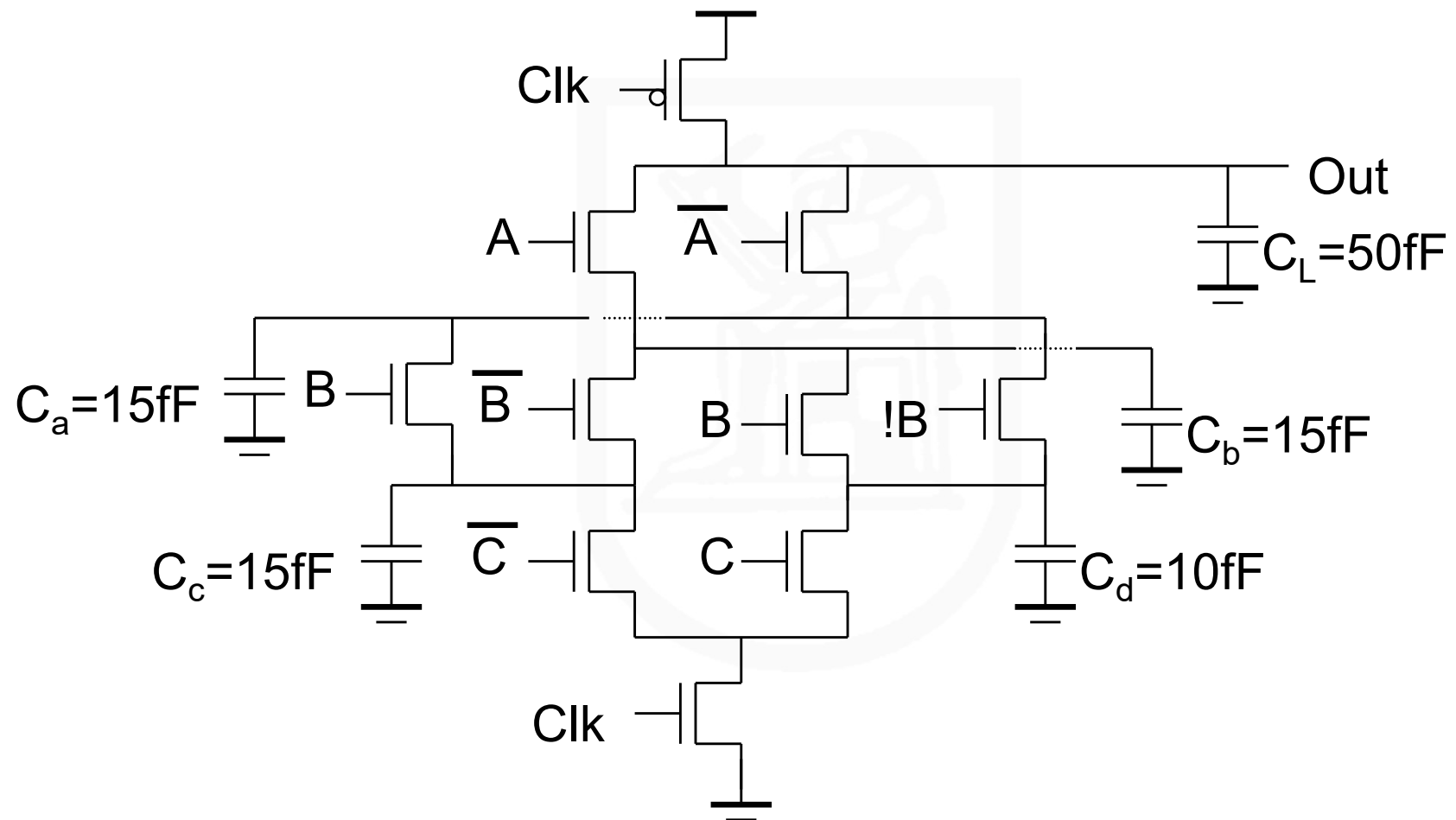

Charge Sharing

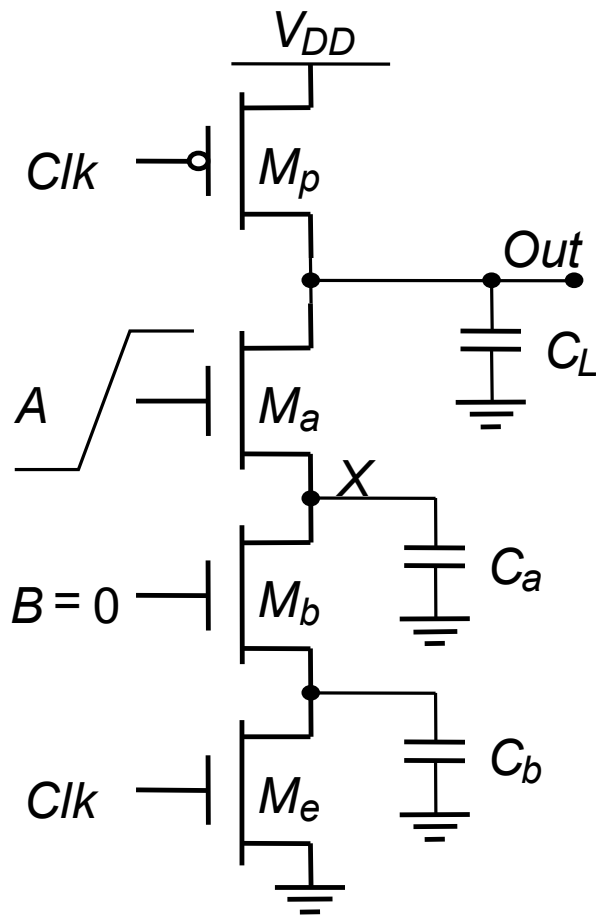

case 1) if $\Delta V_{out} < V_{Tn}$

$$C_L V_{DD} = C_L V_{out}(t) + C_a (V_{DD} - V_{Tn}(V_X))$$


or

$$\Delta V_{out} = V_{out}(t) - V_{DD} = -\frac{C_a}{C_L} (V_{DD} - V_{Tn}(V_X))$$

case 2) if $\Delta V_{out} > V_{Tn}$

$$\Delta V_{out} = -V_{DD} \left(\frac{C_a}{C_a + C_L} \right)$$

Solution to Charge Redistribution

 


Precharge the internal nodes using a clock-driven transistor (at the cost of increased area and power)

Other Effects


- **Capacitive coupling**
- **Substrate coupling**
- **Minority charge injection**
- **Supply noise (ground bounce)**

Cascading Dynamic Gates

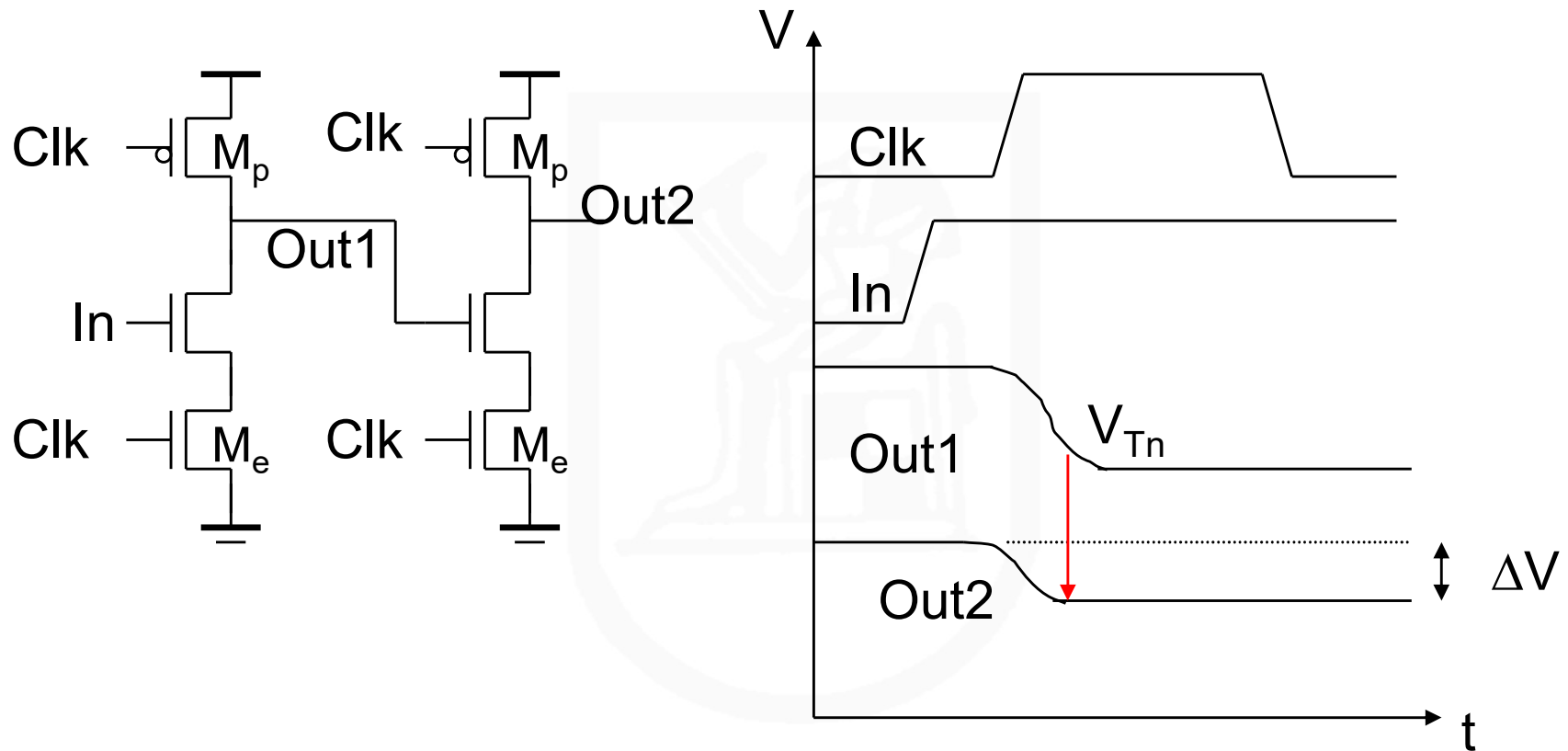


Only 0 \rightarrow 1 transitions allowed at inputs

Domino Logic

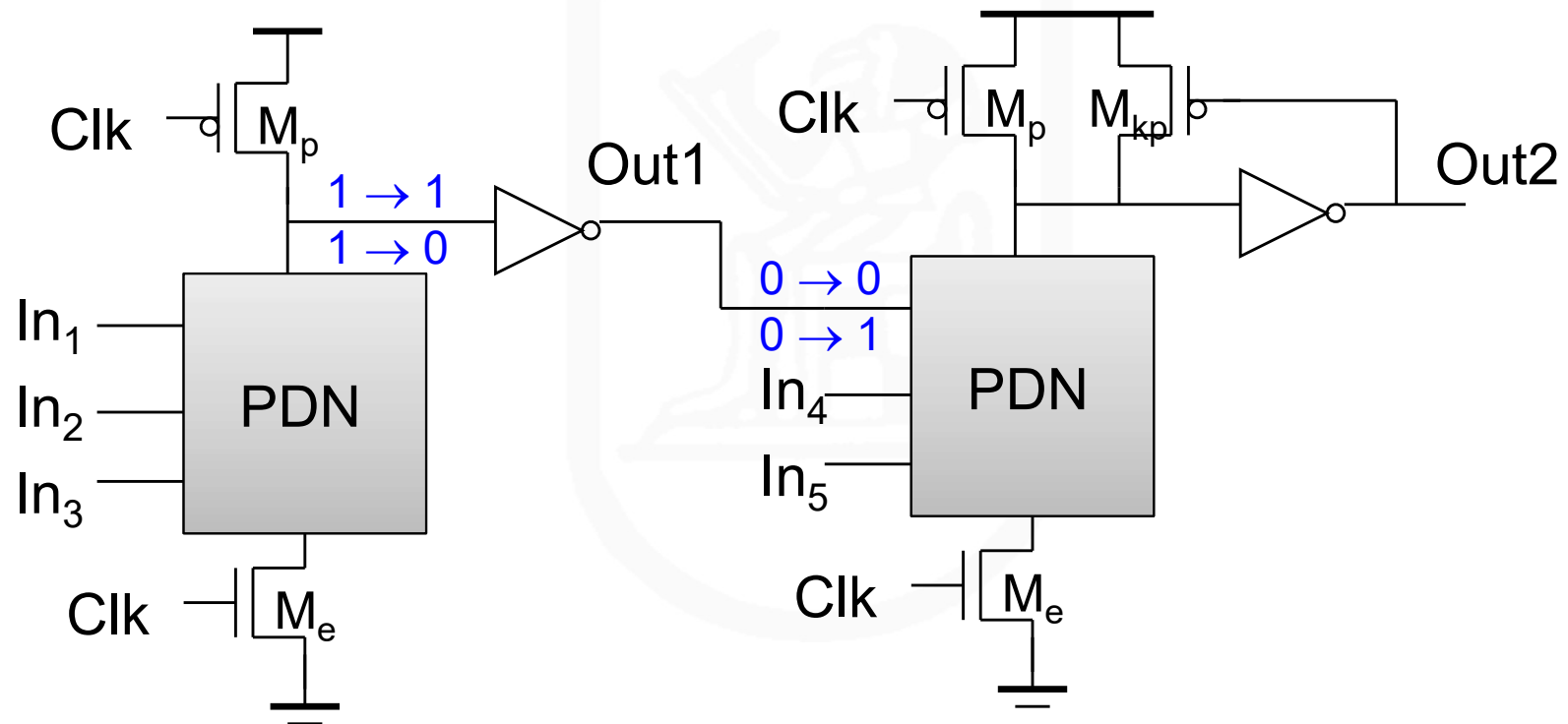

Why Domino?

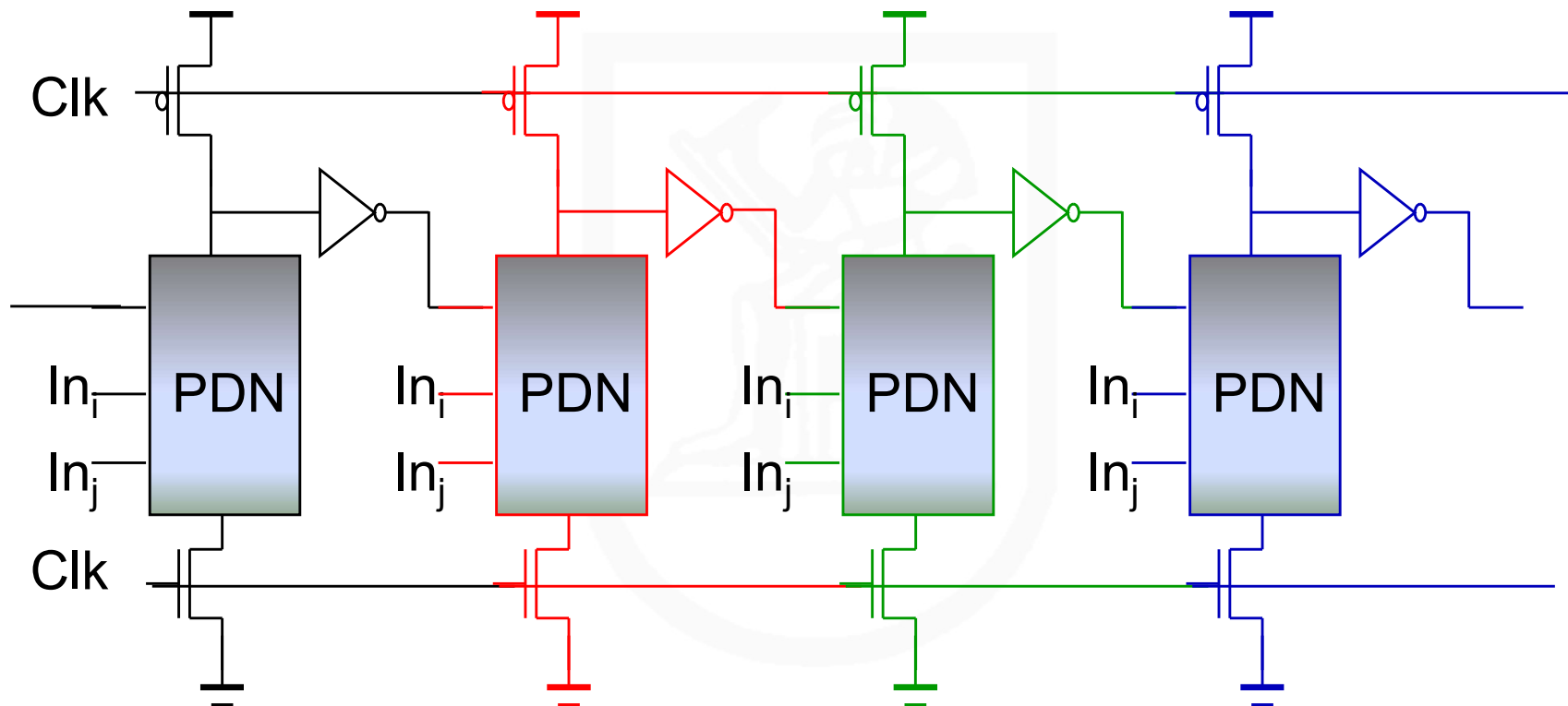


Like falling dominos!


Properties of Domino Logic

- **Only non-inverting logic can be implemented**
- **Very high speed**
 - static inverter can be skewed, only L-H transition
 - Input capacitance reduced – smaller logical effort

Designing with Domino Logic

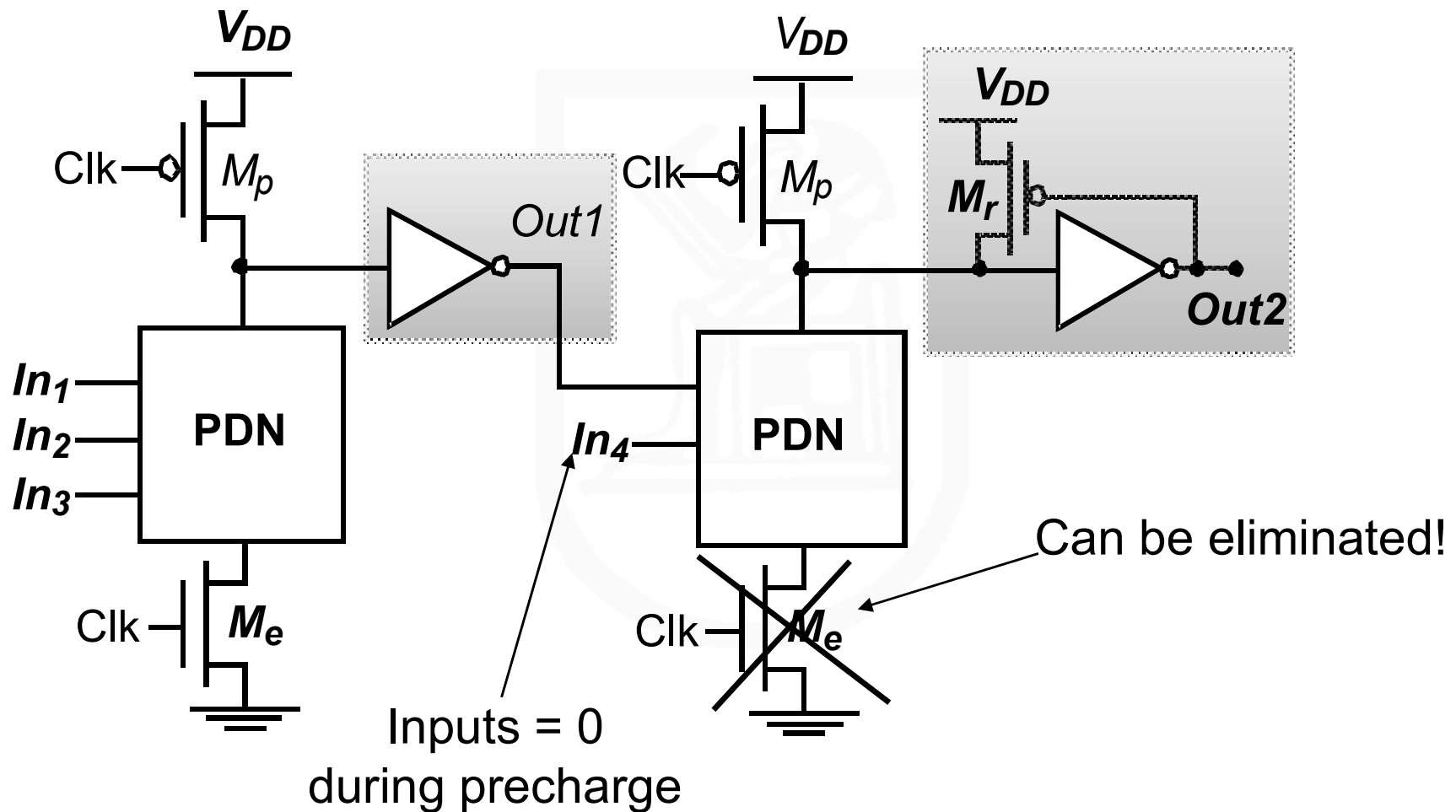

Footless Domino

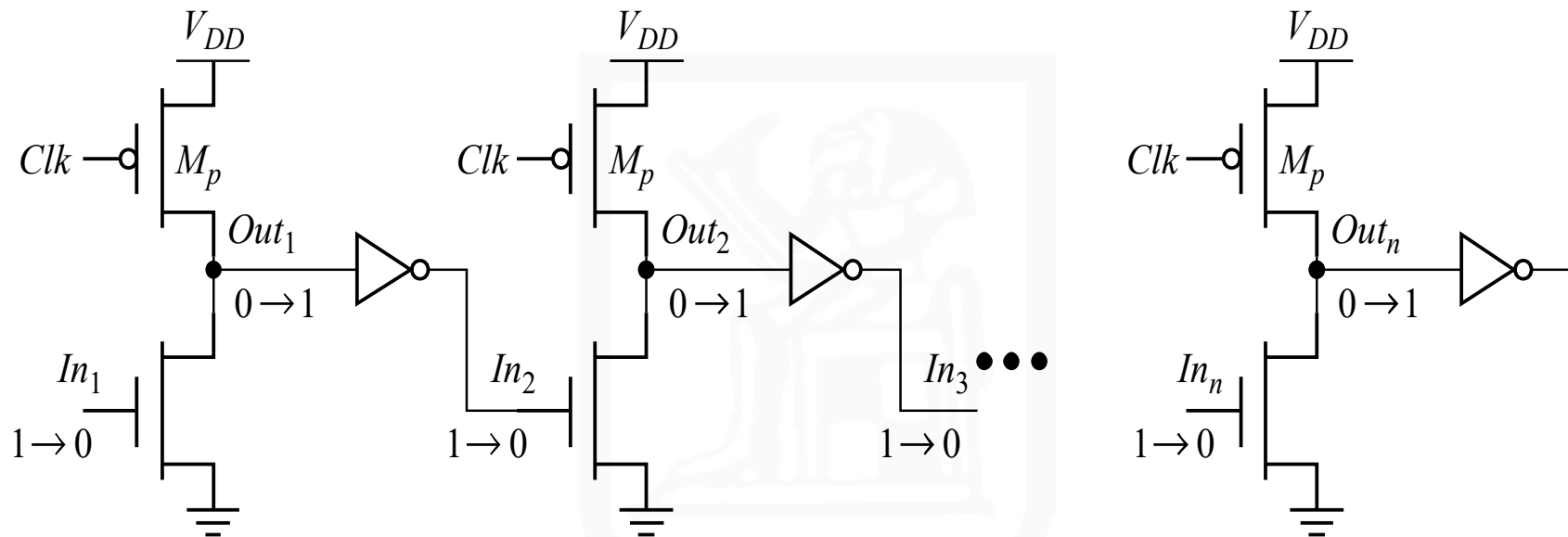

The first gate in the chain needs a foot switch
Precharge is rippling – short-circuit current
A solution is to delay the clock for each stage