



ELC 3252 : Control Engineering Section 2

Presented By : Eng. Youssef Hassan Mohamed

E-mail: youssef_hasan_gamal@hotmail.com

Spring 2022

Electronic Systems

R



$$v(t) = R i(t)$$

$$V(s) = R I(s)$$

$$TF = Z(s) = R$$

L




$$v(t) = L \frac{di}{dt}$$

$$V(s) = L (SI(s) - i(0))$$

$$TF = Z(s) = sL$$

C

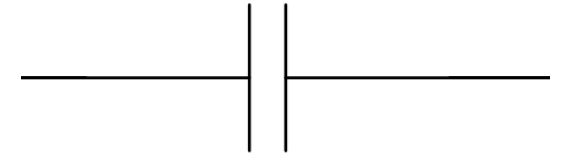

$$i(t) = C \frac{dv}{dt}$$

$$I(s) = C(V(s) - v(0))$$

$$TF = Z(s) = \frac{1}{sC}$$


Electronic Systems

Operational Amplifier

- $v^+ = v^- = 0$


- $\frac{V_{in}}{Z1} = -\frac{V_{out}}{Z2}$

- $TF = \frac{V_{out}}{V_{in}} = -\frac{Z2}{Z1}$

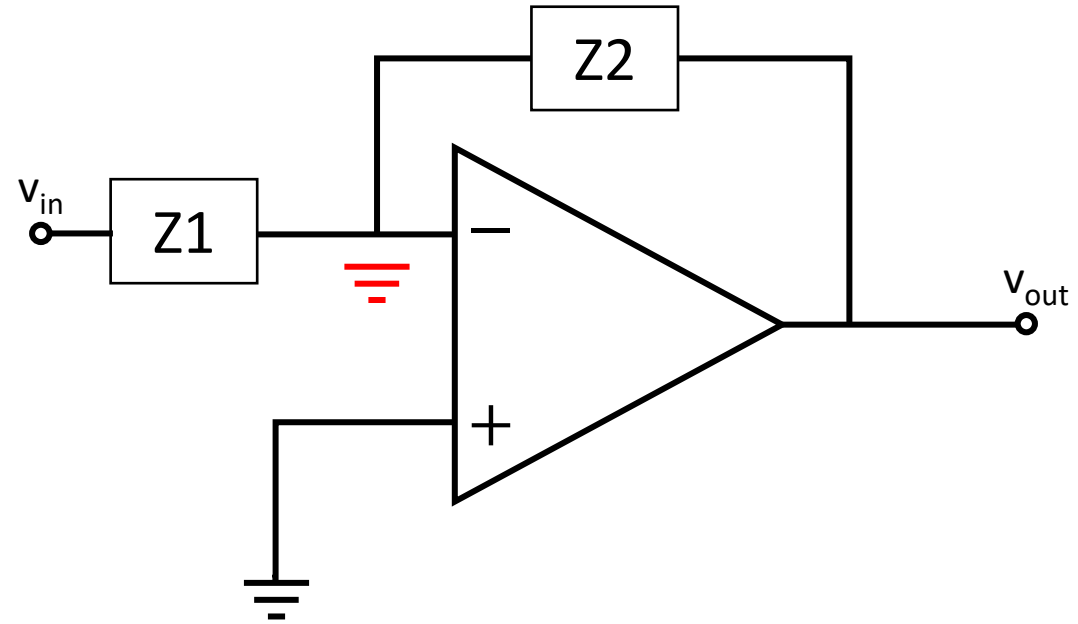

Sheet 2

1. For the circuit shown, obtain the transfer function $V_o(s)/V_i(s)$.

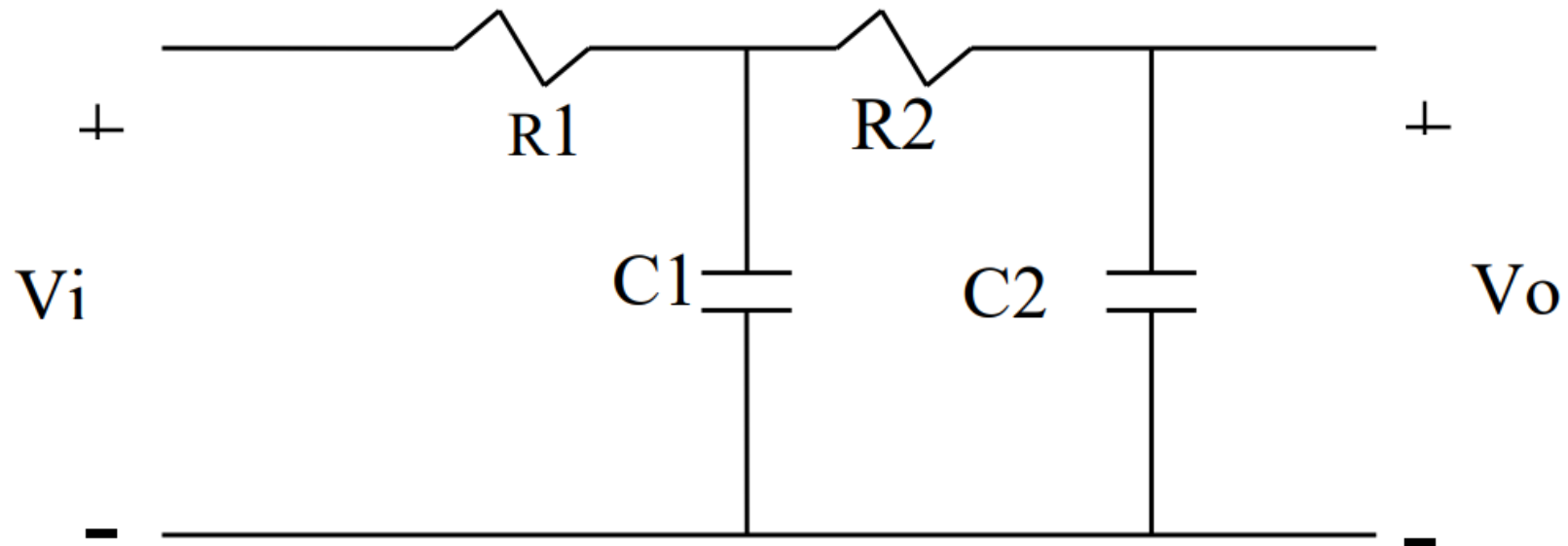

Sheet 2

2. For the Ideal Op-amp circuit shown, obtain the transfer function $V_o(s)/V_i(s)$

