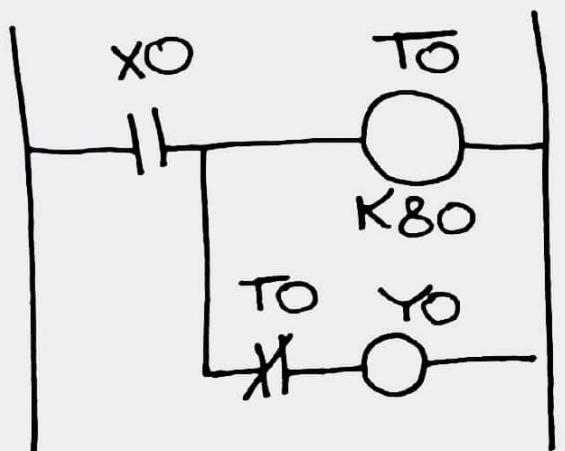



PLC Sheet 1

i)




\leftrightarrow LD X0
 OUT TO
 K80
 ANI TO
 OUT Y0

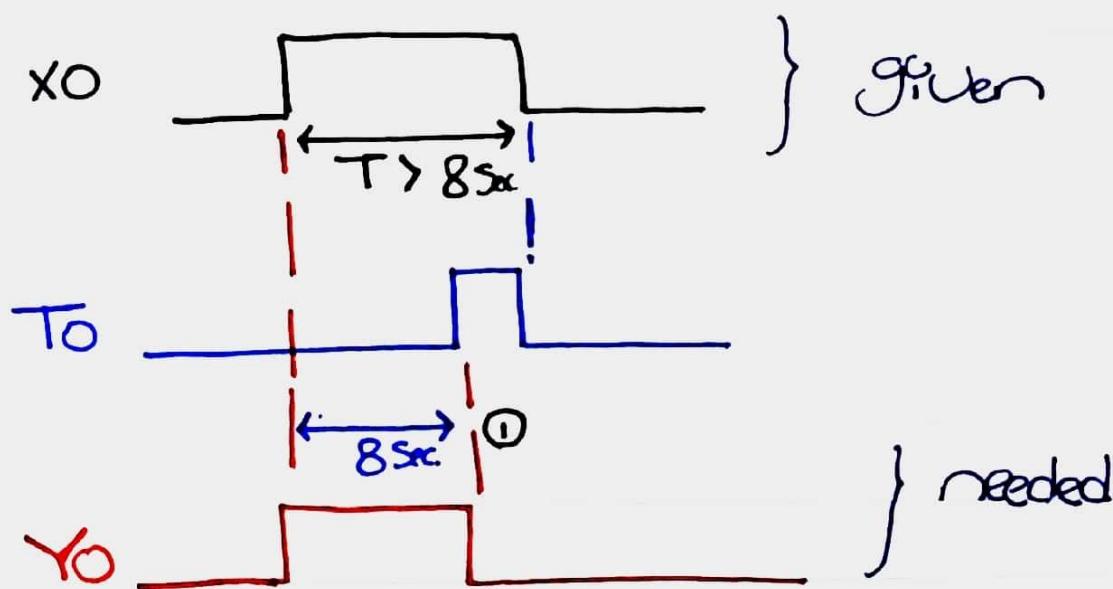} Corresponding logic instruction program



2)

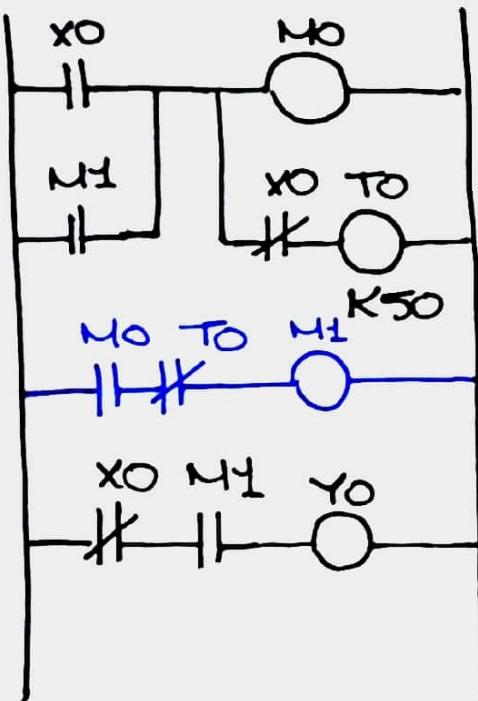

LD X0
 OR M1
 OUT M0
 ANI X0
 OUT T0
 K50
 LD M0
 ANI T0
 OUT M1
 LDI X0
 AND M1
 OUT Y0

$$\begin{aligned} M0 &= (X0 + M1) \\ T0(K50) &= (X0 + M1) \cdot \overline{X0} \end{aligned}$$


$$M1 = M0 \cdot \overline{T0}$$

Trace
Scientifically ↓

$$Y0 = \overline{X0} \cdot M1$$


X0	0	1	1	0	0	0	0
M0	0	0	0	0	1	1	0
T0	0	0	0	0	0	1	0
M1	0	1	1	1	1	0	0
Y1	0	0	0	1	1	0	0
						①	

} Given

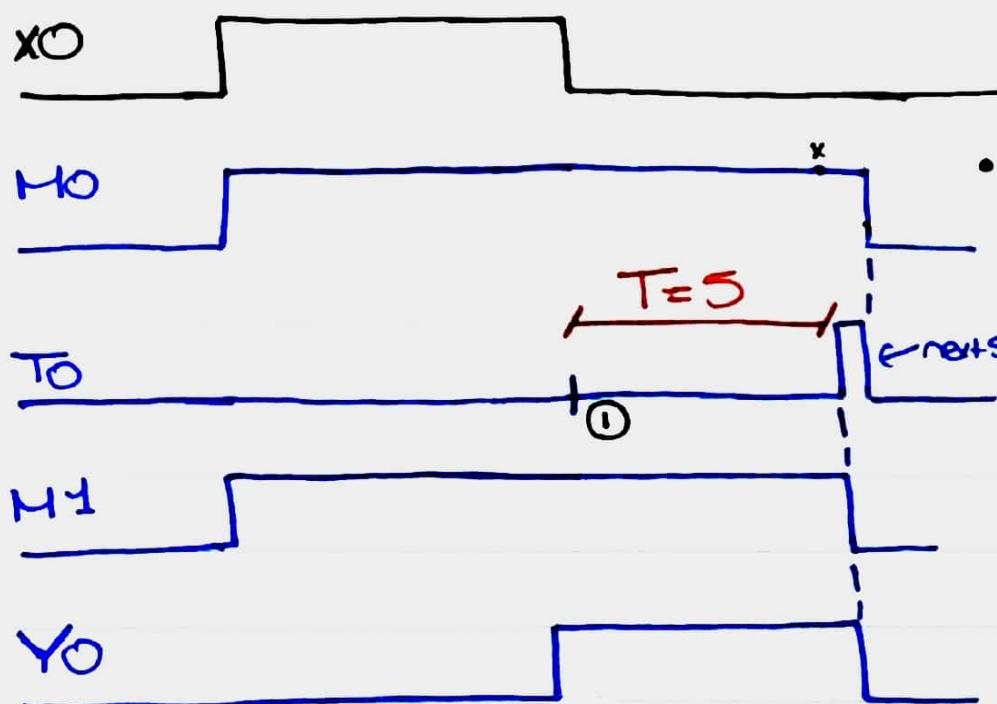

- Should actually drop here but it's okay to miss that (TA) and drop at x.

3)

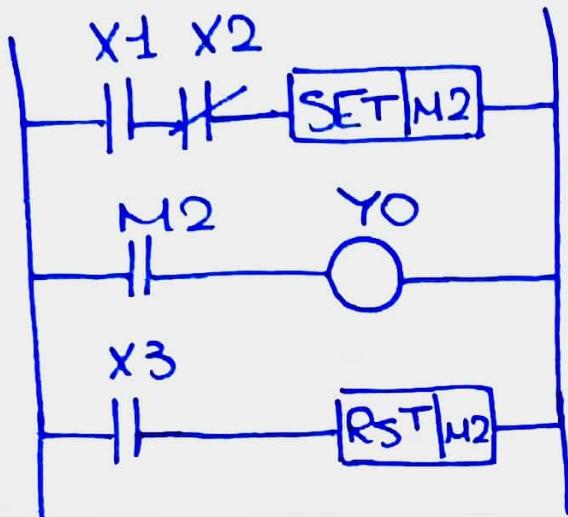

LD x1

ANI x2

SET M2

LD M2

OUT Y0


LD x3

RST M2

$$\cdot \text{SET}(M2) \equiv X1 \bar{X}2$$

$$\cdot Y0 \equiv M2$$

$$\cdot \text{RST}(M2) \equiv X3$$

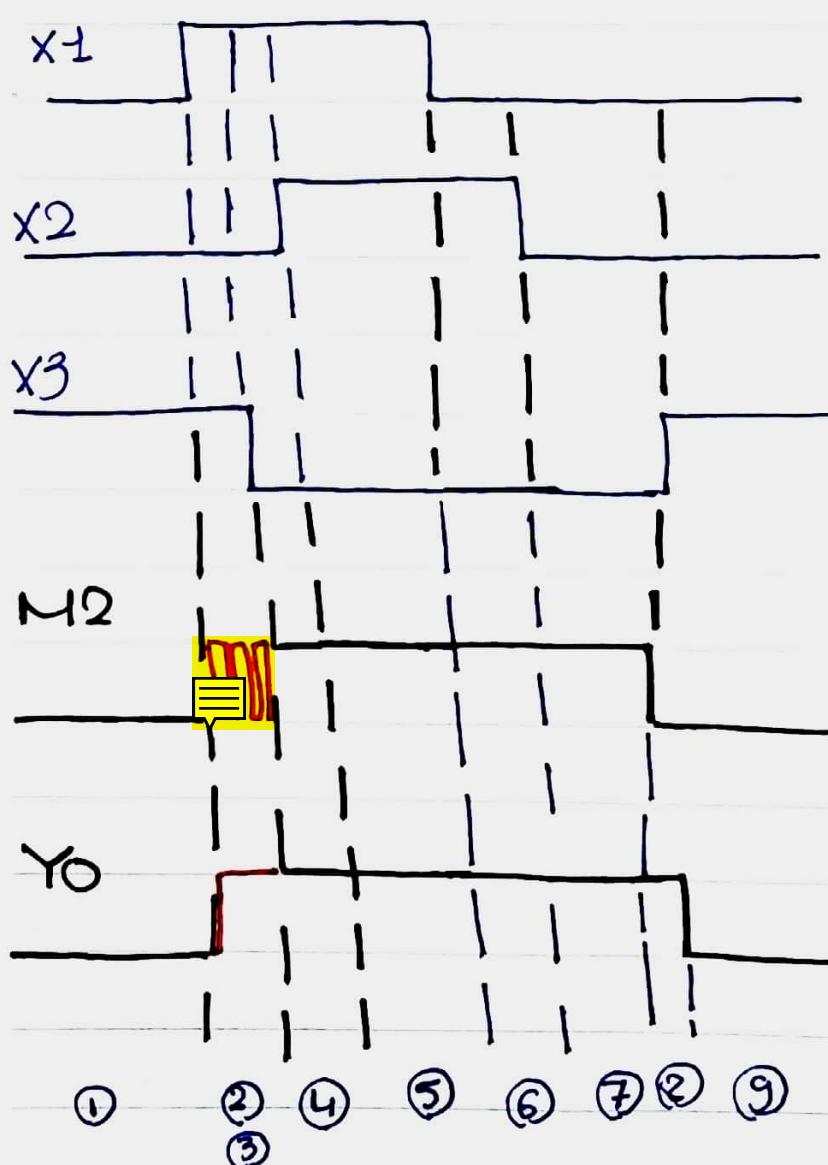

	①	②	③	④	⑤	⑥
X1	0	1	0	1	0	1
X2	0	1	0	1	0	1
X3	1	1	1	1	1	1
M2	0	1	0	1	0	0
Y0	0	1	0	1	0	1

• Now even if x1, x2 change
it will only drop when x3
is high and whereas Yt
drops, Y has took value
already → reflected next
cycle

	⑥	⑦	⑧	⑨
x1	0	0	0	0
x2	1	0	0	0
x3	0	0	0	1
M2	1	1	1	0
Y0	1	0	0	0

4) Draw ladder Diagram Such that

- X_0 becomes on $\rightarrow Y_0$ is activated
- From the Moment X_0 is off $\rightarrow Y_0$ is deactivated in 20 sec


$$\text{Set}(Y_0) \equiv X_0$$

• When X_0 becomes low we don't want $Y_0 \equiv 0$ immediately (so self-latch or Set/Reset)



$$T_1(K_2) \equiv \overline{X_0} \cdot Y_0$$

$$\text{RST}(Y_0) = T_1$$

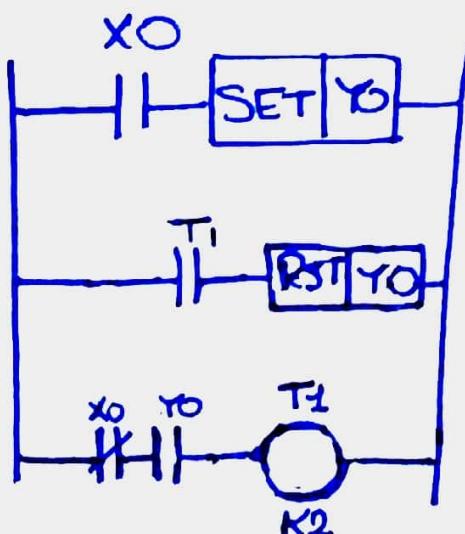If it's low already
then should not time
(no automatic turn off)



or equivalently

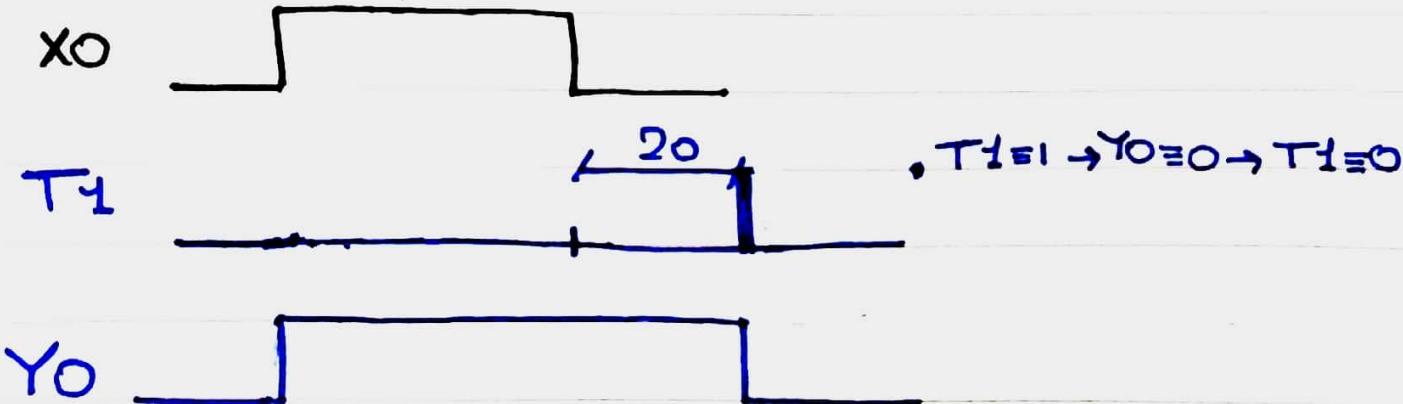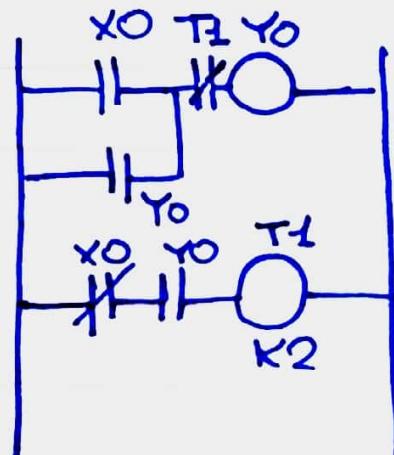

5) Draw ladder diagram such that

- There are 3 inputs x_1, x_2, x_3
- One output y_1
- Activated when exactly 2 out of the 3 inputs become on and deactivated o.w.

$$Y_1 \equiv (x_1 \cdot x_2 \cdot \bar{x}_3) + (x_1 \cdot \bar{x}_2 \cdot x_3) + (\bar{x}_1 \cdot x_2 \cdot x_3)$$

LD x_1

AND x_2

ANI x_3

LD x_1

ANI x_2

AND x_3

ORB


LDI x_1

AND x_2

AND x_3

ORB

OUT Y_1

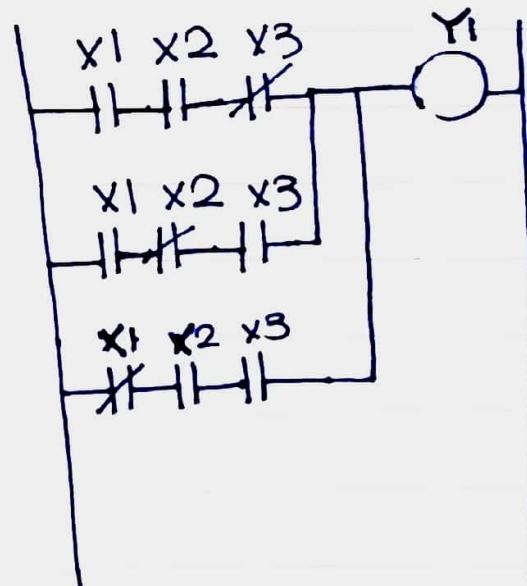


6)

Important!


Also solved in lecture

Given:

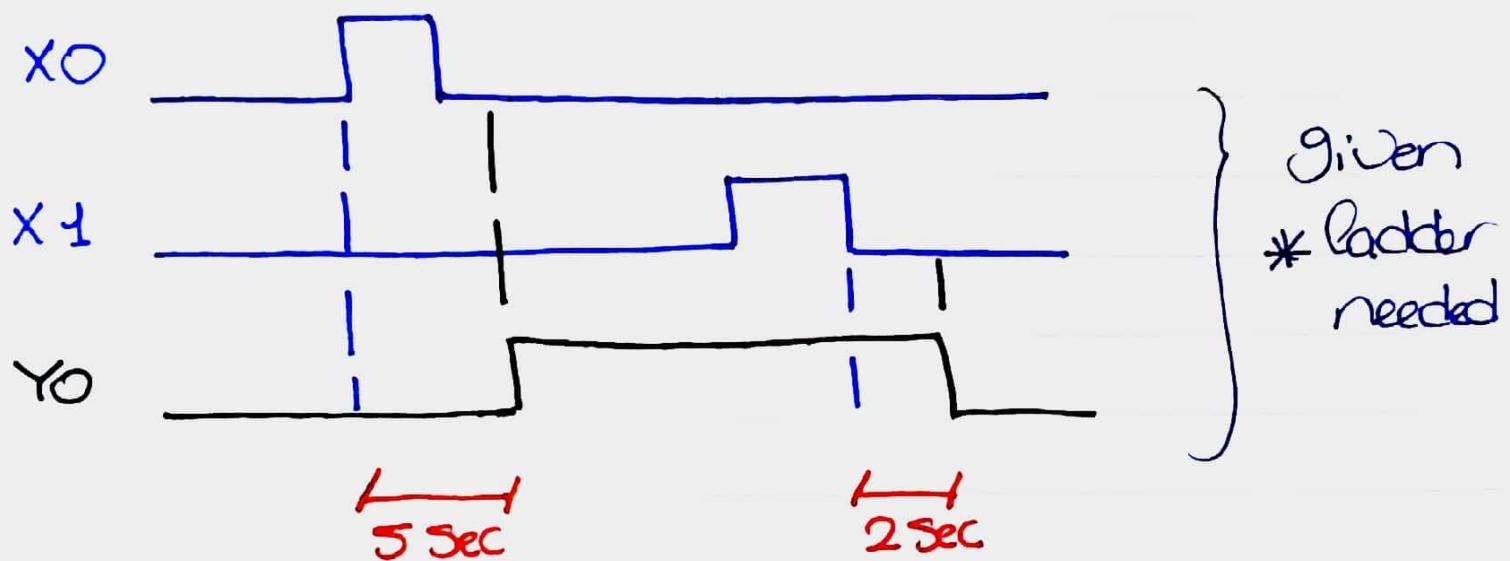

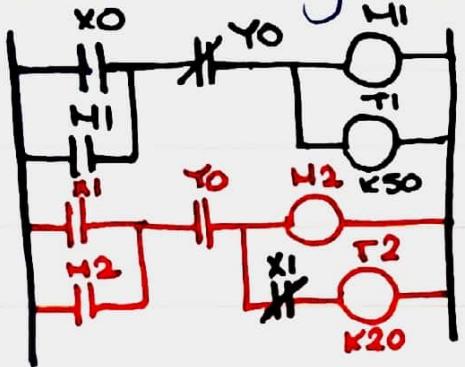
1. Rising edge on X_0 Sets a 5 Second timer and it keeps timing even after $X_0=0 \rightarrow$ The timer Sets Y_0 high at timeout
2. Falling edge on X_1 Sets a 2 Second timer
→ Such falling edge must come after a rising edge (i.e. check for rising then add a condition to trigger at falling) □

→ Since no timer should be set if Y_0 is already high
① or already low ② we capture these 2 by drawing



Captures ①



Captures ②

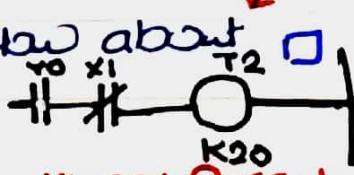Worked in
#4

How about
• X_1 not Pressed
→ automatic turn off

- Note that M1, M2 are needed so that the rising edge on X0, X1 resp. is captured whenever it occurs

Now need to add as well

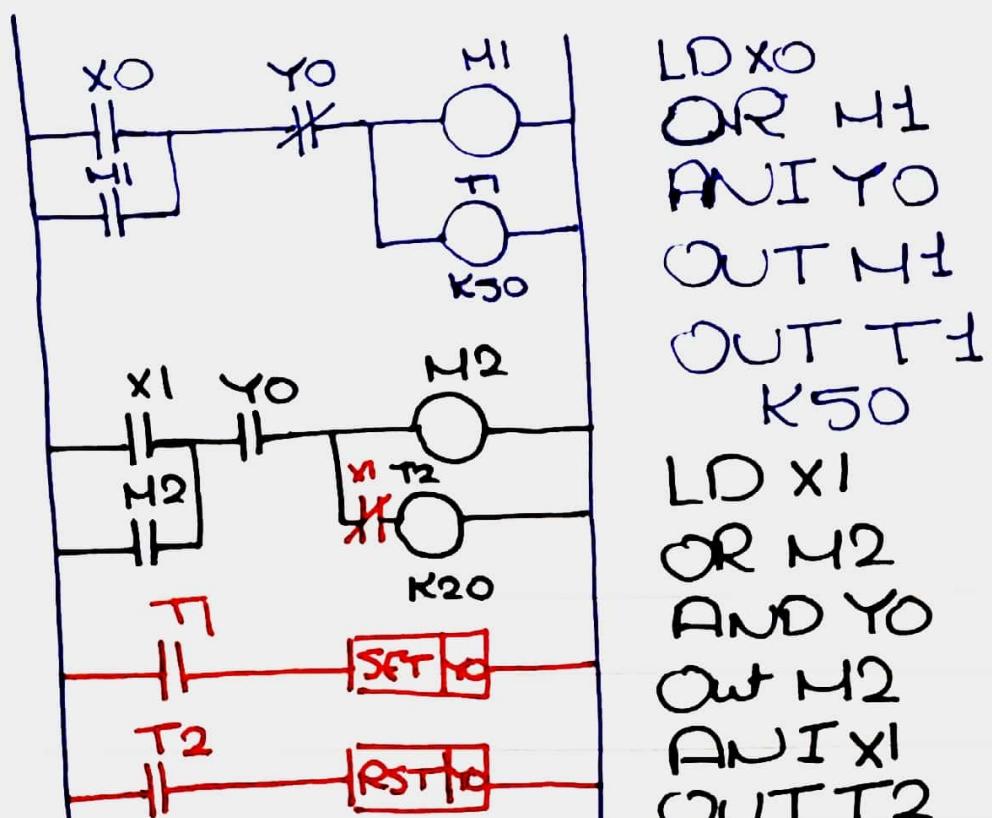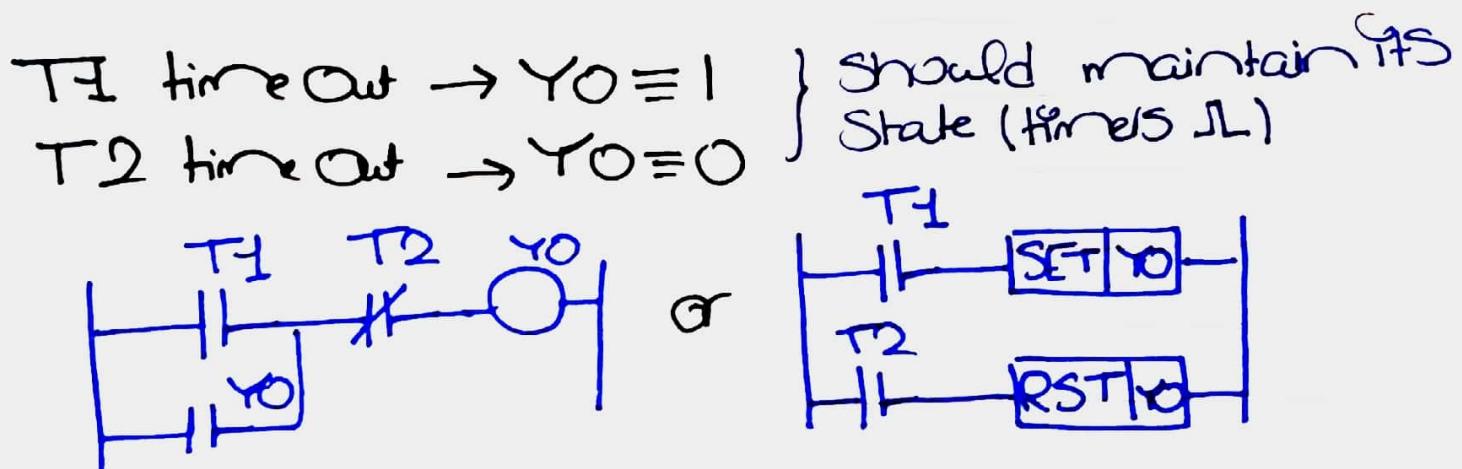


LD X0
OR M1
ANI Y0
OUT M1
OUT T1
K50
LD X1
OR M2
AND Y0
Out M2
ANI X1
OUT T2
K20


LD T1
SET Y0
LD T2
RST Y0

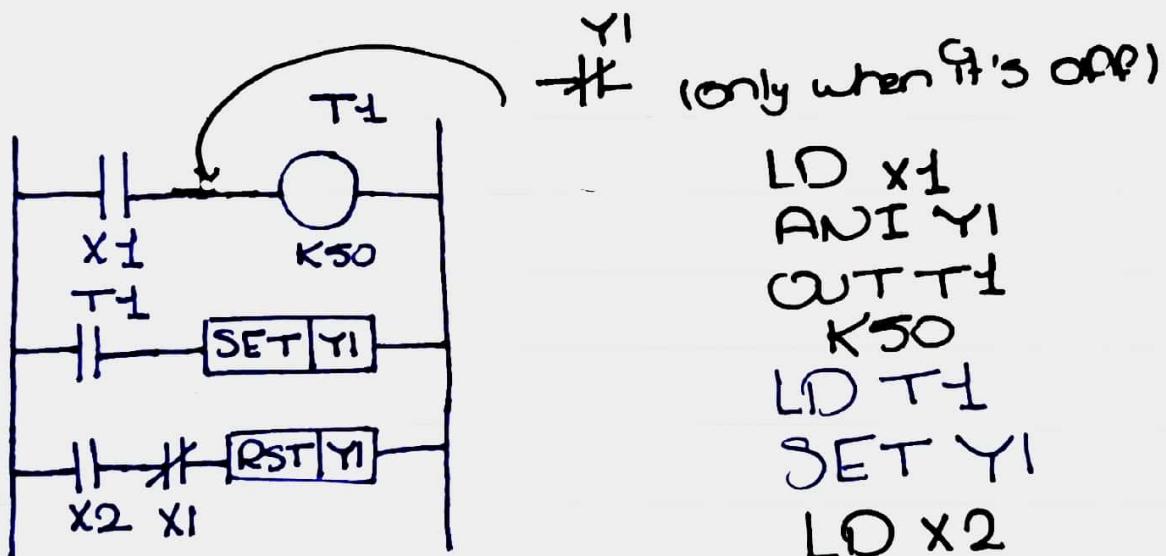7)

- X1 Continuously Pressed For 5sec → activate or more → Y1
else → not activated
- X2 Pressed while X1 isn't → Deactivate Y1





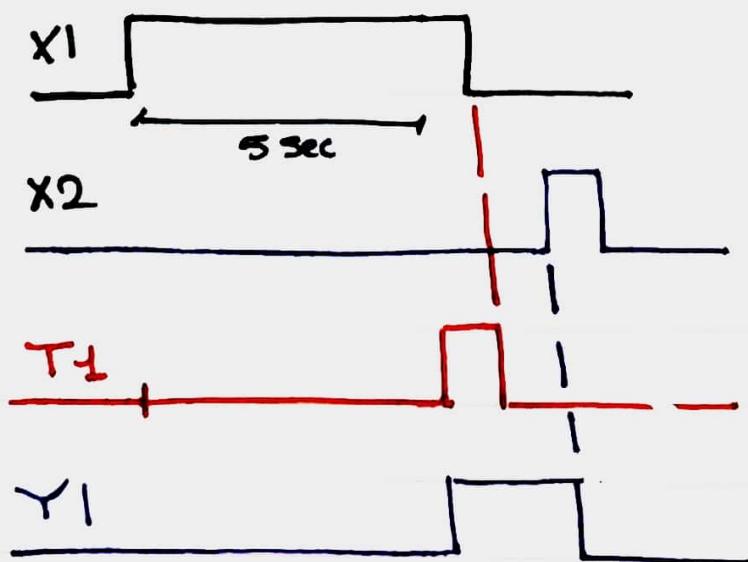LD X1
ANI Y1
OUT T1
K50
LD T1
SET Y1
LD X2
LDI X1
RST Y1




8)

Will be 1 after 3 rising edges on X1

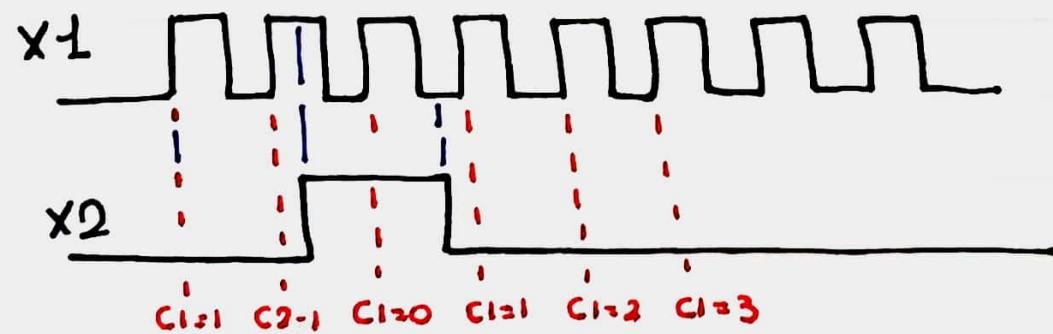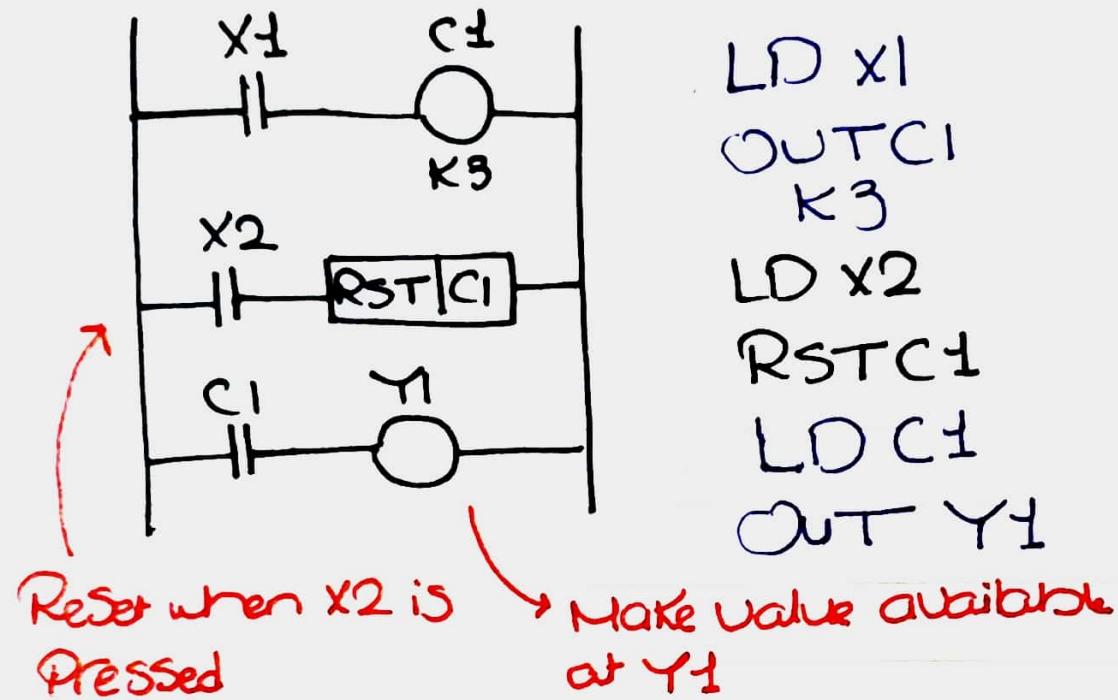


Y1 (and C1)

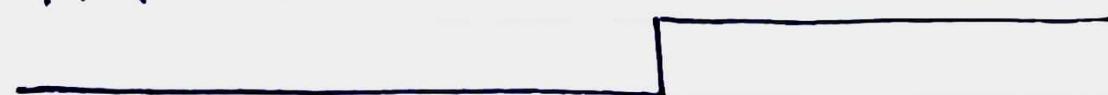

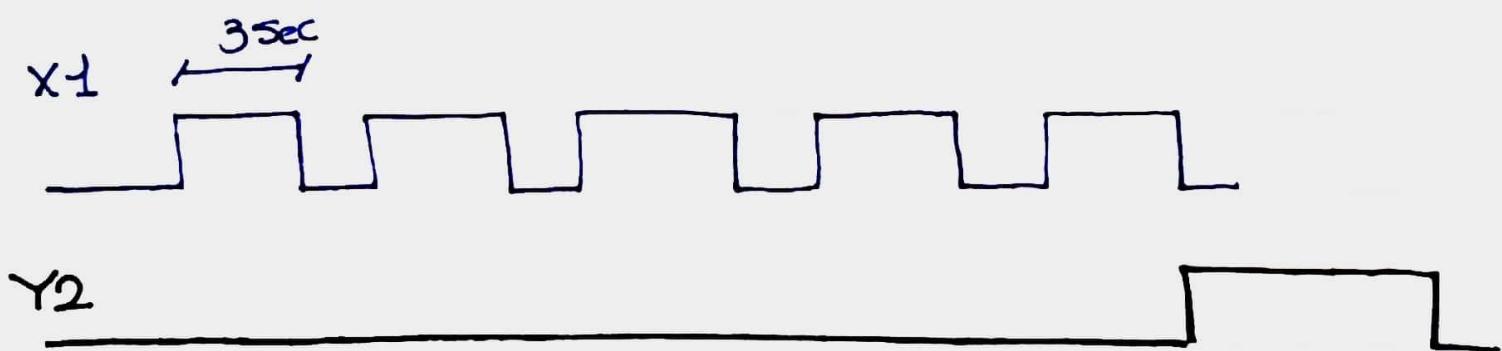g) Draw ladder diagram such that

- X_1 is pressed and released 5 times with each press lasting > 3 seconds


Y_2 is activated for 20 minutes $\xrightarrow{\hspace{1cm}}$



- Let's start by ignoring the 20 minute constraint.

- Use a timer that is set when X_1 is high for > 3 seconds
- Let a counter count the rising edges on that timer (each is associated with one X_1 pulse lasting > 3 seconds)
- Such counter would be reset when Y_1 goes high (Objective fulfilled)
- Hence, when it sets Y_2 's value we'll need to self-latch

Thus,

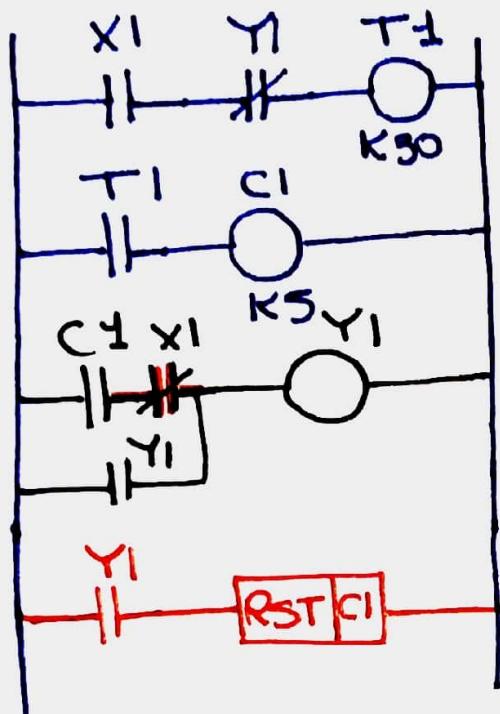


} Count Puses of $T > 3 \text{ sec}$
 (and Set at 5 of them)

 } whenever 5 Puses are counted
 (and it's assured that the
 last one is also over)
 then Set Y_1
 } reset Counter when Y_1
 is high


- Now if we want the output to only last for 12000 deciSeconds we can introduce a disable latch condition to the 3rd ring (it has none so far) that comes from a timer that starts when Y_1 is set.

i.e. update the 3rd ring to

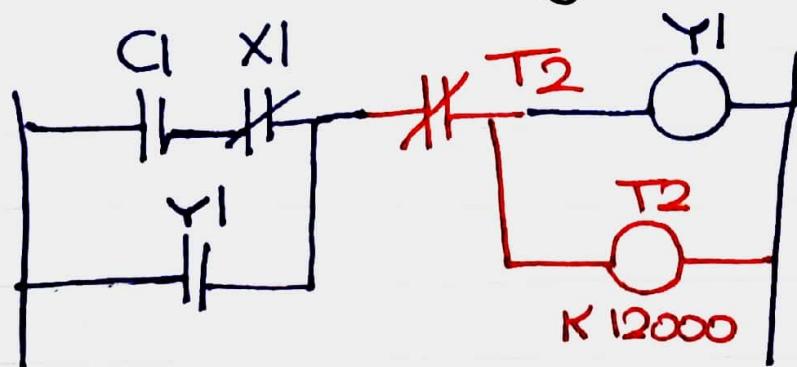

10) 6-a)



• Solved in lecture

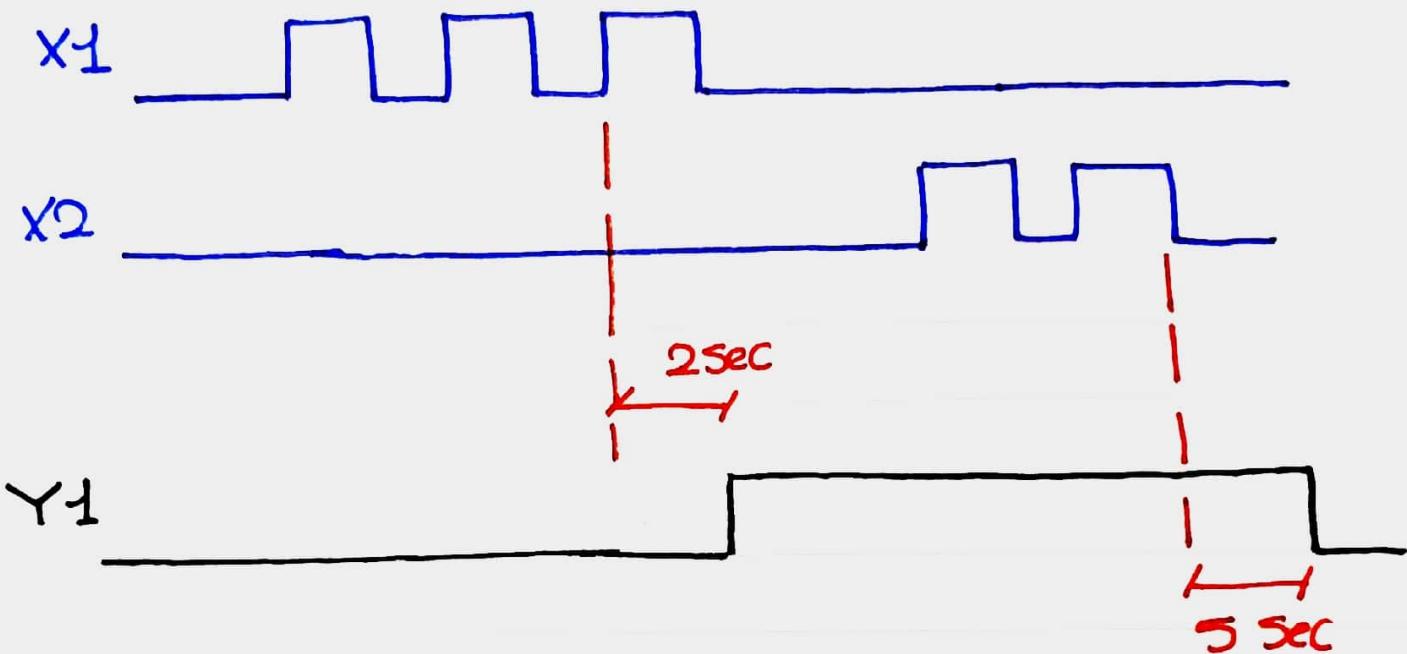


1. Y_1 is set once X_1 rises 3 times and then 2 seconds have lasted \rightarrow reset counter at $Y_1=1$

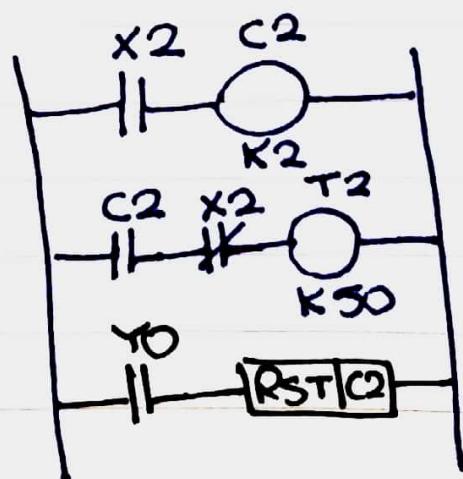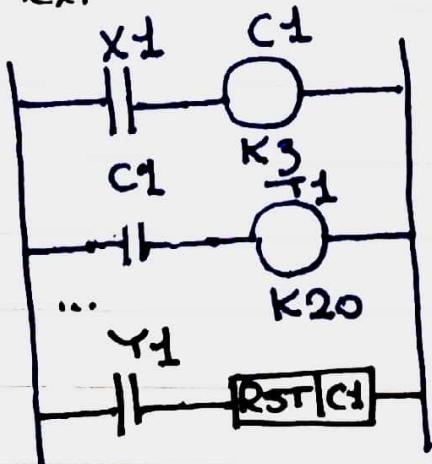2. It's reset once X_2 falls 2 times and then 5 seconds have lasted \rightarrow reset counter at $Y_1=0$

• Once we're done with these, timer output logic will be next



Timer- OutPut logic

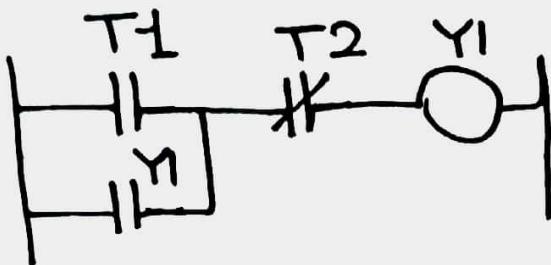


- Set whenever T_1 times out
- Reset whenever T_2 times out


- Now need to revisit ①, ② so that
 - Counting is disabled if Y is already in the right state
 - Rising edges don't count if the other input is high (Perhaps* good practice but optional)

* Check [CE Lecture 13] to round it out.

10) 16-b)

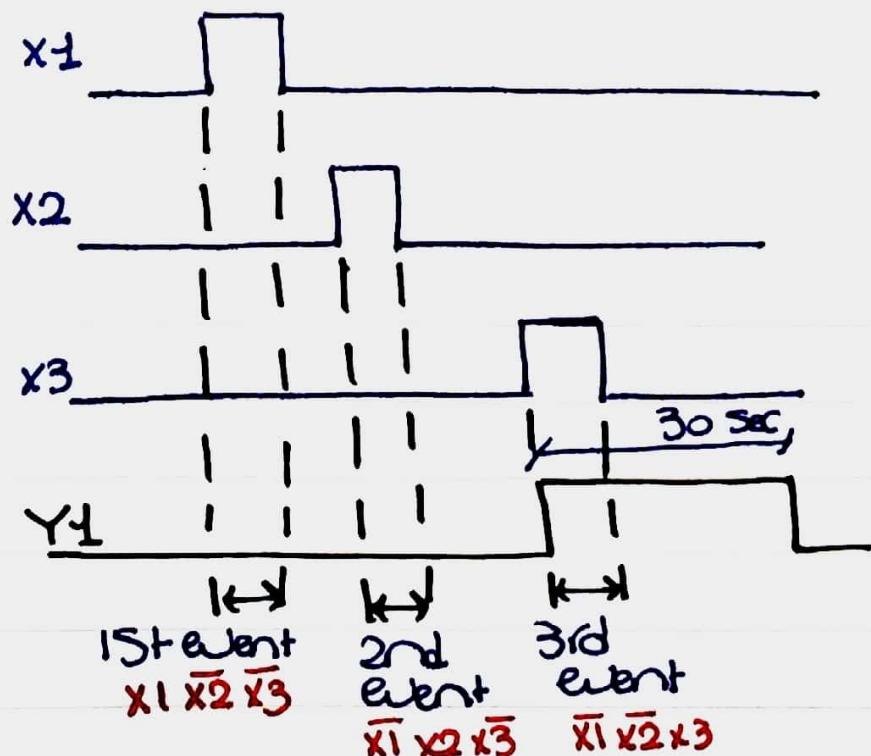

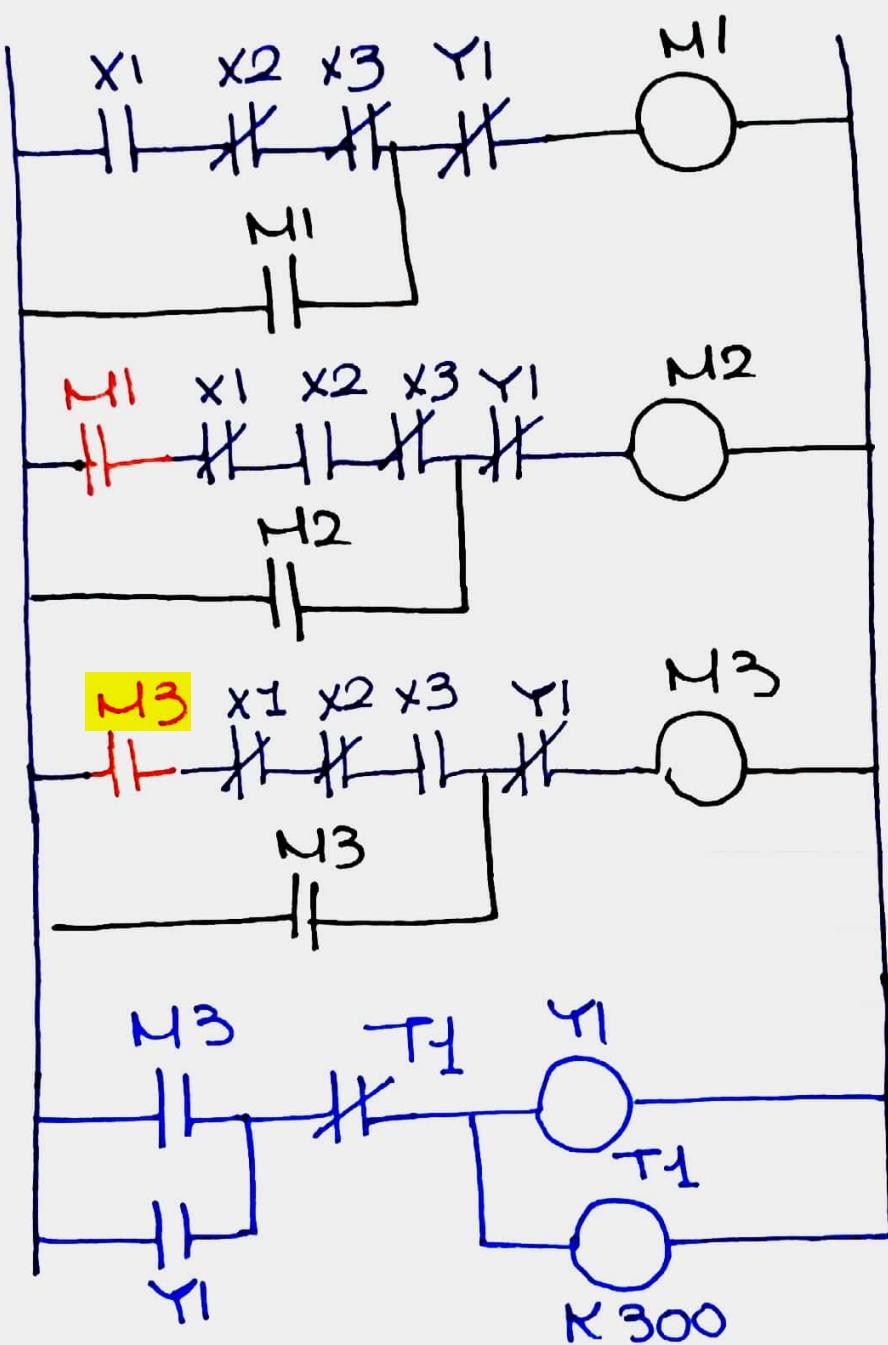- Have a sequence of events that should take place at a particular order.
- When event #1 occurs, store in a marker
- Use it while checking for next event & store in another marker...



- M1 stores occurrence of 1st event

- stores occurrence of 1st & 2nd event

- stores occurrence of all 3 events (rising edge at 3rd)

- take action based on M3 (all events occurred)


* Notice that once Y1 goes high we reset the markers (Objective of $T_1 = 1$ is done and so they can be reused)

* Confirm that you have the ability to write the Instruction Programs for last 2 ladders.

Thank you !!.

Some PLC Common Patterns


1. Self-latching

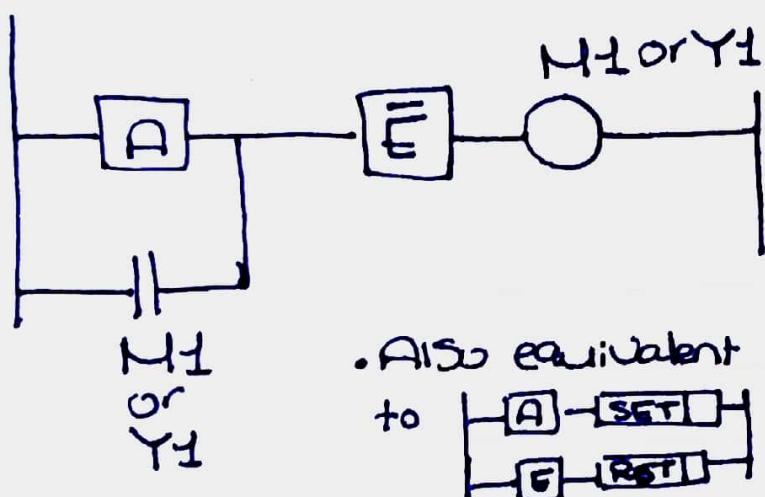

- Want M_1 or Y_1 to be high one A is satisfied.
- and to reset once / be disabled as long as E is satisfied.


Basic example) $A = \frac{1}{x_0}$

$$\bar{E} = \frac{1}{x_2}$$

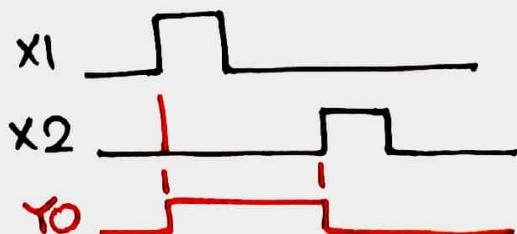


. Models a Push button

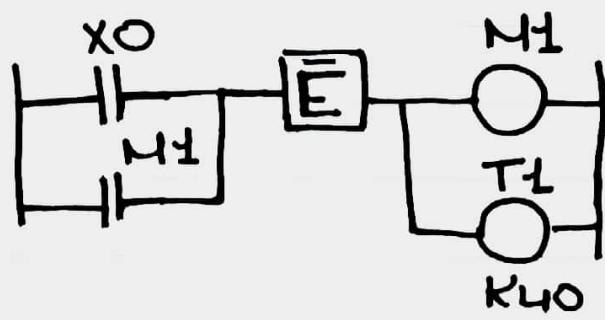2. Timer Starts at rising edge of X_0 (e.g. button Press)





- \bar{E} is what resets the timer
- M_1 makes it possible to drop X_0 again (+ve edge triggered)

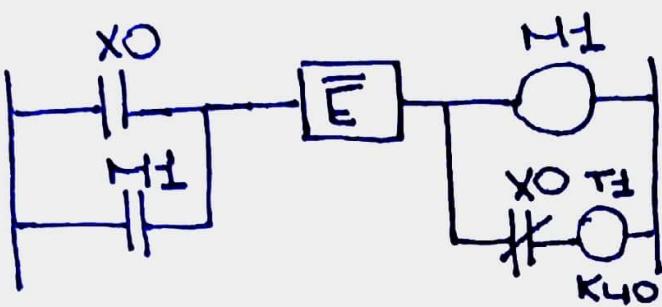3. Timer Starts at Falling edge of X0 (button release)




- Just like the rising edge case but we wait first for $\rightarrow \text{X0}$ (Falling edge) to trigger the timer.


4. OutPut enabled after N rising edges

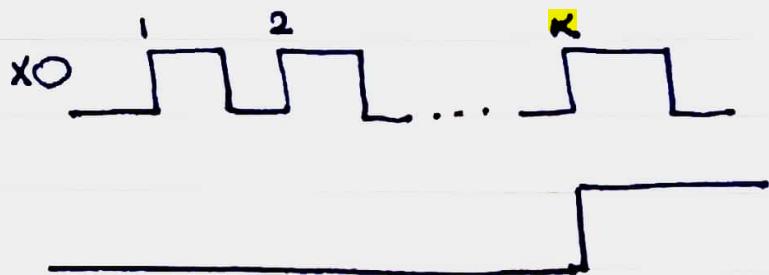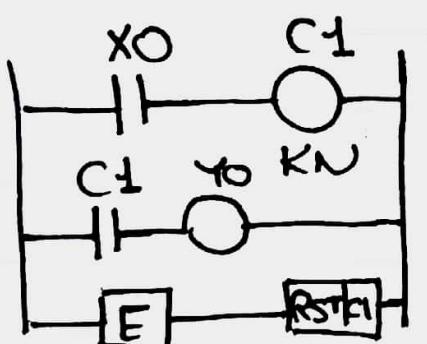

5. OutPut enabled after N Falling edges

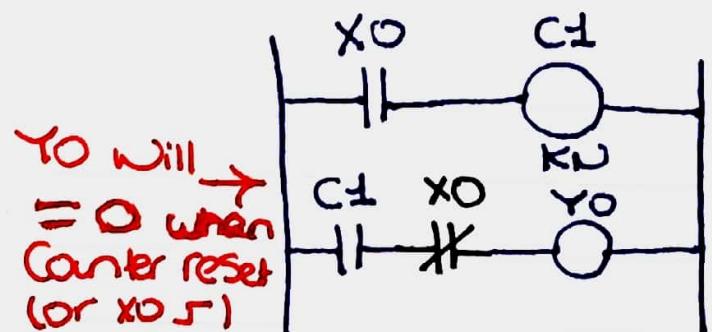


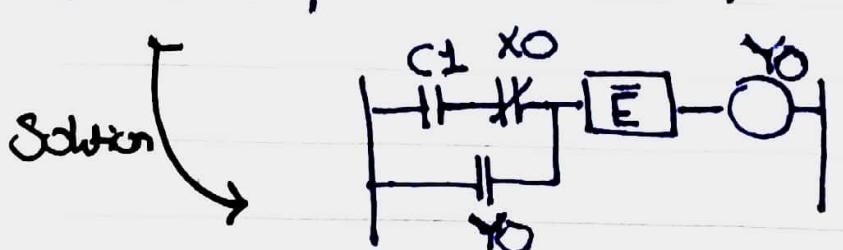- This counts N rising edges
- Then waits for one more falling edge before energizing output.




→ Y0 is set up N falling edges occur & reset upon E.

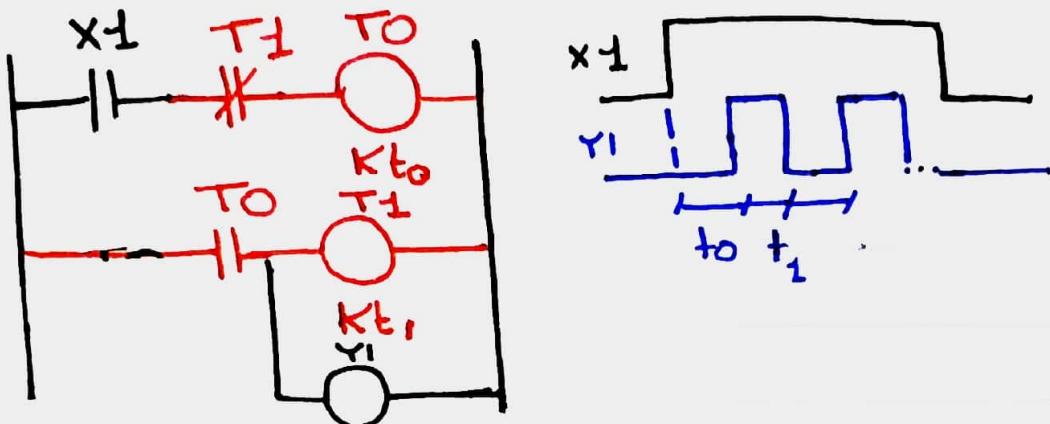
6. Clock that is off for t_0 deciseconds and on for t_1 deciseconds as long as x_1 is high



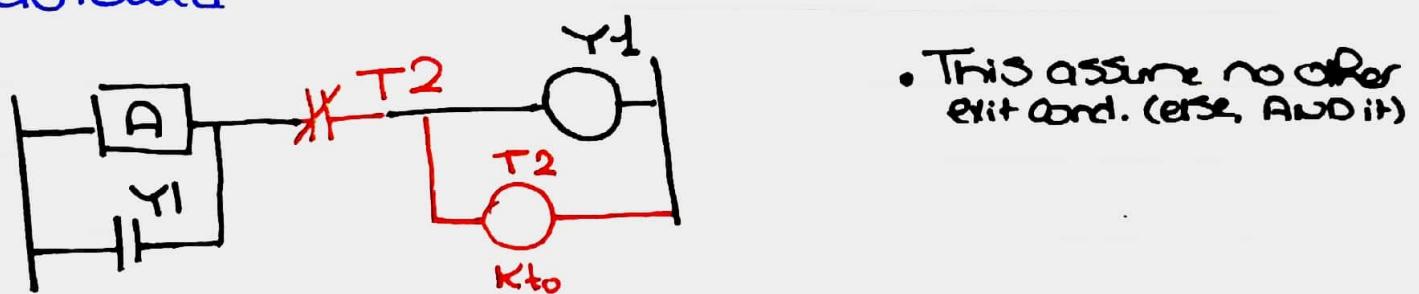7. Output that last to deciseconds only since activated



8. Count the no. of input pulses | (N) each of duration $> t_1$

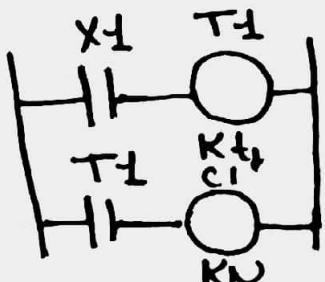

9. Wait for t_1 after N rising edges

