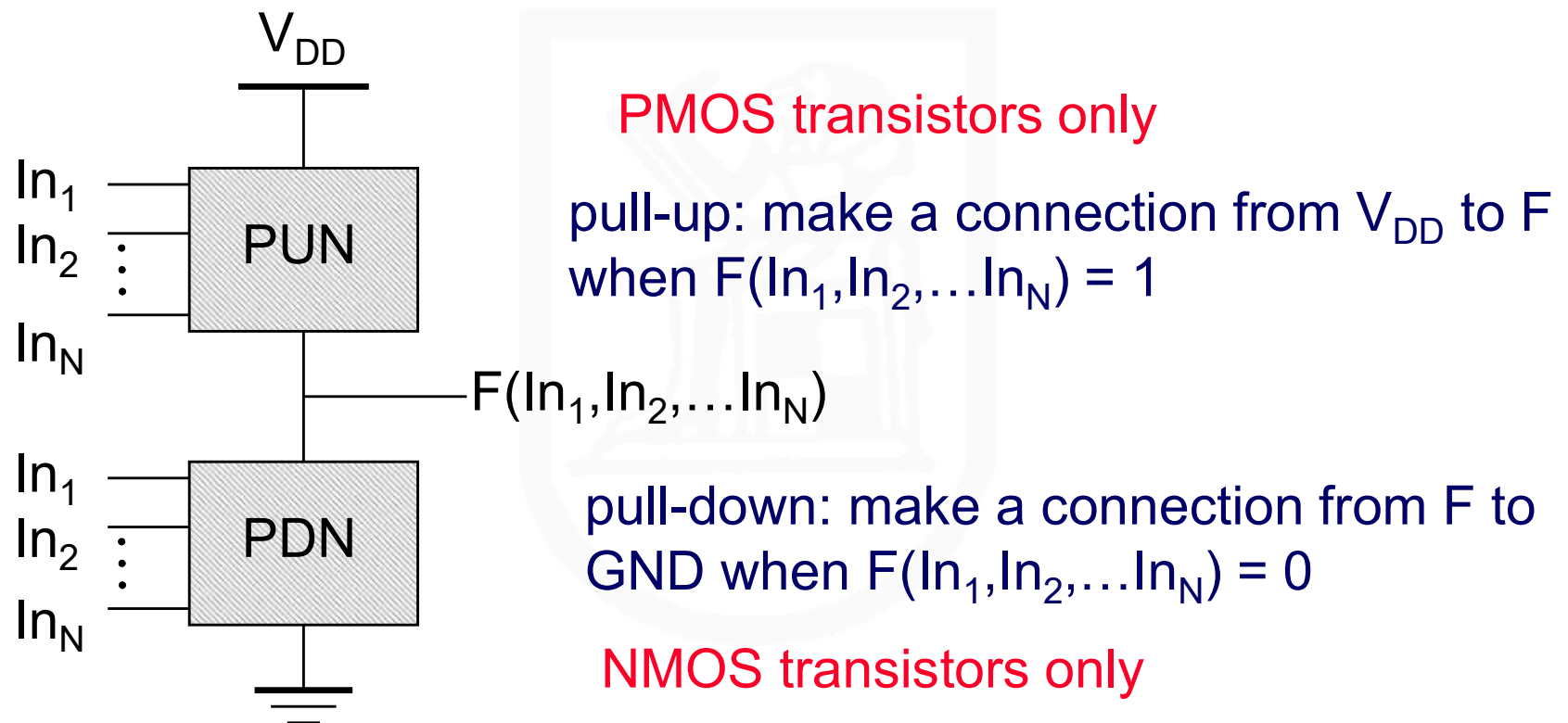


# Static Complementary CMOS: Complex Gates


- Pull-up network (PUN) and pull-down network (PDN)




PUN and PDN are **dual** logic networks

# Threshold Drops

PUN

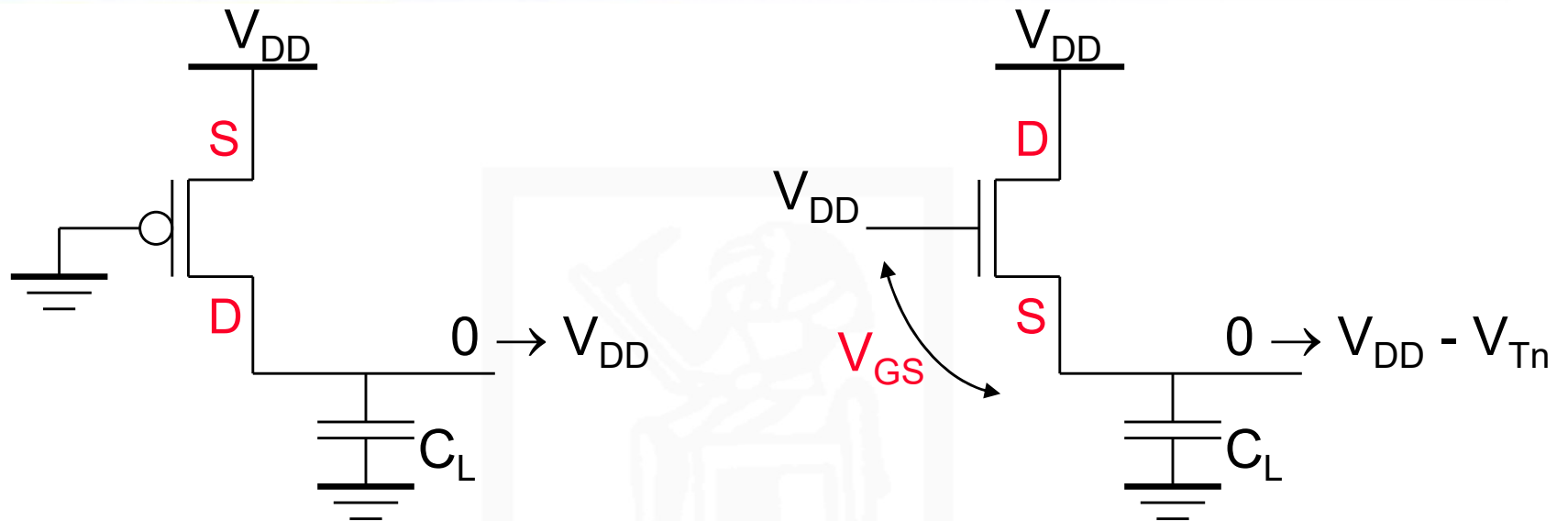


PDN

 

 
# Construction of PDN

- NMOS devices in **series** implement a NAND function



 - NMOS devices in **parallel** implement a NOR function



# Dual PUN and PDN


- PUN and PDN are dual networks
  - DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad [!(A + B) = !A \cdot !B \text{ or } !(A | B) = !A \& !B]$$


$$\overline{A \cdot B} = \overline{A} + \overline{B} \quad [!(A \cdot B) = !A + !B \text{ or } !(A \& B) = !A | !B]$$

- a **parallel** connection of transistors in the PUN corresponds to a **series** connection of the PDN
- A “complementary gate” is naturally **inverting** (NAND, NOR, AOI, OAI)
- Number of transistors for an N-input logic gate is **2N**


# CMOS NAND

 


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 


# CMOS NOR

 


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 

# Complex CMOS Gate

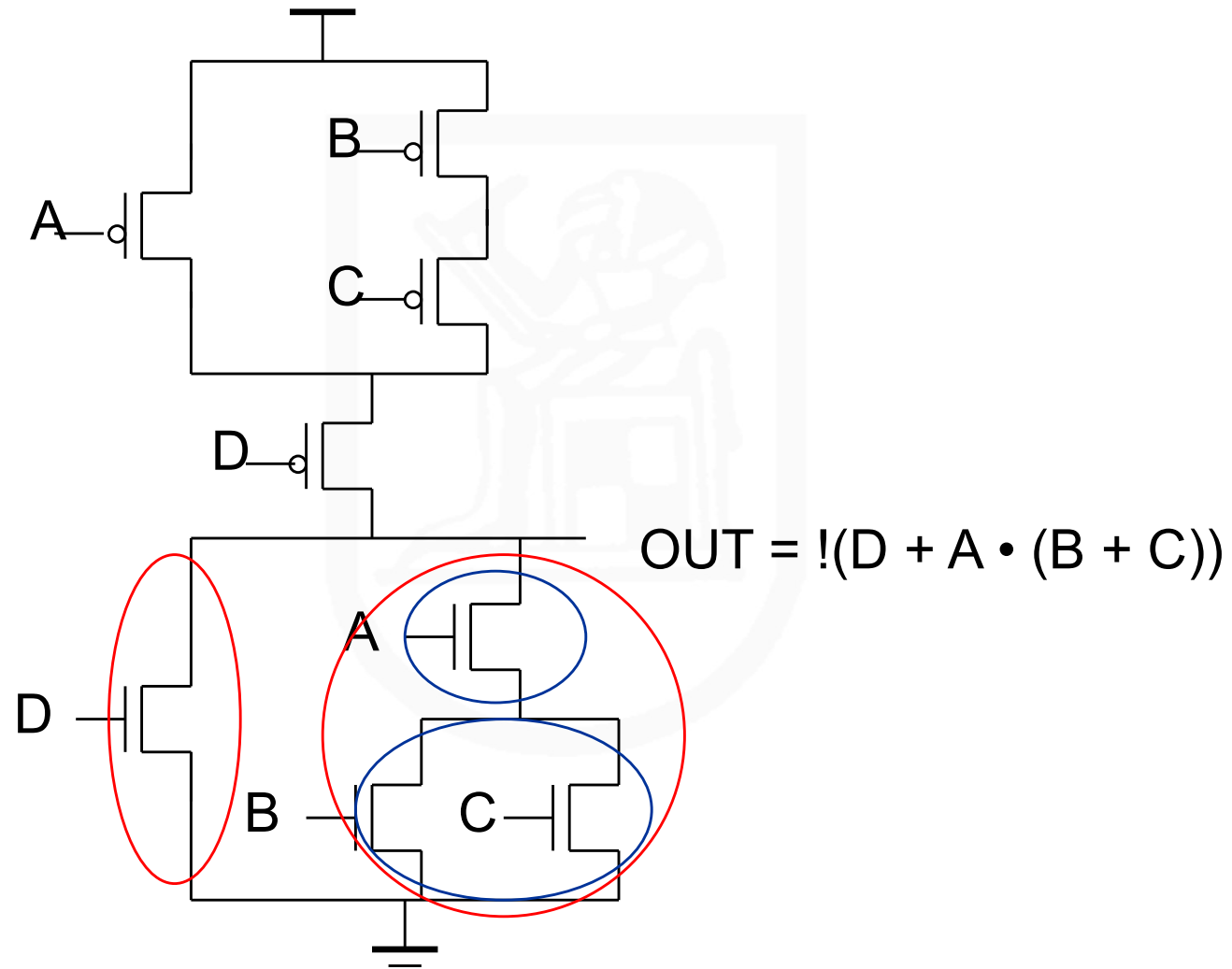

# Standard Cell Layout Methodology

 


# What logic function is this?

Contacts, vias and wells are not shown!




# OAI21 Logic Graph

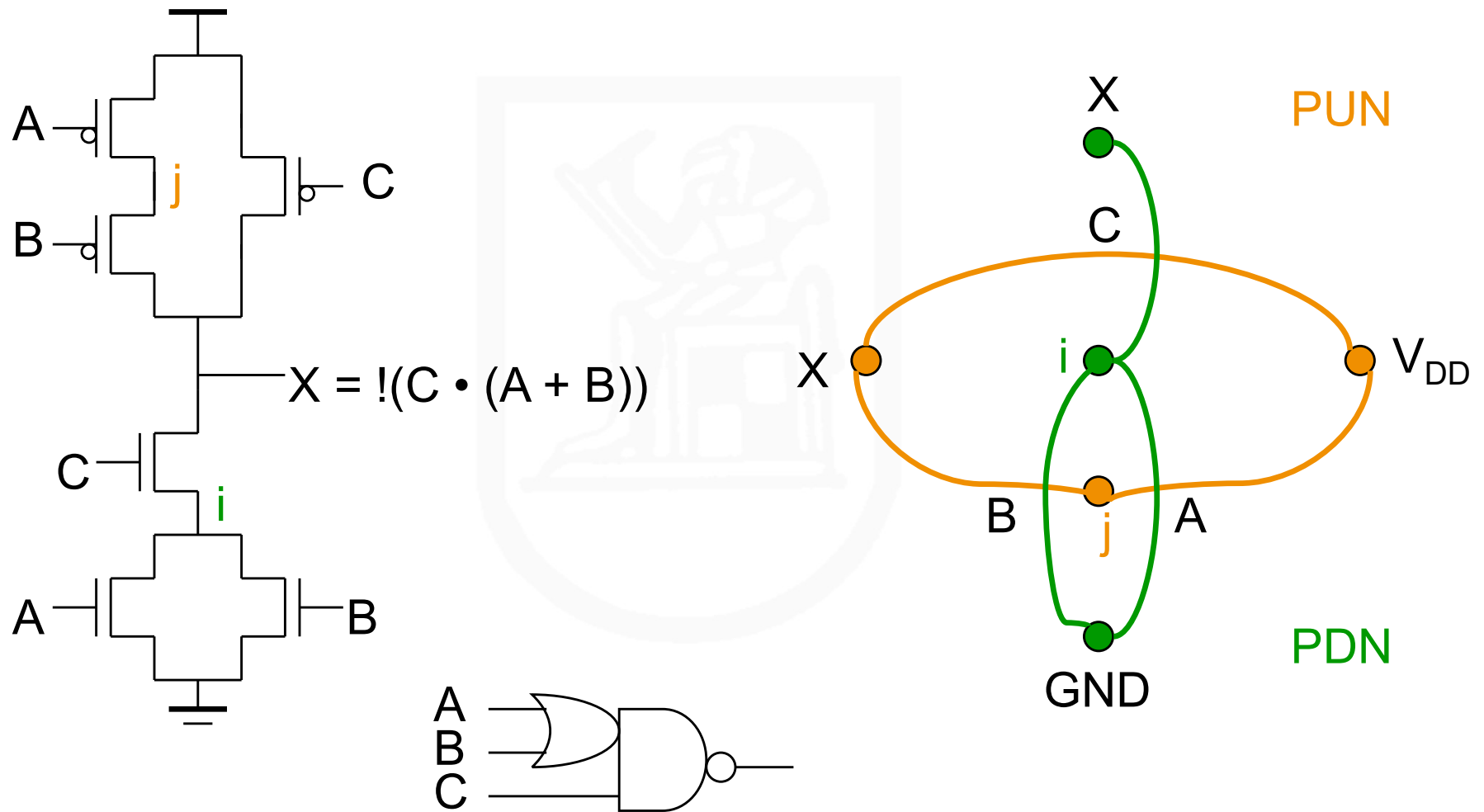

 
# Consistent Euler Path


- ❑ An uninterrupted diffusion strip is possible only if there exists an Euler path in the logic graph
  - Euler path: a path through all nodes in the graph such that each edge is visited once and only once.
- ❑ For a single poly strip for every input signal, the Euler paths in the PUN and PDN must be **consistent** (the same)



 
# Two Stick Layouts of $!(C \cdot (A + B))$



# OAI22 Logic Graph

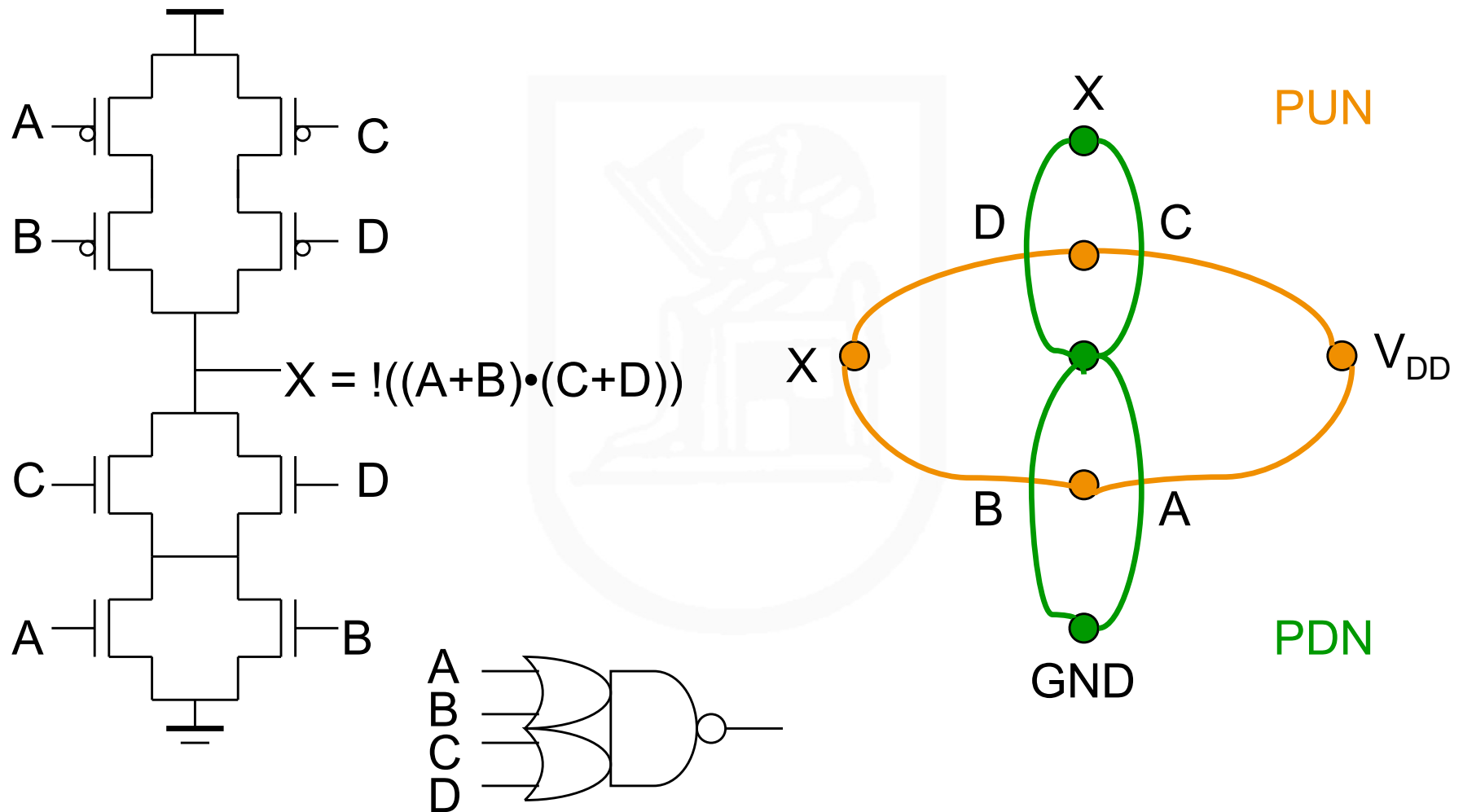


# OAI22 Layout



 


# XNOR/XOR Implementation

XNOR

 


XOR

   

- How many transistors in each?
- Can you create the stick transistor layout for the lower left circuit?
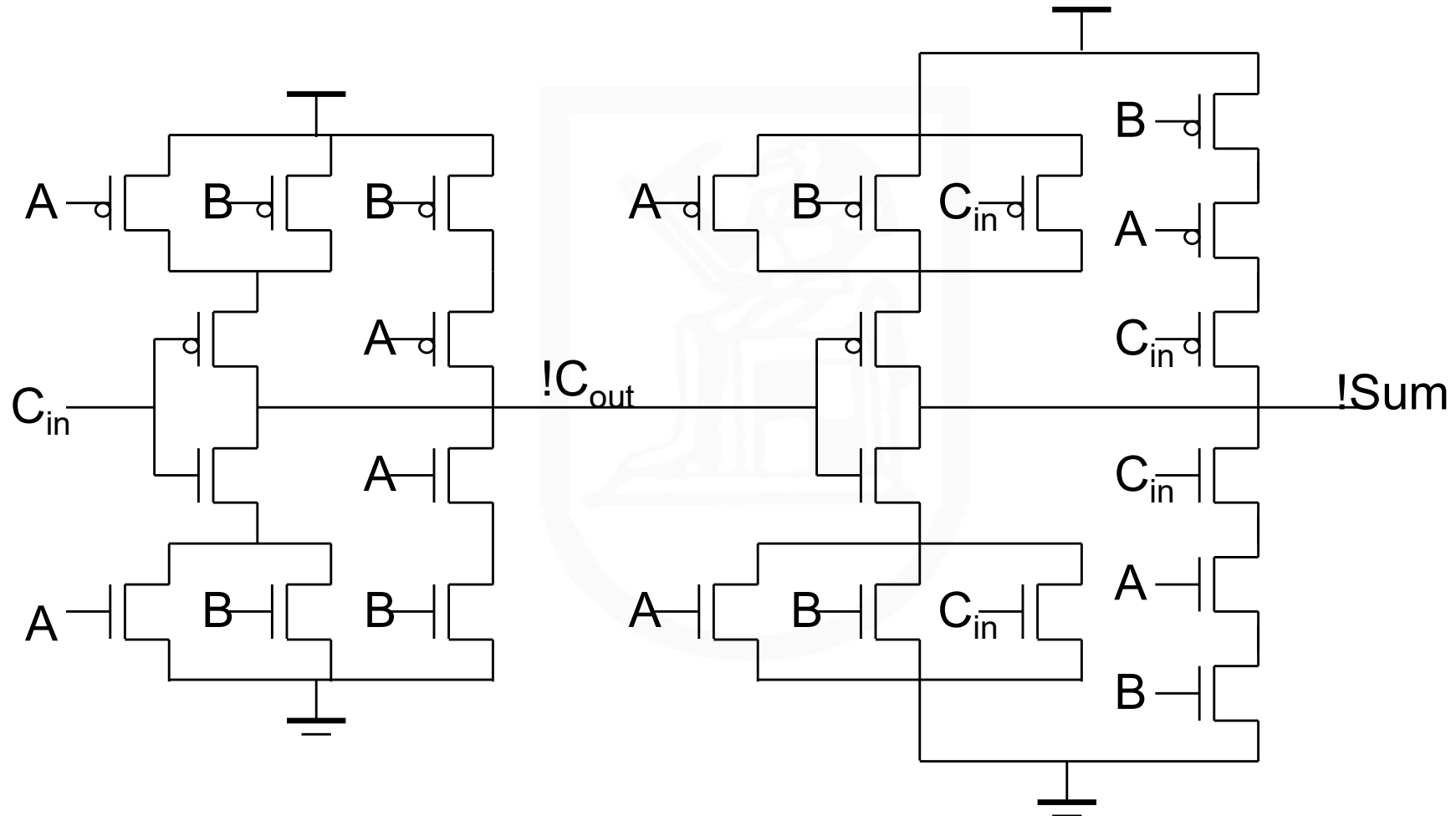
# Static CMOS Full Adder Circuit

$$\overline{C_{out}} = \overline{C_{in}} \& (\overline{A} \mid \overline{B}) \mid (\overline{A} \& \overline{B}) \quad \overline{Sum} = C_{out} \& (\overline{A} \mid \overline{B} \mid \overline{C_{in}}) \mid (\overline{A} \& \overline{B} \& \overline{C_{in}})$$




$$C_{out} = C_{in} \& (A \mid B) \mid (A \& B)$$

$$Sum = \overline{C_{out}} \& (A \mid B \mid C_{in}) \mid (A \& B \& C_{in})$$
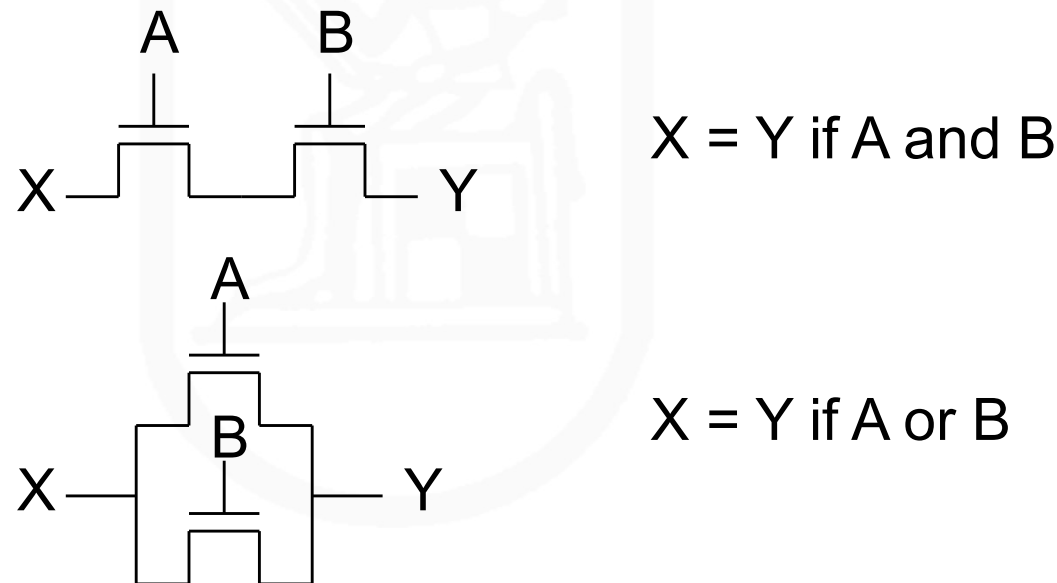
# NMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- NMOS switch closes when the gate input is high




- Remember - NMOS transistors pass a **strong** 0 but a **weak** 1



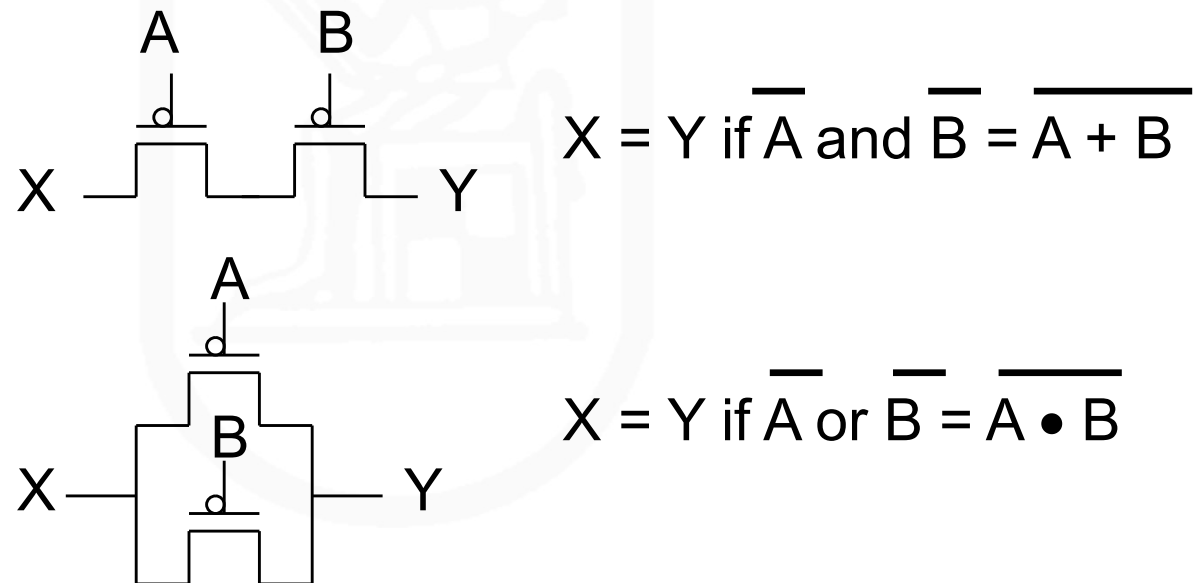
# PMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- PMOS switch closes when the gate input is low




- Remember - PMOS transistors pass a **strong** 1 but a **weak** 0

# Pass Transistor (PT) Logic

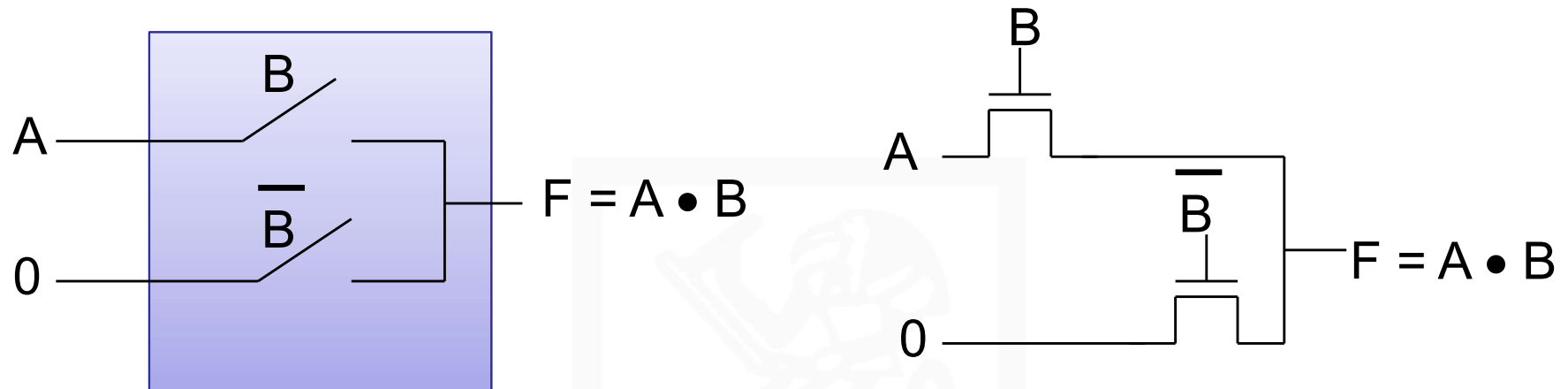

- ❑ Gate is static – a low-impedance path exists to both supply rails under all circumstances
- ❑  $N$  transistors instead of  $2N$
- ❑ No static power consumption
- ❑ Ratioless
- ❑ Bidirectional (versus unidirectional)

# VTC of PT AND Gate

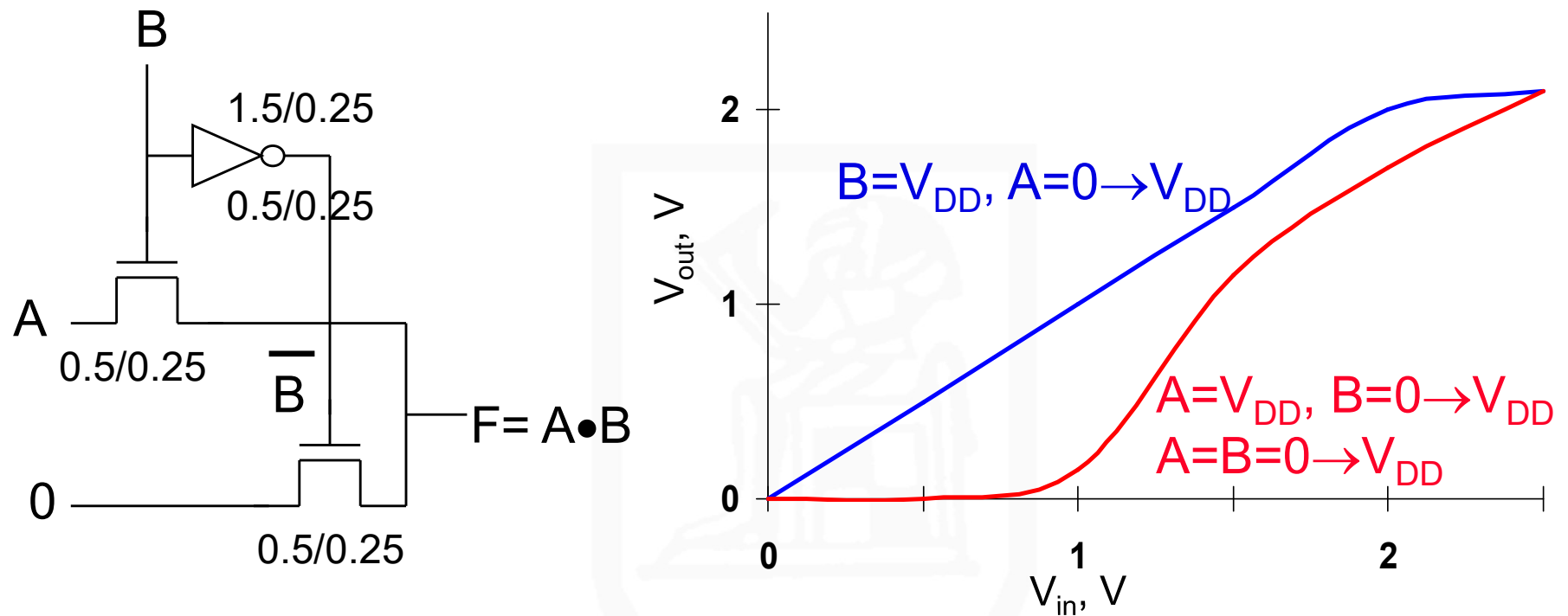

- Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)

# Remember

## Voltage-Current Relation: Linear Mode

For long-channel devices ( $L > 0.25$  micron)

- When  $V_{DS} \leq V_{GS} - V_T$

$$I_D = k'_n W/L [(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$$





where

$k'_n = \mu_n C_{ox} = \mu_n \epsilon_{ox}/t_{ox}$  = is the **process transconductance parameter** ( $\mu_n$  is the carrier mobility ( $m^2/Vsec$ ))

$k_n = k'_n W/L$  is the **gain factor** of the device

For small  $V_{DS}$ , there is a linear dependence between  $V_{DS}$  and  $I_D$ , hence the name resistive or **linear** region

# Differential PT Logic (CPL)

    


# CPL Properties


---

- **Differential** so complementary data inputs and outputs are always available (so don't need extra inverters)
- Still static, since the output defining nodes are always tied to  $V_{DD}$  or GND through a low resistance path
- Design is **modular**; all gates use the same topology, only the inputs are permuted.
- Simple XOR makes it attractive for structures like **adders**
- Fast (assuming number of transistors in series is small)
- Additional routing overhead for complementary signals
- Still have static power dissipation problems

# CPL Full Adder

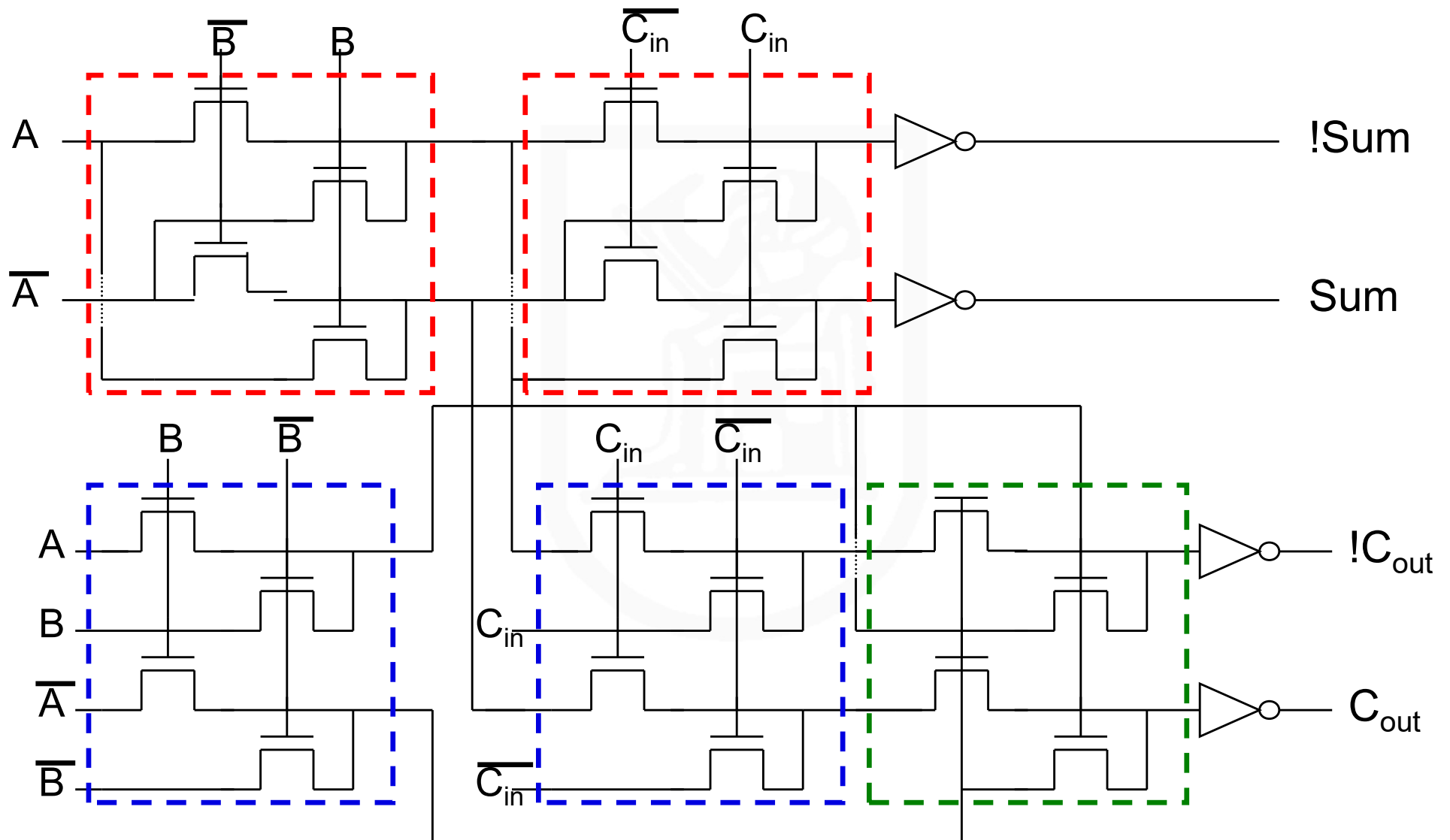


# NMOS Only PT Driving an Inverter

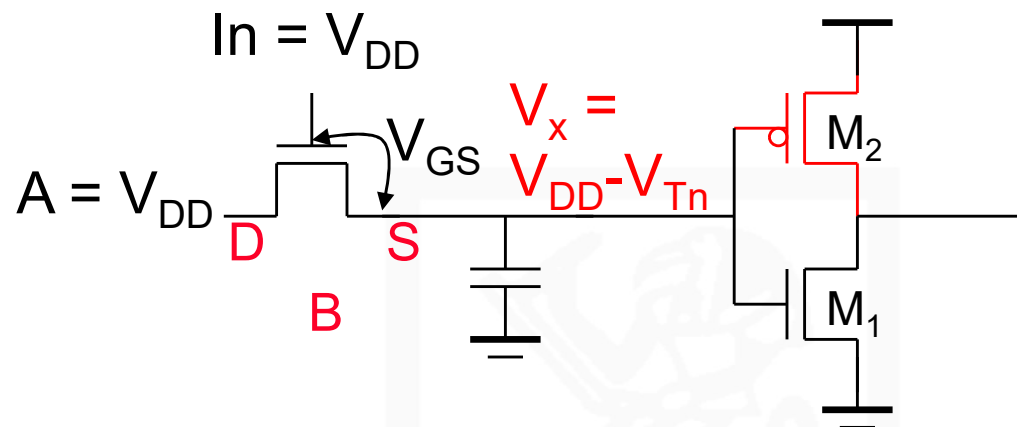

- $V_x$  does not pull up to  $V_{DD}$ , but  $V_{DD} - V_{Tn}$
- Threshold voltage drop causes static power consumption ( $M_2$  may be weakly conducting forming a path from  $V_{DD}$  to GND)
- Notice  $V_{Tn}$  increases for pass transistor due to **body effect** ( $V_{SB}$ )



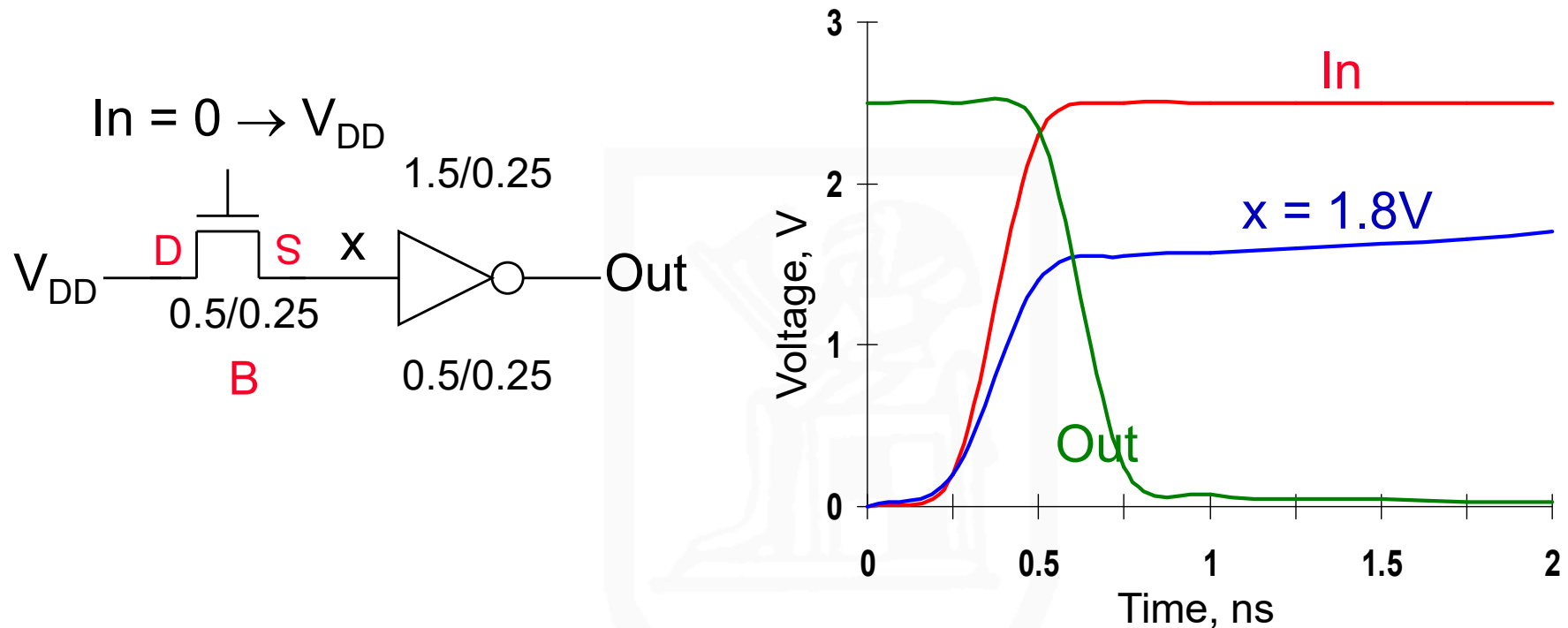
# Voltage Swing of PT Driving an Inverter



- **Body effect** – large  $V_{SB}$  at x - when pulling high (B is tied to GND and S charged up close to  $V_{DD}$ )
- So the voltage drop is even worse

$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{(|2\phi_f| + V_x)} - \sqrt{|2\phi_f|}))$$

# Cascaded NMOS Only PTs

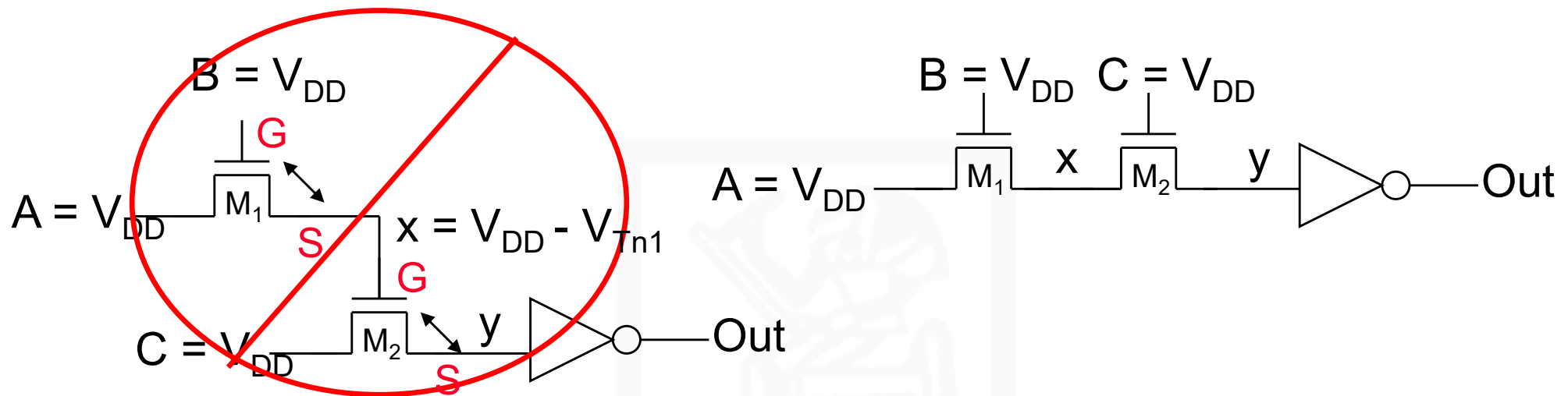


Swing on  $y = V_{DD} - V_{Tn1} - V_{Tn2}$

Swing on  $y = V_{DD} - V_{Tn1}$


- ❑ Pass transistor gates should **never** be cascaded as on the left
- ❑ Logic on the right suffers from static power dissipation and reduced noise margins

## Solution 1: Level Restorer

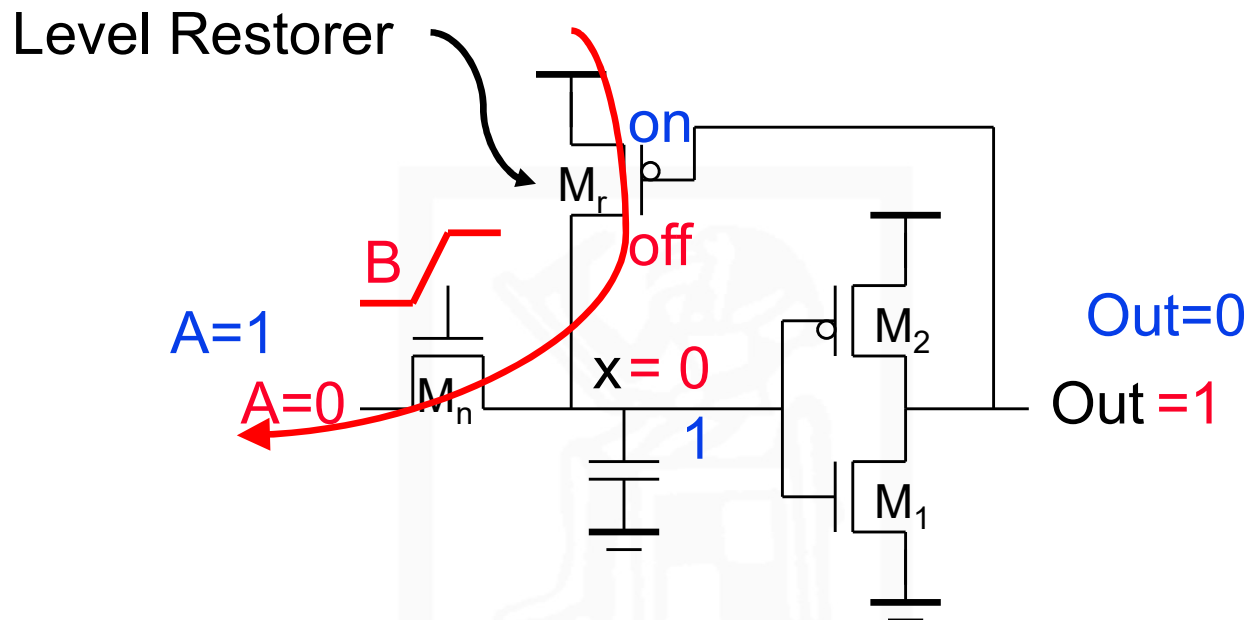

- ❑ Full swing on x (due to Level Restorer) so no static power consumption by inverter
- ❑ No static backward current path through Level Restorer and PT since Restorer is only active when A is high
- **For correct operation  $M_r$  must be sized correctly (ratioed)**

 
# Transient Level Restorer Circuit Response



- Restorer has speed and power impacts: increases the cap at x, slowing down the gate; increases  $t_r$  (but decreases  $t_f$ )
 
# Solution 2: Multiple $V_T$ Transistors


- Technology solution: Use (near) zero  $V_T$  devices for the NMOS PTs to eliminate *most* of the threshold drop (body effect still in force preventing full swing to  $V_{DD}$ )



- ❑ Impacts static power consumption due to subthreshold currents flowing through the PTs (even if  $V_{GS}$  is below  $V_T$ )

# Solution 3: Transmission Gates (TGs)

- Most widely used solution

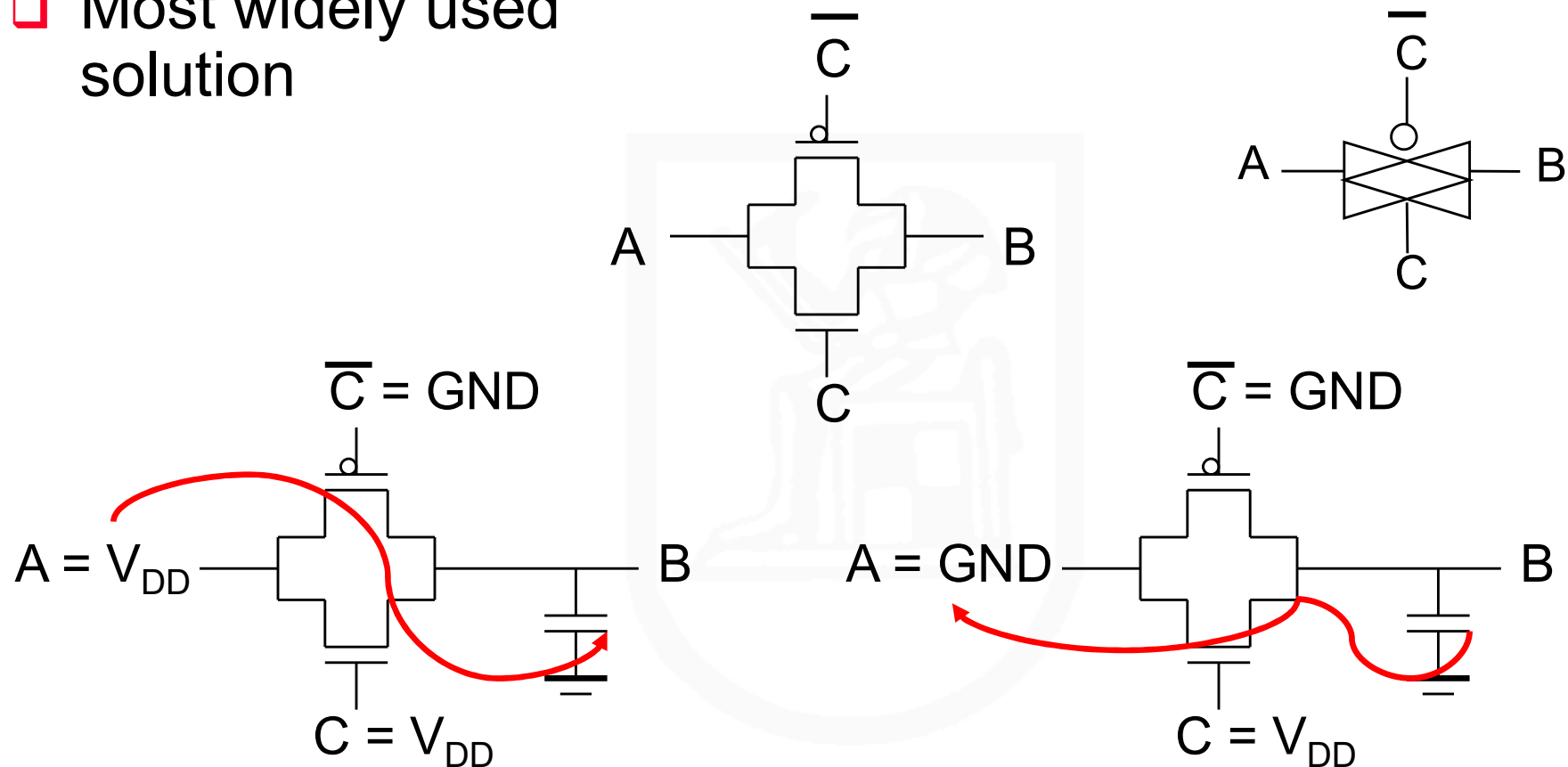

- Full swing *bidirectional* switch controlled by the gate signal  $C$ ,  $A = B$  if  $C = 1$**