

IC Design Flows



- The MOS Transistor
- Analog and Circuit Design
- Digital Logic Families**
- Productivity Gap
- Digital Design Flows


CMOS Circuit Styles

- **Static complementary CMOS** - except during switching, output connected to either V_{DD} or GND via a low-resistance path
 - high noise margins
 - full rail to rail swing
 - V_{OH} and V_{OL} are at V_{DD} and GND, respectively
 - low output impedance, high input impedance
 - no steady state path between V_{DD} and GND (**no** static power consumption)
 - delay a function of load capacitance and transistor resistance
 - comparable rise and fall times (under the appropriate transistor sizing conditions)
- **Dynamic CMOS** - relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes
 - simpler, faster gates, cycle has pre-charge and evaluation phases
 - increased sensitivity to noise

Static Inverter Behavior

- Steady-state parameters of a gate – *static behavior* – tell how robust a circuit is with respect to both variations in the manufacturing process and to noise disturbances.
- Digital circuits perform operations on Boolean variables
 $x \in \{0, 1\}$
- A logical variable is associated with a *nominal voltage level* for each logic state
 
$$1 \Leftrightarrow V_{OH} \text{ and } 0 \Leftrightarrow V_{OL}$$



$$V_{OH} = ! (V_{OL})$$



$$V_{OL} = ! (V_{OH})$$

- Difference between V_{OH} and V_{OL} is the logic or *signal swing* V_{sw}

DC Operation


Voltage Transfer Characteristics (VTC)

  - Plot of output voltage as a function of the input voltage




Mapping Logic Levels to the Voltage Domain

 - The regions of acceptable high and low voltages are delimited by V_{IH} and V_{IL} that represent the points on the VTC curve where the gain = -1




Noise Margins

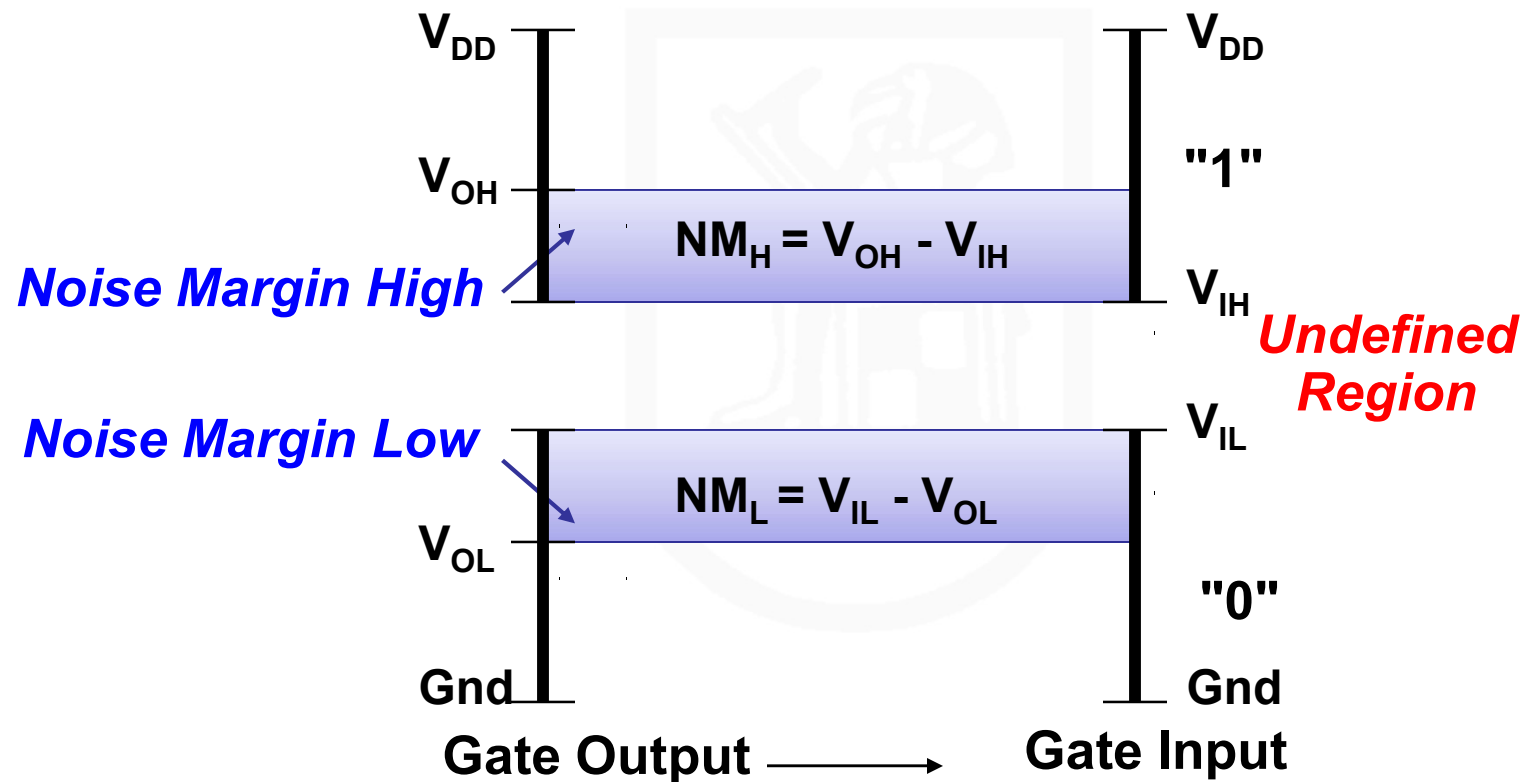- For robust circuits, want the “0” and “1” intervals to be as large as possible




- Large noise margins are desirable, but not sufficient


The Regenerative Property

 
 
$$v_1 = f(v_0) \Rightarrow v_1 = \text{finv}(v_2)$$



Regenerative Gate

 


Nonregenerative Gate

- The VTC must have a transient region with a gain greater than 1 (in absolute value) bordered by two valid zones where the gain is smaller than 1. Such a gate has two stable operating points.

The Regenerative Property

 
- A gate with regenerative property ensures that a disturbed signal converges back to a nominal voltage level



Noise Immunity

- Noise margin expresses the ability of a circuit to overpower a noise source
 - noise sources: supply noise, cross talk, interference, offset
- Absolute noise margin values are deceptive
 - a floating node is more easily disturbed than a node driven by a low impedance (in terms of voltage)
- **Noise immunity** expresses the ability of the system to process and transmit information correctly in the presence of noise
- For good noise immunity, the signal swing (i.e., the difference between V_{OH} and V_{OL}) and the noise margin have to be large enough to overpower the impact of fixed sources of noise

Noise in Digital Integrated Circuits

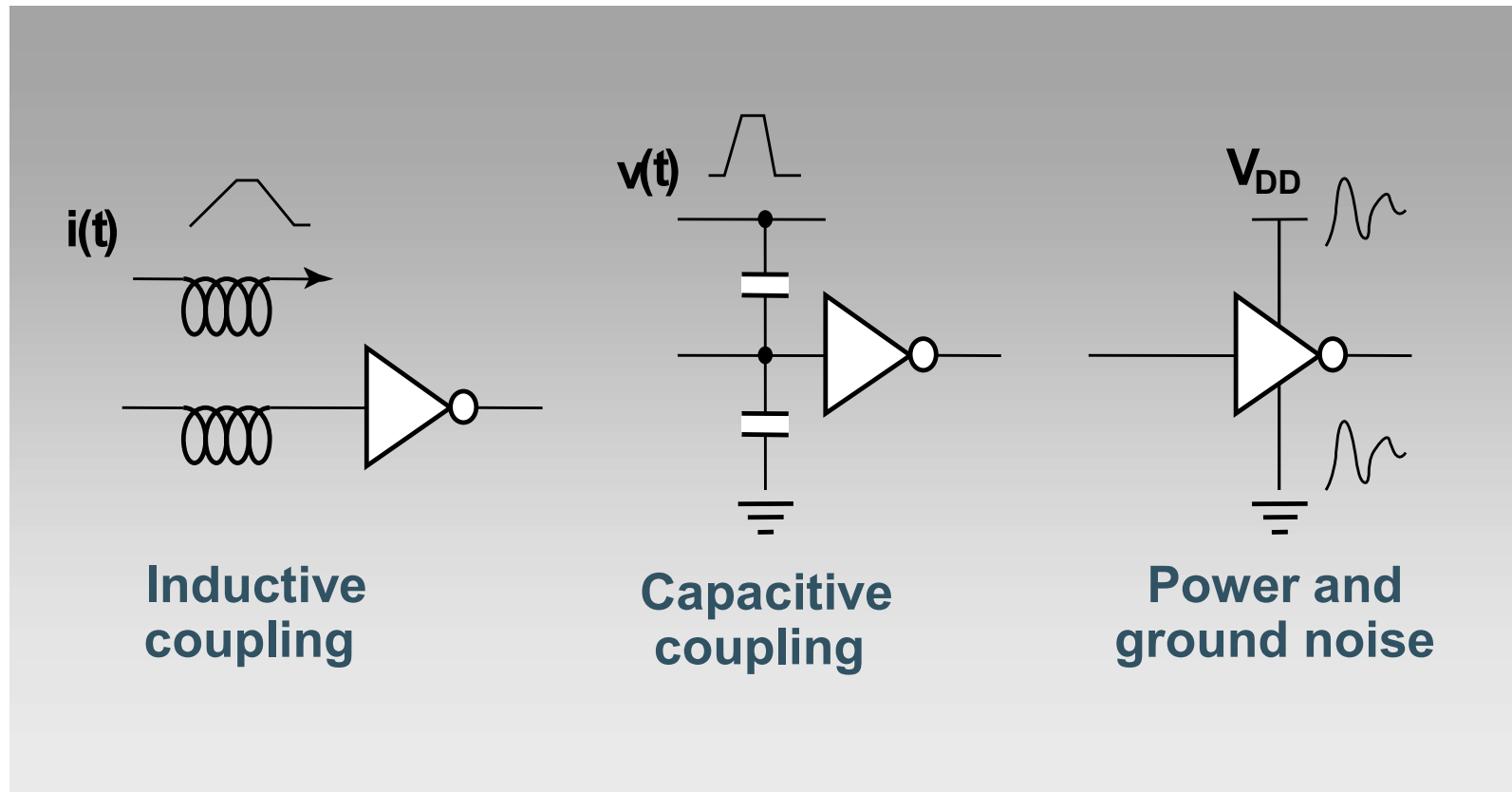


Directivity

- A gate must be **unidirectional**: changes in an output level should not appear at any unchanging input of the same circuit
 - In real circuits, *full* directivity is an illusion (e.g., due to capacitive coupling between inputs and outputs)
- Key metrics: **output impedance** of the driver and **input impedance** of the receiver
 - ideally, the output impedance of the driver should be zero and
 - input impedance of the receiver should be infinity

Fan-In and Fan-Out


- ❑ **Fan-out – number of load gates connected to the output of the driving gate**

- gates with large fan-out are slower

 


- ❑ **Fan-in – the number of inputs to the gate**

 - gates with large fan-in are bigger and slower



The Ideal Inverter

 - **The ideal gate should have**
 - infinite gain in the transition region
 - a gate threshold located in the middle of the logic swing
 - high and low noise margins equal to half the swing
 - input and output impedances of infinity and zero, resp.




$$R_i = \infty$$

$$R_o = 0$$

$$\text{Fanout} = \infty$$


$$NM_H = NM_L = V_{DD}/2$$

Delay Definitions

 

Modeling Propagation Delay

 - Model circuit as first-order RC network



$$v_{out}(t) = (1 - e^{-t/\tau})V$$

$$\text{where } \tau = RC$$

Time to reach 50% point is
 $t = \ln(2) \tau = 0.69 \tau$

Time to reach 90% point is
 $t = \ln(9) \tau = 2.2 \tau$

□ Matches the delay of an inverter gate

Power and Energy Dissipation

- Power consumption: how much energy is consumed per operation and how much heat the circuit dissipates
 - supply line sizing (determined by **peak power**)

$$P_{\text{peak}} = V_{\text{dd}} i_{\text{peak}}$$

- battery lifetime (determined by **average power dissipation**)

$$p(t) = v(t)i(t) = V_{\text{dd}} i(t)$$

$$P_{\text{avg}} = 1/T \int p(t) dt = V_{\text{dd}}/T \int i_{\text{dd}}(t) dt$$

- packaging and cooling requirements
- Two important components: static and **dynamic**

$$\downarrow f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{\text{clock}} \downarrow$$

$$P \text{ (watts)} = C_L V_{\text{dd}}^2 f_{0 \rightarrow 1} + t_{\text{sc}} V_{\text{dd}} I_{\text{peak}} f_{0 \rightarrow 1} + V_{\text{dd}} I_{\text{leakage}}$$

Power and Energy Dissipation

- Propagation delay and the power consumption of a gate are related
- Propagation delay is (mostly) determined by the speed at which a given amount of energy can be stored on the gate capacitors
 - the faster the energy transfer (higher power dissipation) the faster the gate
- For a given technology and gate topology, the product of the power consumption and the propagation delay is a constant
 - **Power-delay product (PDP) – energy consumed by the gate per switching event = $P_{av} \times t_p$**
- An ideal gate is one that is fast and consumes little energy, so the ultimate quality metric is
 - **Energy-delay product (EDP) = $E \times t_p = \text{power} \times \text{delay}^2$**