



Computer Engineering Department
Faculty of Engineering
Cairo University

CMP3020 VLSI Design

Problem Set #2

Review: sheet#1 problem 14

Problem #1

Determine the mode of operation (saturation, linear, or cutoff) and drain current I_d for each of the following configurations given below.

Assume: $K_n = 115 \mu A/V^2$, $V_{to} = 0.43$, $\lambda = 0.06 V^{-1}$, $W/L = 1$, $V_{sb} = 0$

- a. NMOS: $V_{gs} = 2.5$, $V_{ds} = 2.5$
- b. NMOS: $V_{gs} = 3.3$, $V_{ds} = 2.2$
- c. NMOS: $V_{gs} = 0.3$, $V_{ds} = 0.1$
- d. NMOS: $V_{gs} = 0.6$, $V_{ds} = 0.1$

Problem #2: sheet#1 problem 17

Problem #3

Two Transistor M1 has $V_{oh} = 5$, $V_{lo} = 1$, $V_{ih} = 3$, $V_{il} = 1.5$ and another transistor M2 has $V_{oh} = 4.5$, $V_{lo} = 0.5$, $V_{ih} = 4$, $V_{il} = 1$, which transistor is more noise immune and why?

Problem #4

[E, None, 3.3.2] Below in Figure 0.8 is an I-V transfer curve for an NMOS transistor. In this problem, the objective is to use this I-V curve to obtain information about the transistor. The transistor has $(W/L) = (1\mu/1\mu)$. It may also be assumed that velocity saturation does not play a role in this example. Also assume $-2\Phi_F = 0.6V$. Using Figure 0.8 determine the following parameters: device V_{TO} , γ , λ .


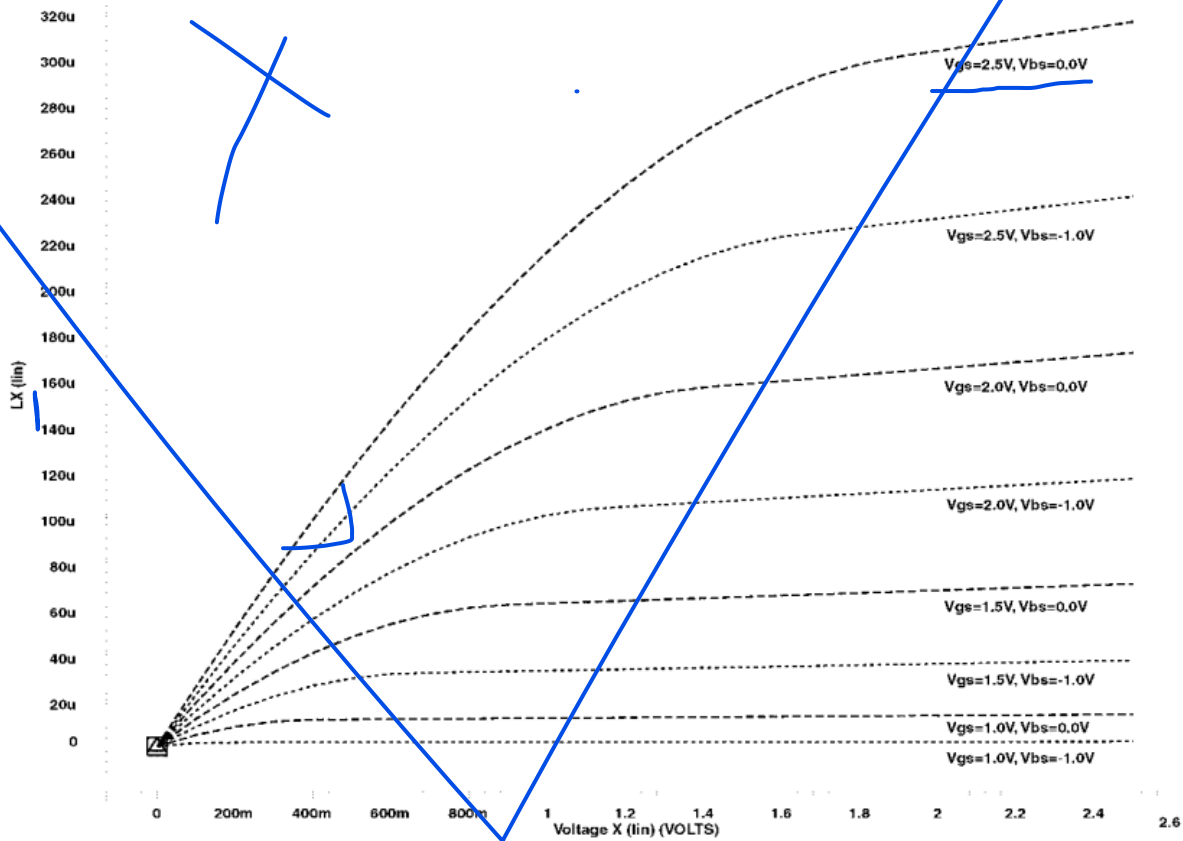


Figure 0.8 I-V curves

Problem #5

How Many Transistor in Each Fig?

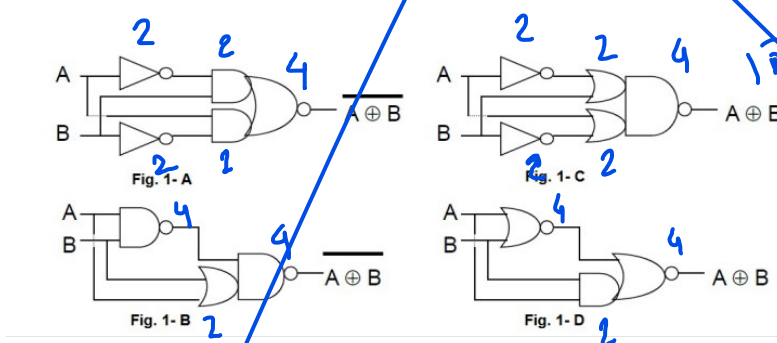

ay haga d5la 3la not bndrb el inputs
bto3ha fe 2