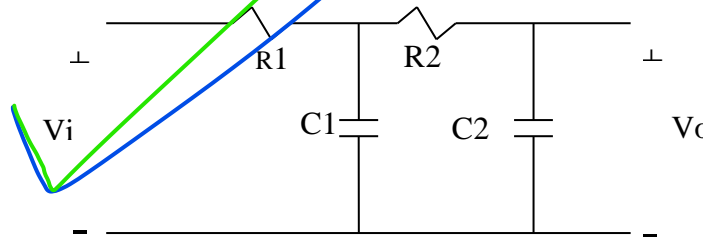



Sheet 2 Mathematical Modeling

1. For the circuit shown, obtain the transfer function $V_o(s)/V_i(s)$.




$$\begin{aligned} V_o &= I / (SC2) \\ I &= I_2 + I_3 \\ V_{in} &= IR_1 + I_2 / (SC1) \\ V_{in} &= IR_1 + I_3 (R_2 + 1/SC2) \\ \text{solve 3 equations simult} \\ \text{kirshoff law} \\ \text{get TF} \end{aligned}$$

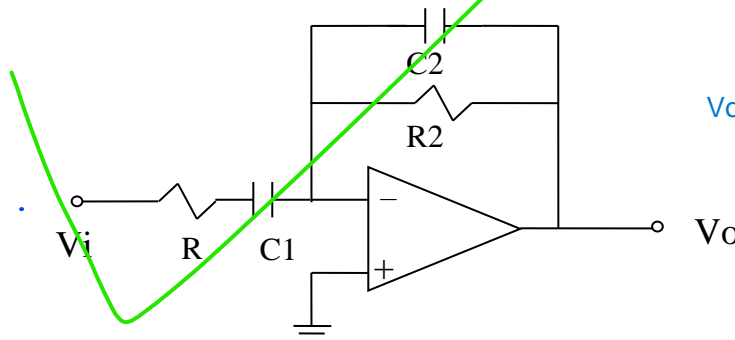2. For the Ideal Op-amp circuit shown, obtain the transfer function $V_o(s)/V_i(s)$




$$V_{out}/v_{in} = -Z_2 / Z_1$$

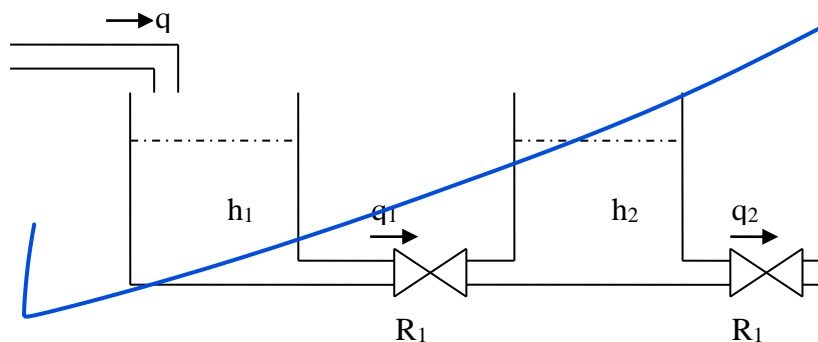3. The figure shows a process plant containing of two tanks of areas A_1 and A_2 . Derive the transfer function that relates q_2 to q .



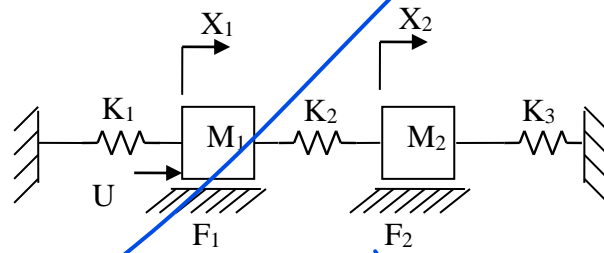4. Derive the differential equations that represent the mechanical system shown, where U is a force that affects the mass M_1 and hence derive the transfer functions $X_1(s)/U(s)$ and $X_2(s)/U(s)$. If the force U has a value of 1 N find the steady state values of X_1 and X_2 .



it is all about math fa to be solved tomorrow